
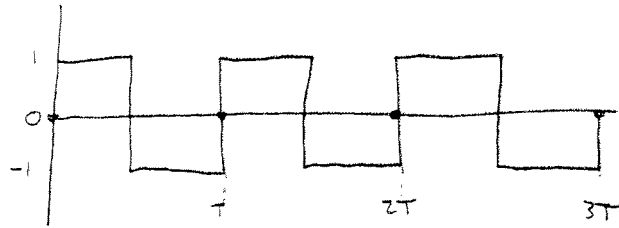


13.19

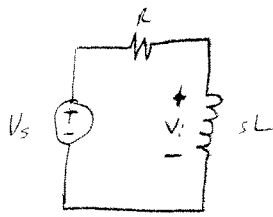

$$V_s = u(t) - 2u(t - \frac{T}{2}) + 2u(t - T) - 2u(t - \frac{3T}{2}) + 2u(t - 2T) - 2u(t - \frac{5T}{2}) + 2u(t - 3T)$$

$$V_i = V_s \frac{sL}{sL + R} = V_s \frac{s}{s + \frac{R}{L}}$$

$$0 \leq t \leq \frac{T}{2}$$

USING #6

$$\left( \frac{s}{s + \frac{R}{L}} \right) u(t) = \left( \frac{s}{s + \frac{R}{L}} \right) \left( \frac{1}{s} \right) u(t) = \frac{1}{s + \frac{R}{L}} u(t)$$

USING #41

SUBSTITUTE FOR  $a$

$$e^{-at} u(t) \Leftrightarrow \frac{1}{s + a}$$

$$e^{-\frac{R}{L}t} u(t) \Leftrightarrow \frac{1}{s + \frac{R}{L}}$$

$$\frac{T}{2} \leq t \leq T$$

$$-2u(t - \frac{T}{2}) \frac{s}{s + \frac{R}{L}}$$

USING PAIR #7

$$u(t - a) \Leftrightarrow \frac{e^{-as}}{s}$$

AND SUBSTITUTE FOR  $a$

$$u(t - \frac{T}{2}) \Leftrightarrow \frac{e^{-\frac{T}{2}s}}{s}$$

AND USING PROPERTY #3 TO FACTOR IN SCALAR

$$\frac{2e^{-\frac{T}{2}s}}{s} \frac{s}{s + \frac{R}{L}} = \frac{-2e^{-\frac{T}{2}s}}{s + \frac{R}{L}}$$

USING PAIR #42


$$e^{-a(t-b)} u(t-b) \Leftrightarrow \frac{e^{-bs}}{s + a}$$

SUBSTITUTE FOR  $a$ , AND USE PROPERTY #3 FOR

SCALAR MULTIPLICATION WE GET:

$$-2e^{-\frac{R}{L}(t-\frac{T}{2})} \Leftrightarrow \frac{-2e^{-\frac{T}{2}S}}{S}$$

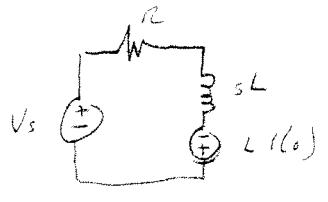BUT WE MUST ALSO TAKE INTO ACCOUNT THE INITIAL VALUE GIVEN FROM THE PREVIOUS TIME INTERVAL. TO CONSIDER THIS WE MUST FOLLOW THE INDUCTOR TRANSFORM MODEL.



THIS MEANS THAT WE ADD THE VOLTAGE ACROSS THE INDUCTOR FOR OUR SECOND TIME PERIOD ( $\frac{T}{2} \rightarrow T$ ) AND ADD IT WITH ITS INITIAL VALUE, BUT TO FIND ITS INITIAL CONDITION WE MUST FIND THE FINAL VALUE FROM THE PREVIOUS TIME PERIOD ( $0 \rightarrow \frac{T}{2}$ ).

$$e^{-\frac{R}{L}(\frac{T}{2})} u(t) = \text{FINAL VALUE OF PREVIOUS TIME PERIOD } (0 \rightarrow \frac{T}{2}).$$

$$\boxed{\left[-2e^{-\frac{R}{L}(t-\frac{T}{2})} + e^{-\frac{R}{L}(\frac{T}{2})}\right] u(t) = V_L(t)} \quad \left(\frac{T}{2} \leq t \leq T\right)$$

$$T \leq t \leq \frac{3T}{2}$$

$$V_i(t) = ZU(t-T) \frac{S}{S + \frac{R}{L}}$$

USING PAIR # 7  $U(t-a) \Leftrightarrow \frac{e^{-as}}{s}$

SUBSTITUTE FOR  $a$ , AND USE PROPERTY # 3 TO FACTOR IN SCALAR

$$ZU(t-T) \Leftrightarrow \frac{e^{-Ts}}{s}$$

$$V_i(t) = \frac{Ze^{-Ts}}{s} \frac{S}{S + \frac{R}{L}}$$

$$= \frac{Ze^{-Ts}}{S + \frac{R}{L}}$$

USING PROPERTY # 42  $e^{-a(t-b)} U(t-b) \Leftrightarrow \frac{e^{-bs}}{s+a}$

SUBSTITUTE FOR  $a$ , AND USE PROPERTY # TO FACTOR IN SCALAR

$$V_i(t) = Ze^{-\frac{R}{L}(t-T)} U(t)$$


BUT AGAIN WE MUST FOLLOW THE SAME MODEL MENTIONED ON PAGE TWO, SO FOLLOWING THE SAME ANALYSIS WE GET

$$V_i(t) = \left[ -Ze^{-\frac{R}{L}(T-\frac{T}{2})} + e^{-\frac{R}{L}(\frac{T}{2})} \right] U(t)$$

IS THE FINAL VALUE OF  $t = T$


SO  $V_i(t) = \left[ -Ze^{-\frac{R}{L}(\frac{T}{2})} + e^{-\frac{R}{L}(\frac{T}{2})} + Ze^{-\frac{R}{L}(t-T)} \right] U(t)$

WHERE  $T \leq t \leq \frac{3T}{2}$

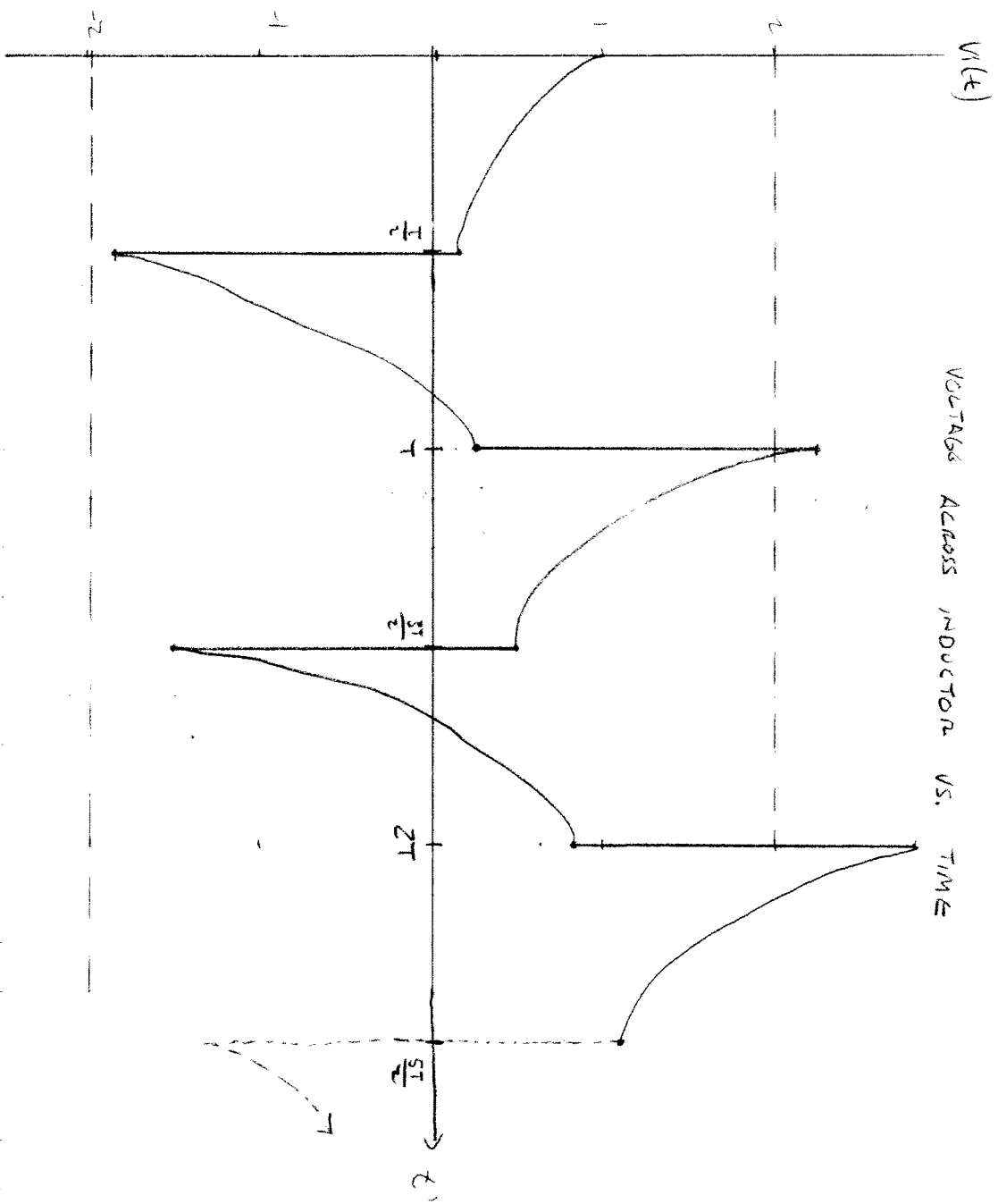


AS YOU CAN SEE FROM THE GRAPH THE VOLTAGE ACROSS THE INDUCTOR INCREASES AS TIME INCREASES, THIS IS BECAUSE OF THE INITIAL VOLTAGE ACROSS THE INDUCTOR FROM THE PREVIOUS TIME PERIOD.

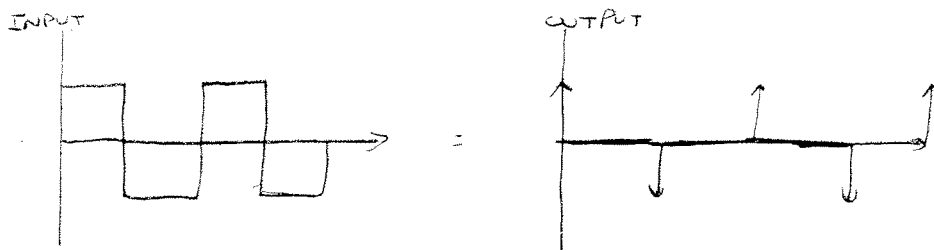PART B A DIFFERENTIATING CIRCUIT WOULD TRANSFORM OUR INPUT VOLTAGE AS FOLLOWS



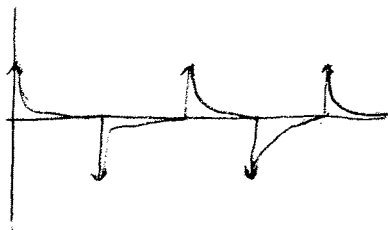OUR CIRCUIT DOES THIS AS WELL. BUT IT LOOKS MORE LIKE THE FOLLOWING





THEREFORE WE CAN CLASSIFY OUR CIRCUIT AS A DIFFERENTIATING CIRCUIT.

PART C

SINCE WE ARE GIVEN  $R \gg L$ , THEN WE CAN EVALUATE  $\tau = \frac{L}{R}$  AS RELATIVELY SMALL. USING THE TABLE ON PAGE 218 IN THE "TRANSIENT BEHAVIOR IN THE TIME DOMAIN" SECTION, WE CAN VERIFY THAT WITH A SERIES RL CIRCUIT WITH A SMALL  $\tau$ , THE INDUCTOR VOLTAGE IS PROPORTIONAL TO THE DERIVATIVE OF THE INPUT VOLTAGE.

13.20

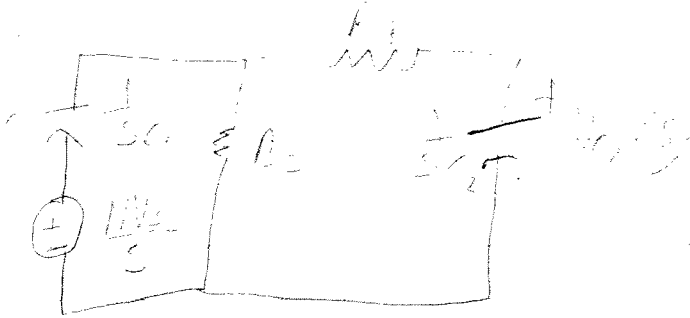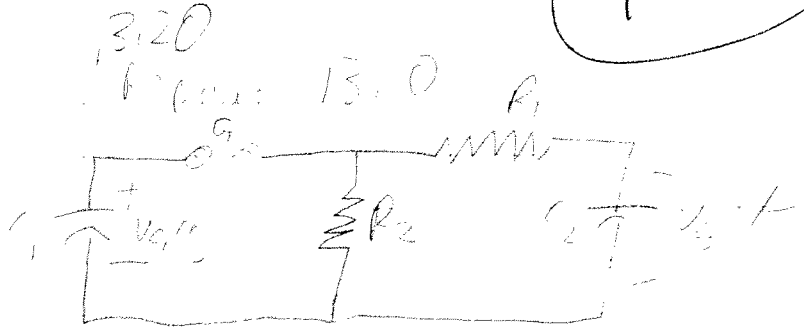

$$V_2 = \frac{V_0 \cdot \frac{1}{sC_2}}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} \cdot \left( \frac{1}{1 + sC_2 R_2} \right)$$

$$= \frac{V_0}{s} \cdot \frac{\frac{1}{sC_2}}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} \cdot \left( \frac{1}{1 + sC_2 R_2} \right)$$

$$= \frac{V_0}{s} \cdot \frac{\frac{1}{sC_2}}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} \cdot \left( \frac{1}{1 + sC_2 R_2} \right)$$

$$= \frac{V_0}{s} \cdot \frac{\frac{1}{sC_2}}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} \cdot \left( \frac{1}{1 + sC_2 R_2} \right)$$

$$= \frac{NV_0 C_1 R_2}{(R_2 C_1 R_1 C_2) s^2 + s(R_2 C_1 + R_1 C_2 + R_2 C_2) + 1}$$

$$= \frac{\frac{NV_0}{R_1 R_2 C_2}}{s^2 + s \left( \frac{R_2 C_1 + R_1 C_2 + R_2 C_2}{R_2 C_1 R_2} \right) + \frac{1}{R_2 C_1 R_2 C_2}} = \frac{\frac{NV_0}{R_1 R_2 C_2}}{s^2 + \left( \frac{R_2 C_1 + R_1 C_2 + R_2 C_2}{R_2 C_1 R_2} \right) s + \frac{1}{R_2 C_1 R_2 C_2}}$$

$$\frac{1}{s^2} = \frac{1}{(s-a)(s-b)}$$

$$= \frac{1}{k_1(s-a) + k_2(s-b)} \quad \text{with } k_1 = \frac{1}{a-b}, k_2 = \frac{1}{b-a}$$

Partial Fractions

$$\frac{e^{-at} - e^{-bt}}{s^2} = \frac{1}{s-a} - \frac{1}{s-b}$$

$$= \frac{1}{k_1(s-a) + k_2(s-b)} = \frac{1}{k_1(s-a) + k_2(s-b)}$$

$$= \frac{1}{k_1} \left( \frac{e^{-at} - e^{-bt}}{s-a} \right)$$

$$\frac{N \cdot V_s}{s} \left[ \left[ \frac{R_1 \cdot R_2 \cdot s \cdot C_2 + R_2}{R_1 \cdot s \cdot C_2 + 1 + R_2 \cdot s \cdot C_2} \right] \left[ \frac{1}{s \cdot C_2} \right] \right]$$

$$\left[ \frac{R_1 \cdot R_2 \cdot s \cdot C_2 + R_2}{R_1 \cdot s \cdot C_2 + 1 + R_2 \cdot s \cdot C_2} + \frac{1}{s \cdot C_1} \right] \left[ R_1 + \frac{1}{s \cdot C_2} \right]$$

$$C_1 \cdot R_2 \cdot N \cdot \frac{V_s}{\left( R_2 \cdot s^2 \cdot C_1 \cdot R_1 \cdot C_2 + R_2 \cdot s \cdot C_1 + s \cdot R_1 \cdot C_2 + 1 + s \cdot R_2 \cdot C_2 \right)}$$



$$R_1 := 1 \cdot 10^2 \quad R_2 := 1 \cdot 10^3 \quad C_1 := 1 \cdot 10^{-6} \quad C_2 := 10 \cdot 10^{-6} \quad NV_s := 30 \cdot 10^3$$

$$a := \frac{-\left(\frac{C_1 \cdot R_2 + R_1 \cdot C_2 + R_2 \cdot C_2}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}\right) - \sqrt{\left(\frac{C_1 \cdot R_2 + R_1 \cdot C_2 + R_2 \cdot C_2}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}\right)^2 - \frac{4}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}}{2}$$


$$\frac{1}{a} = 8.392 \cdot 10^{-5}$$

$$b := \frac{-\left(\frac{C_1 \cdot R_2 + R_1 \cdot C_2 + R_2 \cdot C_2}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}\right) + \sqrt{\left(\frac{C_1 \cdot R_2 + R_1 \cdot C_2 + R_2 \cdot C_2}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}\right)^2 - \frac{4}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}}{2}$$

$$\frac{1}{b} = 0.012$$


$$t := 0, \frac{1}{100} \cdot \max\left(\left|\frac{1}{a}\right|, \left|\frac{1}{b}\right|\right) \dots 4 \cdot \max\left(\left|\frac{1}{a}\right|, \left|\frac{1}{b}\right|\right)$$
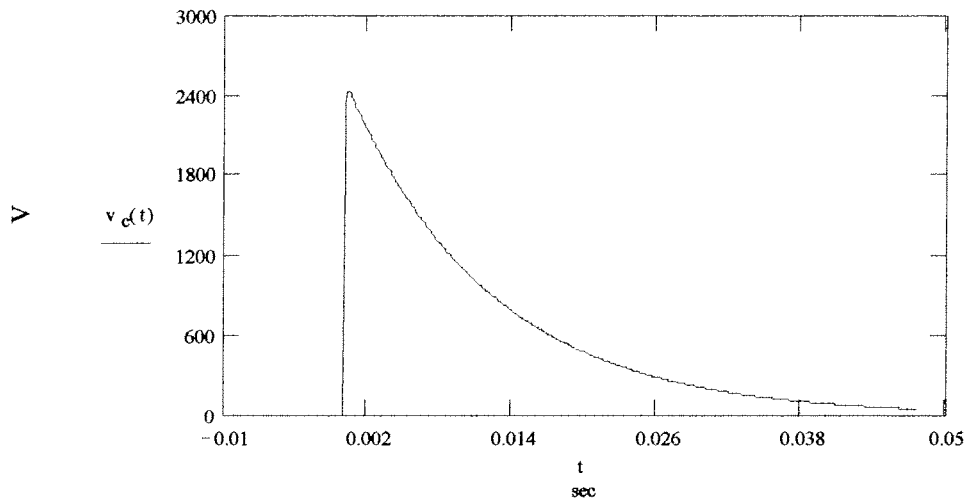
$$v_c(t) := \frac{NV_s}{R_1 \cdot C_2} \cdot \left(\frac{e^{-a \cdot t} - e^{-b \cdot t}}{b - a}\right) \cdot \Phi(t)$$



13.20

## Problem 13-20

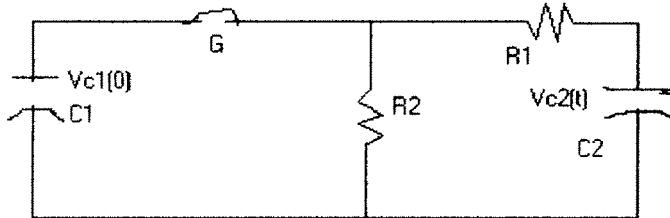

The solution for the voltage across the capacitor  $C_2$  is obtained using voltage division twice. The first division gets me voltage across  $R_2$  (which is the same as the voltage across  $R_1 + C_2$ ). The second voltage division divides the voltage across  $R_2$  between  $C_2$  and  $R_1$ . The first voltage division is the first bracketed part of the equation. For notation, I used absolute value bars to indicate parallelism. So in the following equation,  $R_2$  is in parallel with  $(R_1 + 1/S \cdot C_2)$ .

$$V_{c2}(s) = \left[ \frac{R_2 \left| R_1 + \frac{1}{S \cdot C_2} \right|}{R_2 \left| R_1 + \frac{1}{S \cdot C_2} \right| + \frac{1}{S \cdot C_1}} \right] \left[ \frac{\frac{1}{S \cdot C_2}}{\frac{1}{S \cdot C_2} + R_1} \right] \frac{N V_s}{S}$$

Expand out the parallel resistor equations:

$$V_{c2}(s) = \frac{\frac{R_2 \cdot R_1 + \frac{R_2}{S \cdot C_2}}{R_2 + R_1 + \frac{1}{S \cdot C_2}} \cdot \frac{1}{S \cdot C_2} \cdot \frac{N \cdot V_s}{S}}{\frac{R_2 \cdot R_1 + \frac{R_2}{S \cdot C_2}}{R_2 + R_1 + \frac{1}{S \cdot C_2}} + \frac{1}{S \cdot C_1}}$$

Simplifying the above equation results in: (MathCAD simplification)

$$V_{c2}(s) = R_2 \cdot \frac{C_1}{(R_2 \cdot S^2 \cdot C_1 \cdot R_1 \cdot C_2 + R_2 \cdot S \cdot C_1 + R_2 \cdot S \cdot C_2 + R_1 \cdot S \cdot C_2 + 1)} \cdot N \cdot V_s$$

The function corresponding to this Laplace transform is number 125.

$$\left( \frac{e^{-at} - e^{-bt}}{b - a} \right) \cdot \Phi(t) \quad a \neq b \quad \iff \quad \frac{1}{(s + a) \cdot (s + b)}$$

We are interested in the denominator so we can find a and b (1/a and 1/b are time constants):

$$R_2 \cdot S^2 \cdot C_1 \cdot R_1 \cdot C_2 + R_2 \cdot S \cdot C_1 + R_2 \cdot S \cdot C_2 + R_1 \cdot S \cdot C_2 + 1$$

$$\text{Denominator} = S^2 + \frac{R_2 \cdot C_1 + R_2 \cdot C_2 + R_1 \cdot C_2}{R_2 \cdot C_1 \cdot R_1 \cdot C_2} \cdot S + \frac{1}{R_2 \cdot C_1 \cdot R_1 \cdot C_2}$$

The next page shows the equations for a and b, and the graph of the output from this voltage zapper.

$$R_1 := 100 \quad R_2 := 1000 \quad C_1 := 0.000010 \quad C_2 := 0.000001 \quad NV_s := 30000$$

$$a := \frac{\left( \frac{C_1 \cdot R_2 + C_2 \cdot R_2 + C_2 \cdot R_1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} \right) - \sqrt{\left( \frac{C_1 \cdot R_2 + C_2 \cdot R_2 + C_2 \cdot R_1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} \right)^2 - \frac{4}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}}{2}$$

$$b := \frac{\left( \frac{C_1 \cdot R_2 + C_2 \cdot R_2 + C_2 \cdot R_1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} \right) + \sqrt{\left( \frac{C_1 \cdot R_2 + C_2 \cdot R_2 + C_2 \cdot R_1}{R_1 \cdot R_2 \cdot C_1 \cdot C_2} \right)^2 - \frac{4}{R_1 \cdot R_2 \cdot C_1 \cdot C_2}}}{2}$$


$$\frac{1}{a} = 9.083 \cdot 10^{-5}$$


$$\frac{1}{b} = 0.011$$

$$t := 0, \frac{1}{100} \cdot \max \left[ \left[ \frac{1}{a} \right], \left[ \frac{1}{b} \right] \right] .. 4 \cdot \max \left[ \left[ \frac{1}{a} \right], \left[ \frac{1}{b} \right] \right]$$

$$V_c(t) := \left[ \frac{NV_s}{R_1 \cdot C_2} \cdot \left( \frac{e^{-a \cdot t} - e^{-b \cdot t}}{b - a} \right) \cdot \Phi(t) \right]$$

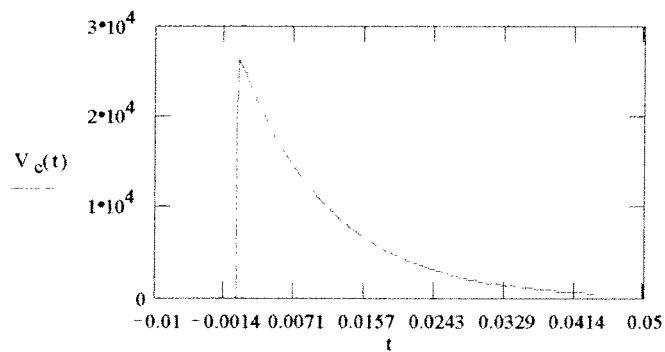This equation is the time domain solution.




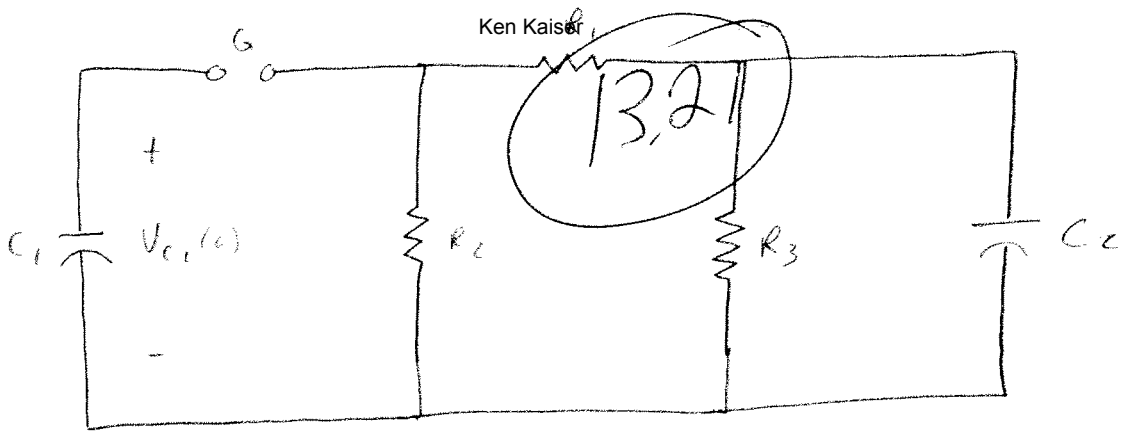

$R_1 = 100 \Omega$     $R_2 = 1k\Omega$     $C_1 = 10\mu F$     $C_2 = 1\mu F$     $V_{C1} = 50\mu V$

ALSO

$V_{C1} = NV_S$

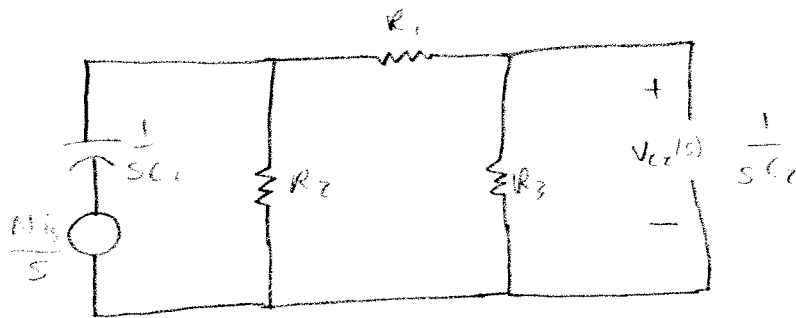

SIMPLIFY THE EQUATION IN LAPLACE  
SEE THE NEXT PAGE

$$V_{C2} := \frac{N \cdot V_s}{s} \cdot \frac{\left[ \frac{1}{R_2} + \frac{1}{R_1 + \left( \frac{1}{R_3} + s \cdot C_2 \right)^{-1}} \right]^{-1}}{\left[ \frac{1}{R_2} + \frac{1}{R_1 + \left( \frac{1}{R_3} + s \cdot C_2 \right)^{-1}} \right]^{-1} + \frac{1}{s \cdot C_2}} \cdot \frac{\left( \frac{1}{R_3} + s \cdot C_2 \right)^{-1}}{\left( \frac{1}{R_3} + s \cdot C_2 \right)^{-1} + R_1}$$

$$V_{C2} := V_s \cdot N \cdot R_2 \cdot C_2 \cdot \frac{R_3}{\left( R_2 \cdot s \cdot C_2 \cdot R_1 + R_2 \cdot s^2 \cdot C_2^2 \cdot R_1 \cdot R_3 + 2 \cdot R_2 \cdot s \cdot C_2 \cdot R_3 + R_1 + R_1 \cdot s \cdot C_2 \cdot R_3 + R_3 + R_2 \right)}$$

TABLE #125 IS USED

Ken Kaiser

$$\left[ \frac{e^{-at} - e^{-bt}}{b-a} \right] u(t) \quad a \neq b \Rightarrow \frac{1}{(s+a)(s+b)}$$

$$V_{c2} = \frac{V_S N R_2 R_3 C_2}{s^2 (R_1 R_2 R_3 C_2^2) + s (2R_2 R_3 C_2 + R_1 R_3 C_2 + R_1 R_2 C_2) + (R_1 + R_2 + R_3)} \Rightarrow \frac{1}{(s+a)(s+b)}$$

$$\begin{aligned} s+a &= 0 & s+b &= 0 \\ s &= -a & s &= -b \end{aligned}$$

THE QUADRATIC FORMULA IS USED TO OBTAIN  $a$  &  $b$ .

$$a = \frac{-(2R_2 R_3 C_2 + R_1 R_3 C_2 + R_1 R_2 C_2) + \sqrt{(2R_2 R_3 C_2 + R_1 R_3 C_2 + R_1 R_2 C_2)^2 - 4(R_1 R_2 R_3 C_2^2)(R_1 + R_2 + R_3)}}{2(R_1 R_2 R_3 C_2^2)}$$

$$b = \frac{-(2R_2 R_3 C_2 + R_1 R_3 C_2 + R_1 R_2 C_2) - \sqrt{(2R_2 R_3 C_2 + R_1 R_3 C_2 + R_1 R_2 C_2)^2 - 4(R_1 R_2 R_3 C_2^2)(R_1 + R_2 + R_3)}}{2(R_1 R_2 R_3 C_2^2)}$$

THE FUNCTION FOR  $V_c(t)$  IS.

$$V_c(t) = N V_S R_2 R_3 C_2 \left( \frac{e^{-at} - e^{-bt}}{b-a} \right) u(t) \quad a \neq b$$

USING THE GIVEN VALUES THE FOLLOWING ANALYSIS IS OBTAINED.

$$R_1 := 100$$

$$R_2 := 1000$$

$$C_1 := 10 \cdot 10^{-6}$$

$$C_2 := 1 \cdot 10^{-6}$$

$$NV_s := 30000$$

$$R_3 := 100$$

$$a := \frac{-(2 \cdot R_2 \cdot R_3 \cdot C_2 + R_1 \cdot R_3 \cdot C_2 + R_1 \cdot R_2 \cdot C_2) + \sqrt{(2 \cdot R_2 \cdot R_3 \cdot C_2 + R_1 \cdot R_3 \cdot C_2 + R_1 \cdot R_2 \cdot C_2)^2 - 4 \cdot (R_1 \cdot R_2 \cdot R_3 \cdot C_2^2) \cdot (R_1 + R_2 + R_3)}}{2 \cdot (R_1 \cdot R_2 \cdot R_3 \cdot C_2^2)}$$

$$\frac{1}{a} = 2.205 \cdot 10^{-4}$$


$$b := \frac{-(2 \cdot R_2 \cdot R_3 \cdot C_2 + R_1 \cdot R_3 \cdot C_2 + R_1 \cdot R_2 \cdot C_2) - \sqrt{(2 \cdot R_2 \cdot R_3 \cdot C_2 + R_1 \cdot R_3 \cdot C_2 + R_1 \cdot R_2 \cdot C_2)^2 - 4 \cdot (R_1 \cdot R_2 \cdot R_3 \cdot C_2^2) \cdot (R_1 + R_2 + R_3)}}{2 \cdot (R_1 \cdot R_2 \cdot R_3 \cdot C_2^2)}$$

$$\frac{1}{b} = 3.778 \cdot 10^{-5}$$

$$t := 0, \frac{1}{100} \cdot \max \left[ \begin{array}{c} \frac{1}{a} \\ \frac{1}{b} \end{array} \right] .. 4 \cdot \max \left[ \begin{array}{c} \frac{1}{a} \\ \frac{1}{b} \end{array} \right]$$
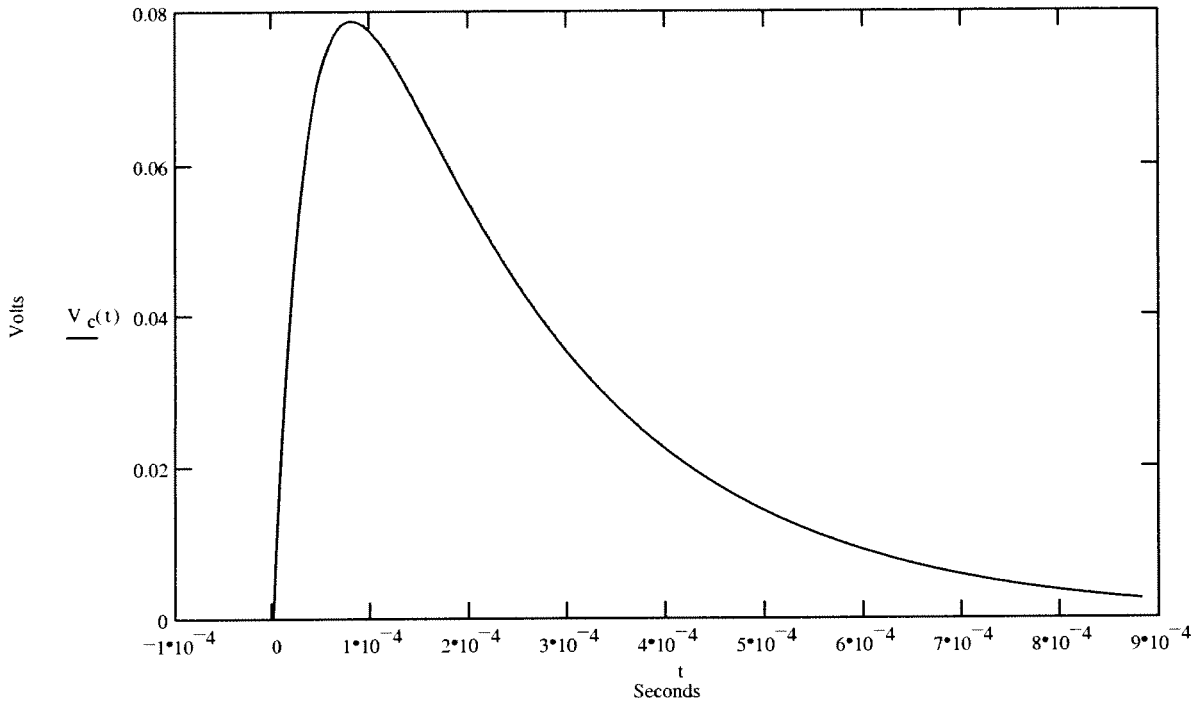
$$V_c(t) := (NV_s \cdot R_2 \cdot R_3 \cdot C_2) \cdot \left( \frac{e^{-at} - e^{-bt}}{b - a} \right) \cdot \Phi(t)$$






13.2

Ken Kaiser


Problem 13.21

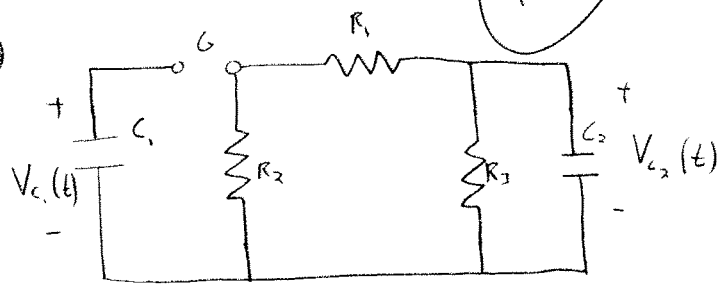

- $C_1 = 10 \mu\text{F}$
- $C_2 = 1 \mu\text{F}$
- $R_1 = 100 \Omega$
- $R_2 = 1 \text{ k}\Omega$
- $R_3 = 100 \Omega$

Numbers changed

$V_{c1}(0) = 30 \text{ mV}$

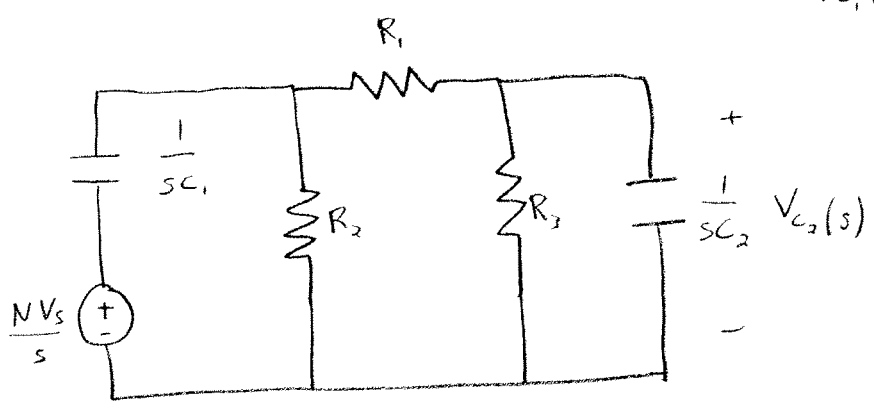

$$V_{c2}(s) = \frac{NV_s}{s} \times \left[ \frac{R_2 // (R_1 + R_3 // \frac{1}{sC_2})}{\frac{1}{sC_1} + R_2 // (R_1 + R_3 // \frac{1}{sC_2})} \right] \left[ \frac{R_3 // \frac{1}{sC_2}}{R_1 + R_3 // \frac{1}{sC_2}} \right]$$

$$V_{c2}(s) = \frac{NV_s}{s} \left[ \frac{R_2 // \left( R_1 + \frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}} \right)}{\frac{1}{sC_1} + R_2 // \left( R_1 + \frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}} \right)} \right] \left[ \frac{\frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}}}{R_1 + \frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}}} \right]$$

$$V_{c2}(s) = \frac{NV_s}{s} \left[ \frac{R_2 \left( R_1 + \frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}} \right)}{R_2 + R_1 + \frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}}} \right] \left[ \frac{\frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}}}{R_1 + \frac{R_3 \frac{1}{sC_2}}{R_3 + \frac{1}{sC_2}}} \right]$$

$$V_{C_2}(s) = \frac{V_s N R_2 R_3 C_2}{(R_1 R_2 R_3 C_2^2) s^2 + (R_1 C_2 R_3 + 2 R_2 R_3 C_2 + R_1 R_2 C_2) s + (R_1 + R_2 + R_3)}$$

$$V_{C_2}(s) = \frac{V_s N R_2 R_3 C_2}{s^2 + \left( \frac{R_1 C_2 R_3 + 2 R_2 R_3 C_2 + R_1 R_2 C_2}{R_1 R_2 R_3 C_2^2} \right) s + \frac{R_1 + R_2 + R_3}{R_1 R_2 R_3 C_2^2}}$$

$$V_{C_2}(s) = \frac{V_s N R_2 R_3 C_2}{s^2 + 2 \left( \frac{R_1 R_3 + 2 R_2 R_3 + R_1 R_2}{2 R_1 R_2 R_3 C_2} \right) s + \frac{R_1 + R_2 + R_3}{R_1 R_2 R_3 C_2^2}}$$

This is in the form of Eq. # 154.

$$\left[ \frac{1}{\sqrt{\omega_0^2 - \alpha^2}} e^{-\alpha t} \sin(\sqrt{\omega_0^2 - \alpha^2} t) \right] u(t) \iff \frac{1}{s^2 + 2\alpha s + \omega_0^2}$$

where:  $\alpha = \left( \frac{R_1 R_3 + 2 R_2 R_3 + R_1 R_2}{2 R_1 R_2 R_3 C_2} \right)$  and  $\omega_0^2 = \frac{R_1 + R_2 + R_3}{R_1 R_2 R_3 C_2^2}$

$\sqrt{\omega_0^2 - \alpha^2}$  will give an imaginary solution so we need to rewrite in exponential form.

We can use:

$$\left( \frac{e^{-at} - e^{-bt}}{b-a} \right) u(t) \iff \frac{1}{(s+a)(s+b)}$$

Solving for a and b in MathCAD

$$a = - \left( \frac{(-R_1 R_3 C_2 - 2R_2 R_3 C_2 - R_2 C_2 R_1 + C_2 \sqrt{R_1^2 R_3^2 - 2R_1^2 R_2 R_3 + 4R_2^2 R_3^2 + R_2^2 R_1^2})}{2R_2 C_2^2 R_1 R_3} \right)$$

$$b = - \left( \frac{(-R_1 R_3 C_2 - 2R_2 R_3 C_2 - R_2 C_2 R_1 - C_2 \sqrt{R_1^2 R_3^2 - 2R_1^2 R_2 R_3 + 4R_2^2 R_3^2 + R_2^2 R_1^2})}{2R_2 R_1 R_3 C_2^2} \right)$$

$$V_{C_2}(t) = V_s N R_2 R_3 C_2 \left( \frac{e^{-at} - e^{-bt}}{b - a} \right) u(t) \quad a \neq b$$

Plotting this time function will give the response of the Voltage across  $C_2$ .

$\bullet = 1 \quad C_1 = 10 \cdot 10^{-6} \quad C_2 = 1 \cdot 10^{-6} \quad R_1 = 100 \quad R_2 = 1000 \quad R_3 = 100 \quad V_s = 30 \cdot 10^3$

$$V_{C_2}(s) := \frac{N \cdot V_s}{s} \cdot \left[ \left( \frac{1}{s \cdot C_2} \right) + \frac{\left[ \begin{array}{c} R_2 \cdot R_1 + \frac{R_3 \cdot \frac{1}{s \cdot C_2}}{R_3 + \frac{1}{s \cdot C_2}} \\ R_2 + R_1 + \frac{R_3 \cdot \frac{1}{s \cdot C_2}}{R_3 + \frac{1}{s \cdot C_2}} \end{array} \right]}{\left[ \begin{array}{c} R_2 \cdot R_1 + \frac{R_3 \cdot \frac{1}{s \cdot C_2}}{R_3 + \frac{1}{s \cdot C_2}} \\ R_2 + R_1 + \frac{R_3 \cdot \frac{1}{s \cdot C_2}}{R_3 + \frac{1}{s \cdot C_2}} \end{array} \right]} \right] \cdot \left[ \begin{array}{c} \frac{R_3 \cdot \frac{1}{s \cdot C_2}}{R_3 + \frac{1}{s \cdot C_2}} \\ R_1 + \frac{R_3 \cdot \frac{1}{s \cdot C_2}}{R_3 + \frac{1}{s \cdot C_2}} \end{array} \right]$$

$$V_{C_2}(s) := V_s \cdot N \cdot R_2 \cdot C_2 \cdot \frac{R_3}{\left( 2 \cdot R_2 \cdot R_3 \cdot s \cdot C_2 + R_2 + R_1 \cdot R_3 \cdot s \cdot C_2 + R_1 + R_3 + R_2 \cdot s^2 \cdot C_2^2 \cdot R_1 \cdot R_3 + R_2 \cdot s \cdot C_2 \cdot R_1 \right)}$$

$$V_{C_2}(s) := V_s \cdot N \cdot R_2 \cdot C_2 \cdot \frac{R_3}{\left[ R_2 \cdot s^2 \cdot C_2^2 \cdot R_1 \cdot R_3 + \left( R_1 \cdot R_3 \cdot C_2 + 2 \cdot R_2 \cdot R_3 \cdot C_2 + R_2 \cdot C_2 \cdot R_1 \right) \cdot s + R_3 + R_2 + R_1 \right]}$$

$$\left[ R_2 \cdot s^2 \cdot C_2^2 \cdot R_1 \cdot R_3 + \left( R_1 \cdot R_3 \cdot C_2 + 2 \cdot R_2 \cdot R_3 \cdot C_2 + R_2 \cdot C_2 \cdot R_1 \right) \cdot s + R_3 + R_2 + R_1 \right] = 0$$

$$\left[ \frac{1}{\left[ 2 \cdot \left[ R_2 \cdot \left[ C_2^2 \cdot \left( R_1 \cdot R_3 \right) \right] \right] \right]} \cdot \left( -R_1 \cdot R_3 \cdot C_2 - 2 \cdot R_2 \cdot R_3 \cdot C_2 - R_2 \cdot C_2 \cdot R_1 + C_2 \cdot \sqrt{R_1^2 \cdot R_3^2 - 2 \cdot R_1^2 \cdot R_3 \cdot R_2 + 4 \cdot R_2^2 \cdot R_3^2 + R_2^2 \cdot R_1^2} \right), \right.$$


$$\left. \frac{1}{\left[ 2 \cdot \left[ R_2 \cdot \left[ C_2^2 \cdot \left( R_1 \cdot R_3 \right) \right] \right] \right]} \cdot \left( -R_1 \cdot R_3 \cdot C_2 - 2 \cdot R_2 \cdot R_3 \cdot C_2 - R_2 \cdot C_2 \cdot R_1 - C_2 \cdot \sqrt{R_1^2 \cdot R_3^2 - 2 \cdot R_1^2 \cdot R_3 \cdot R_2 + 4 \cdot R_2^2 \cdot R_3^2 + R_2^2 \cdot R_1^2} \right), \right.$$


$$a := \frac{1}{\left[2 \cdot R_2 \cdot \left[C_2^2 \cdot (R_1 \cdot R_3)\right]\right]} \cdot \left(-R_1 \cdot R_3 \cdot C_2 - 2 \cdot R_2 \cdot R_3 \cdot C_2 - R_2 \cdot C_2 \cdot R_1 + C_2 \cdot \sqrt{R_1^2 \cdot R_3^2 - 2 \cdot R_1^2 \cdot R_3 \cdot R_2 + 4 \cdot R_2^2 \cdot R_3^2 + R_2^2 \cdot R_1^2}\right)$$

$$b := \frac{1}{\left[2 \cdot R_2 \cdot \left[C_2^2 \cdot (R_1 \cdot R_3)\right]\right]} \cdot \left(-R_1 \cdot R_3 \cdot C_2 - 2 \cdot R_2 \cdot R_3 \cdot C_2 - R_2 \cdot C_2 \cdot R_1 - C_2 \cdot \sqrt{R_1^2 \cdot R_3^2 - 2 \cdot R_1^2 \cdot R_3 \cdot R_2 + 4 \cdot R_2^2 \cdot R_3^2 + R_2^2 \cdot R_1^2}\right)$$

t := 0, 0.00001 .. 0.1

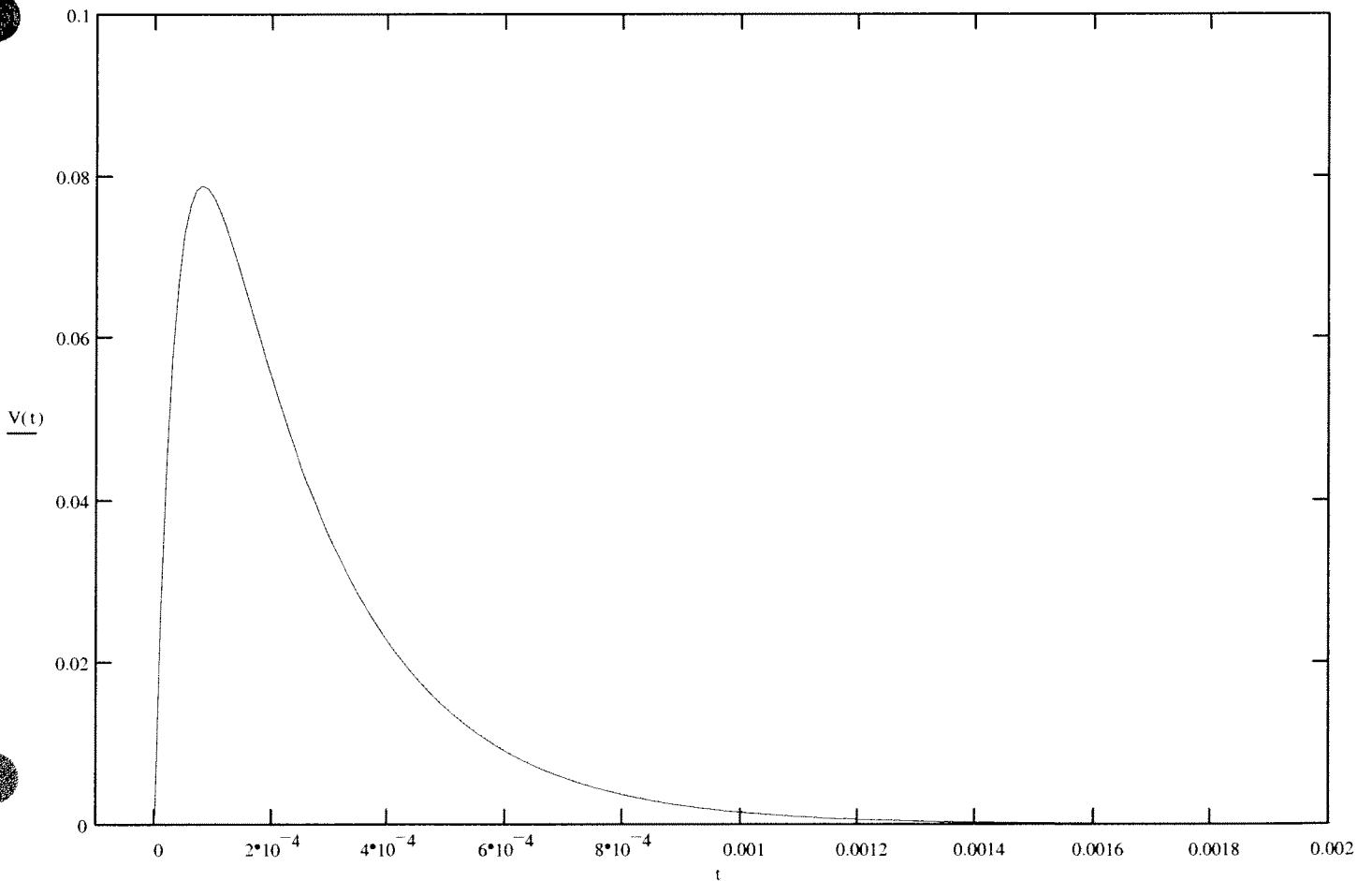
$$V(t) := V_s \cdot N \cdot R_3 \cdot R_2 \cdot C_2 \cdot \frac{e^{-a \cdot t} - e^{-b \cdot t}}{b - a} \cdot \Phi(t)$$



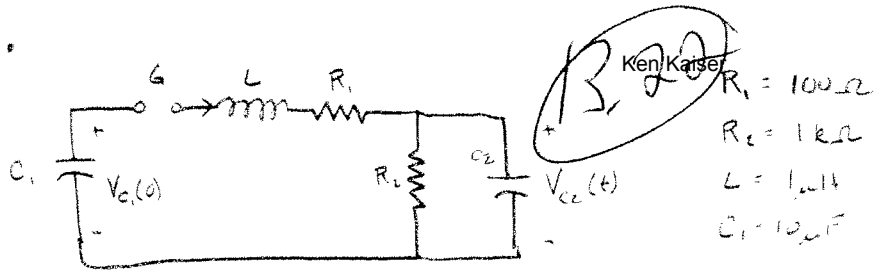

Ken Kaiser  
 $R_1 = 100 \Omega$   
 $R_2 = 1 k\Omega$   
 $L = 1 \mu H$   
 $C_1 = 10 \mu F$

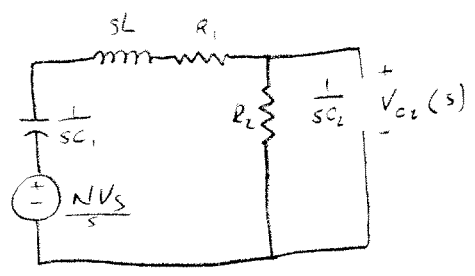$C_2 = 1 \mu F$   
 $V_{c1}(0) = 30 \text{ V}$



$$V_{c2}(s) = \frac{N U_s}{s} \cdot \left( \frac{R_2 \parallel \frac{1}{sC_2}}{R_2 \parallel \frac{1}{sC_2} + \frac{1}{sC_1} + sL + R_1} \right)$$

$$V_{c2}(s) = \frac{N U_s}{s} \cdot \frac{\frac{R_2}{1 + sR_2C_2}}{\frac{R_2}{1 + sR_2C_2} + R_1 + \frac{1}{sC_1} + sL}$$

$$V_{c2}(s) = \frac{C_1 R_2 N U_s}{(R_2 s C_1 + R_1 s C_1 + R_1 s^2 C_1 C_2 R_2 + 1 + s R_2 C_2 + s^2 L C_1 + s^3 L C_1 C_2 R_2)}$$

$$V_{C_2}(s) = \frac{NV_s}{s} \cdot \frac{\frac{R_2}{1+sR_2C_2}}{\frac{R_2}{1+sR_2C_2} + R_1 + \frac{1}{sC_1} + sL}$$

$$= \frac{NV_s}{s} \cdot \frac{R_2}{R_2 + R_1(1+sR_2C_2) + \frac{1}{sC_1}(1+sR_2C_2) + sL(1+sR_2C_2)}$$

$$= \frac{NV_s R_2}{sR_2 + sR_1(1+sR_2C_2) + \frac{1}{C_1}(1+sR_2C_2) + s^2L(1+sR_2C_2)}$$

$$= \frac{C_1 NV_s R_2}{C_1 sR_2 + C_1 sR_1(1+sR_2C_2) + 1 + sR_2C_2 + C_1 s^2L(1+sR_2C_2)}$$

$$= \frac{C_1 NV_s R_2}{sC_1 R_2 + sC_1 R_1 + s^2 C_1 C_2 R_1 R_2 + 1 + sR_2 C_2 + s^2 C_1 L + s^3 C_1 C_2 L R_2}$$

$$= \frac{C_1 NV_s R_2}{s^3 C_1 C_2 L R_2 + s^2 (C_1 C_2 R_1 R_2 + C_1 L) + s (C_1 R_2 + C_1 R_1 + C_2 R_2) + 1}$$

$$= \frac{\frac{NV_s}{C_2 L}}{s^3 + s^2 \left( \frac{C_1 C_2 R_1 R_2 + C_1 L}{C_1 C_2 L R_2} \right) + s \left( \frac{C_1 R_2 + C_1 R_1 + C_2 R_2}{C_1 C_2 L R_2} \right) + \frac{1}{C_1 C_2 L R_2}}$$

THIS IS THE EQUATION I USED.

FROM THE TABLE

$$\left[ \frac{(c-b)e^{-at} + (a-c)e^{-bt} + (b-a)e^{-ct}}{(b-a)(c-b)(a-c)} \right] u(t) \Leftrightarrow \frac{1}{(s+a)(s+b)(s+c)}$$



Circuit II  
Problem 13-22

Solving for s using simple equation

$$A \cdot s^3 + B \cdot s^2 + C \cdot s + D = 0$$

Go to next page. (long solutions)

$$R_1 := 100 \quad C_1 := 10 \cdot 10^{-6}$$

$$R_2 := 1 \cdot 10^3 \quad C_2 := 1 \cdot 10^{-6}$$

$$L := 1 \cdot 10^{-6}$$

Since Mathcad will not solve the following equation directly, use the symbolic solutions for s based on the simple equation, and plug in A,B,C,D.

$$s^3 + s^2 \cdot \frac{C_1 \cdot C_2 \cdot R_1 \cdot R_2 + C_1 \cdot L}{C_1 \cdot C_2 \cdot L \cdot R_2} + s \cdot \left( \frac{C_1 \cdot R_2 + C_1 \cdot R_1 + C_2 \cdot R_2}{C_1 \cdot C_2 \cdot L \cdot R_2} \right) + \frac{1}{C_1 \cdot C_2 \cdot L \cdot R_2} = 0$$

$$A := 1$$

$$A=1$$

$$B := \frac{C_1 \cdot C_2 \cdot R_1 \cdot R_2 + C_1 \cdot L}{C_1 \cdot C_2 \cdot L \cdot R_2}$$

$$B = \frac{C_1 \cdot C_2 \cdot R_1 \cdot R_2 + C_1 \cdot L}{C_1 \cdot C_2 \cdot L \cdot R_2} = 1 \cdot 10^8$$

$$C := \frac{C_1 \cdot R_2 + C_1 \cdot R_1 + C_2 \cdot R_2}{C_1 \cdot C_2 \cdot L \cdot R_2}$$

$$C = \frac{C_1 \cdot R_2 + C_1 \cdot R_1 + C_2 \cdot R_2}{C_1 \cdot C_2 \cdot L \cdot R_2} = 1.2 \cdot 10^{12}$$

$$D := \frac{1}{C_1 \cdot C_2 \cdot L \cdot R_2}$$

$$D = \frac{1}{C_1 \cdot C_2 \cdot L \cdot R_2} = 1 \cdot 10^{14}$$

Now, plug A,B,C,D into equation and solve for s

$$s^3 + 1 \cdot 10^8 \cdot s^2 + 1.2 \cdot 10^{12} \cdot s + 1 \cdot 10^{14} = 0$$

$$\begin{pmatrix} -83.920216400883 \\ -99987998.569657897723 \\ -11917.510125701393 \end{pmatrix}$$

$$a := 83.920216400883$$

$$b := 99987998.569657897723$$

$$c := 11917.510125701393$$

$$A \cdot s^3 + B \cdot s^2 + C \cdot s + D = 0$$

$$\left( \frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A} \right)$$

$$\frac{-1}{2} \left( \frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3} \cdot \frac{\sqrt{3}}{A^2} \right)^{\frac{1}{3}} + \frac{1}{2} \dots$$

$$\left( \frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A} \right)$$

$$\frac{-1}{2} \left( \frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3} \cdot \frac{\sqrt{3}}{A^2} \right)^{\frac{1}{3}} + \frac{1}{2} \dots$$

$$\left( \frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A} \right)$$

$$\begin{aligned}
 & \left( \frac{1}{3} \right) \left( A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \frac{\sqrt{3}}{A^2} \right) \left( \frac{1}{3} \right) \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \\
 & \left( \frac{1}{6} \cdot \frac{C}{A^2} \cdot B - \frac{1}{2} \cdot \frac{D}{A} - \frac{1}{27} \cdot \frac{B^3}{A^3} + \frac{1}{18} \cdot \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \frac{\sqrt{3}}{A^2}} \right) \\
 & \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \left( \frac{1}{3} \right) \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \\
 & \left( \frac{1}{6} \cdot \frac{C}{A^2} \cdot B - \frac{1}{2} \cdot \frac{D}{A} - \frac{1}{27} \cdot \frac{B^3}{A^3} + \frac{1}{18} \cdot \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \frac{\sqrt{3}}{A^2}} \right) \\
 & \left( \frac{1}{3} \right) \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \left( \frac{1}{3} \right) \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \\
 & \left( \frac{1}{6} \cdot \frac{C}{A^2} \cdot B - \frac{1}{2} \cdot \frac{D}{A} - \frac{1}{27} \cdot \frac{B^3}{A^3} + \frac{1}{18} \cdot \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \frac{\sqrt{3}}{A^2}} \right) \\
 & \left( \frac{1}{3} \right) \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \left( \frac{1}{3} \right) \left( \frac{1}{3} \cdot \frac{C}{A} - \frac{1}{9} \cdot \frac{B^2}{A^2} \right) \\
 & \left( \frac{1}{6} \cdot \frac{C}{A^2} \cdot B - \frac{1}{2} \cdot \frac{D}{A} - \frac{1}{27} \cdot \frac{B^3}{A^3} + \frac{1}{18} \cdot \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \frac{\sqrt{3}}{A^2}} \right)
 \end{aligned}$$

$$\left(\frac{1}{3}\right) \frac{1}{3} \frac{B}{A}$$

$$\left(\frac{1}{3}\right) \frac{2 + 4 \cdot D \cdot B^3 \cdot \sqrt{3}}{A^2} + \frac{\left(\frac{1}{3} \frac{C}{A} - \frac{1}{9} \frac{B^2}{A^2}\right)}{\left(\frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \sqrt{3}}\right) \frac{1}{A^2}} \left(\frac{1}{3}\right)$$

$$\left(\frac{1}{3}\right) \frac{2 + 4 \cdot D \cdot B^3 \cdot \sqrt{3}}{A^2} + \frac{\left(\frac{1}{3} \frac{C}{A} - \frac{1}{9} \frac{B^2}{A^2}\right)}{\left(\frac{1}{6} \frac{C}{A^2} \cdot B - \frac{1}{2} \frac{D}{A} - \frac{1}{27} \frac{B^3}{A^3} + \frac{1}{18} \sqrt{4 \cdot C^3 \cdot A - C^2 \cdot B^2 - 18 \cdot C \cdot B \cdot A \cdot D + 27 \cdot D^2 \cdot A^2 + 4 \cdot D \cdot B^3 \cdot \sqrt{3}}\right) \frac{1}{A^2}} \left(\frac{1}{3}\right)$$

$$R_1 := 100 \quad R_2 := 1 \cdot 10^3 \quad C_1 := 10 \cdot 10^{-6} \quad C_2 := 1 \cdot 10^{-6} \quad L := 1 \cdot 10^{-6} \quad NV_s := 30 \cdot 10^3$$

Values for a,b,c

$$s^3 + 1 \cdot 10^8 \cdot s^2 + 1.2 \cdot 10^{12} \cdot s + 1 \cdot 10^{14} = 0$$

$$\begin{pmatrix} -83.920216400883 \\ -99987998.569657897723 \\ -11917.510125701393 \end{pmatrix}$$

$$a := 83.920216400883$$

$$\frac{1}{a} = 0.012$$

$$b := 99987998.569657897723$$

$$\frac{1}{b} = 1 \cdot 10^{-8}$$

$$c := 11917.510125701393$$

$$\frac{1}{c} = 8.391 \cdot 10^{-5}$$

$$t := 0, \frac{1}{100} \cdot \max \begin{pmatrix} \frac{1}{a} \\ \frac{1}{b} \\ \frac{1}{c} \end{pmatrix} \dots 4 \cdot \max \begin{pmatrix} \frac{1}{a} \\ \frac{1}{b} \\ \frac{1}{c} \end{pmatrix}$$

$$V_c(t) := \frac{-NV_s}{C_2 \cdot L} \left[ \frac{(c-b) \cdot e^{-at} + (a-c) \cdot e^{-bt} + (b-a) \cdot e^{-ct}}{(b-a) \cdot (c-b) \cdot (a-c)} \right] \cdot \Phi(t)$$

Circuits II  
Problem 13-22

