

Proof of general form, equation 11

(4)

$$Z_{probe} = \frac{R \frac{1}{j\omega C_p}}{R + \frac{1}{j\omega C_p}} + \overset{\text{ignored}}{j\omega L_C} + \frac{Z_L \frac{1}{j\omega C_L}}{Z_L + \frac{1}{j\omega C_L}}$$

$$= \frac{R}{Rj\omega C_p + 1} + \overset{\text{ignored}}{j\omega L_C} + \frac{Z_L}{Z_L j\omega C_L + 1}$$

let  $Z_L = \frac{R_L \frac{1}{j\omega C_L}}{R_L + \frac{1}{j\omega C_L}}$

$$= \frac{R_L}{R_L j\omega C_L + 1}$$

Sub  $Z_L$ ,

$$\frac{R}{j\omega C_p R + 1} + \frac{\frac{R_L}{j\omega R_L C_L + 1}}{\frac{R}{j\omega R_L C_L + 1} + 1} = \frac{R_L}{R_L j\omega C_L + 1}$$

$$= \frac{R}{j\omega C_p R + 1} + \frac{R_L}{R_L j\omega C_L + j\omega R_L C_L + 1} = \frac{R(R_L j\omega C_L + j\omega R_L C_L + 1) + R_L(j\omega C_p R + 1)}{(R_L j\omega C_L + j\omega R_L C_L + 1)(j\omega C_p R + 1)}$$

$$= \frac{R(R_L j\omega C_L + 1) + R_L(j\omega C_p R + 1)}{(j\omega R_L C_L + 1)(j\omega C_p R + 1)} = \frac{(R+R_L) \left[ 1 + \frac{j\omega}{\left( \frac{R+R_L}{R R_L (C_L + C_p)} \right)} \right]}{\left( 1 + \frac{j\omega}{\frac{1}{R_L C_L}} \right) \left( 1 + \frac{j\omega}{\frac{1}{R C_p}} \right)}$$

(6) General form eq 15

$$\frac{R_x \frac{1}{j\omega C_x}}{R_x + \frac{1}{j\omega C_x}} = \frac{R_x}{j\omega C_x R_x + 1} = \frac{R_x}{j\omega C_x R_x + 1}$$

$$\frac{R_x \frac{1}{j\omega C_x}}{R_x + \frac{1}{j\omega C_x}} + \frac{R_p \frac{1}{j\omega C_p}}{R_p + \frac{1}{j\omega C_p}} = \frac{R_x}{j\omega C_x R_x + 1} + \frac{R_p}{j\omega C_p R_p + 1} = \frac{R_x(j\omega C_p R_p + 1) + R_p(j\omega C_x R_x + 1)}{(j\omega C_x R_x + 1)(j\omega C_p R_p + 1)}$$

$$= \frac{R_x(j\omega R_p C_p + 1)}{R_x(j\omega R_p C_p + 1) + R_p(j\omega C_x R_x + 1)} = \frac{R_x \left( 1 + \frac{j\omega}{\frac{1}{R_p C_p}} \right)}{R_x + R_p \left( 1 + \frac{j\omega}{\frac{1}{R_x C_x}} \right)}$$

pg 320

⑦

$$Z_{probe} = \frac{R}{1 + j\omega RC_p} + 50 = \frac{R + 50 (1 + j\omega RC_p)}{1 + j\omega RC_p} = \frac{R + 50 + j\omega RC_p (R + 50)}{1 + j\omega RC_p}$$

$$= (R + 50) \left( 1 + \frac{j\omega RC_p (R + 50)}{R + 50} \right) \checkmark$$

$$1 + \frac{j\omega}{\frac{1}{RC_p}}$$

⑧

pg 321

$$f_{break} = \frac{1}{2\pi(450)(1pF)} = 354 \text{ MHz}$$

## Chapter 15 Equation 8 &amp; 9

$$j := \sqrt{-1}$$

$$R := 50$$

$$C := 1 \cdot 10^{-12}$$

$$z(w) := \frac{R}{1 + j \cdot w \cdot R \cdot C} + 50$$


$$z(10) = 100 - 2.5i \times 10^{-7} \quad (9)$$

$$z(10^{12}) = 50.02 - i \quad (10)$$


older problem

SECTION IV: PROBES

(10) PASSIVE HIGH Z PROBE:

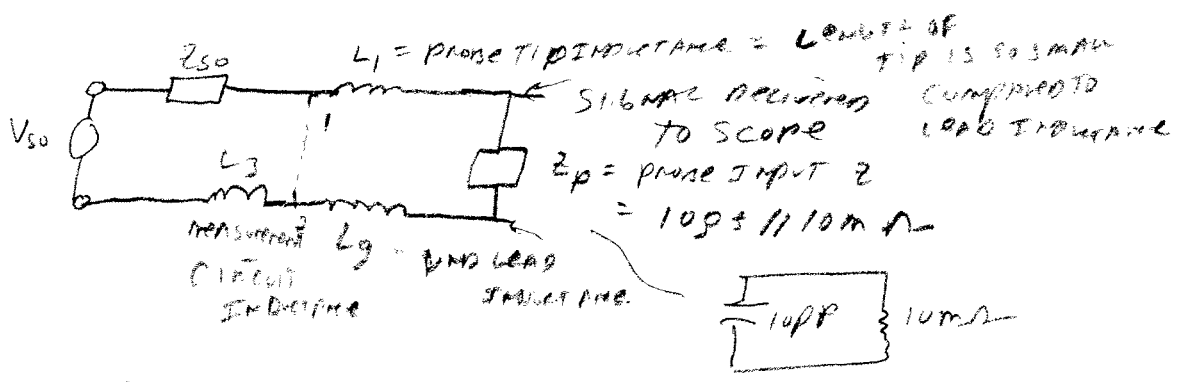

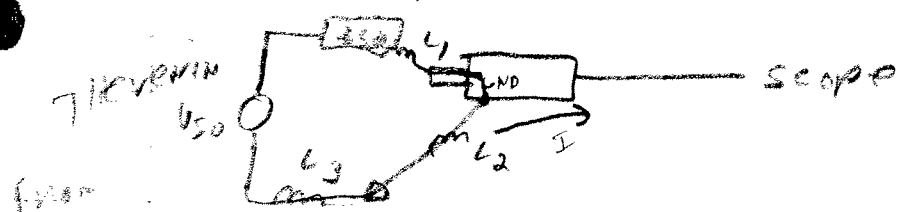15" - TOTAL LENGTH OF 3 INDUCTANCES  
 - PORTION OF INDUCTANCE DUE TO PROBE TIP IS VERY SMALL



from circuit

- L1 PROBE TIP ACCOUNTS TO 3" OF LEAD LENGTH
- L2 GND LEAD INDUCTANCE 6" OF LEAD LENGTH
- L3 INDUCTANCE DUE TO CONDUCTORS IN CIRCUIT TO BE MEASURED.

Lg IS LUMPED AS L1, L2, L3 - IN PROBLEM 15" <sup>3</sup>  
 SO THE TOTAL PATH LENGTH FORMING Lg IS 15"


$Lg = 15" \times 20nH/in = 300nH$

- \* VOLTAGE ACROSS Zp IS SIGNAL DELIVERED TO SCOPE FOR DISPLAY
- \* PROBE RESONANCE EXISTS DUE TO CAPACITANCE POTENTIAL
- \* Zso IS LOW (10Ω) WON'T PROVIDE MUCH DAMPING

WITH  $R_{series} = 300 \Omega$

③ Finally, Plot 3 shows the response DAMPED even further. However, this should be avoided because OVERDAMPING HAS OCCURRED AND VOLTAGE READING WILL BE VERY INACCURATE. THE ATTENUATION IS MAJOR, ACTUALLY LOSING VOLTAGE AT LOW FREQUENCIES AS WELL

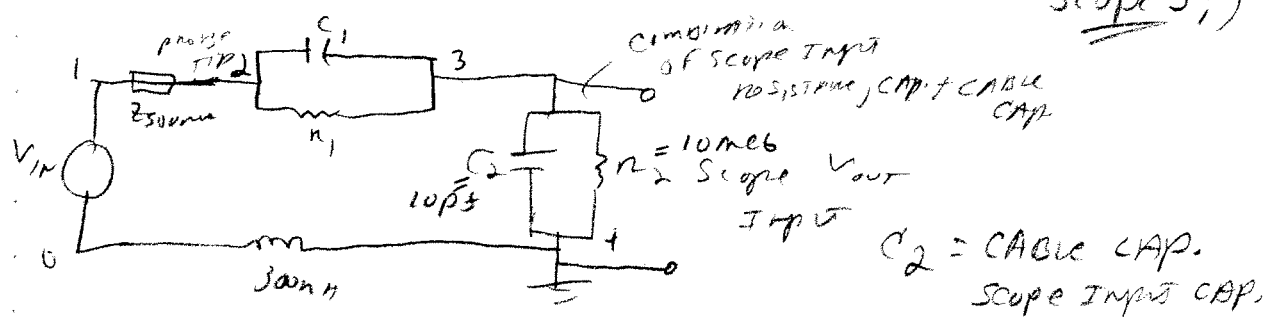\* TO COMPENSATE PROBE, MOST PROBES, HOWEVER USE AN RC COMBINATION TO OBTAIN THE 10:1 VOLTAGE OUTPUT ACROSS THE ENTIRE PROBE'S BANDWIDTH; (SO PROBE CAN BE USED IN DIFFERENT SCOPES!)



$$\frac{V_{out}}{V_{in}} = \left( \frac{R_2}{R_2 + R_1} \left[ \frac{1 + s \cdot C_2 \cdot R_2}{1 + s \cdot C_1 \cdot R_1} \right] \right)^{1/2}$$

ROOT

$$\tau_2 = R_2 C_2 = 0.1 \text{ msec}$$

$$\tau_1 = R_1 C_1 =$$

IF  $R_2 C_2 = R_1 C_1$

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_2 + R_1} - \text{frequency independent response}$$

- proper compensation


~~SEE DISCREPANCY~~

\* IF DIFFERENT SCOPE BEING USED, DIFFERENT INPUT  $Z$ , THEN YOU WOULD HAVE TO ADJUST RC NETWORK TO OBTAIN TIME CONSTANT  $\tau_1 = \tau_2$

SECTION 14: PROBES - PROBLEM 10

```

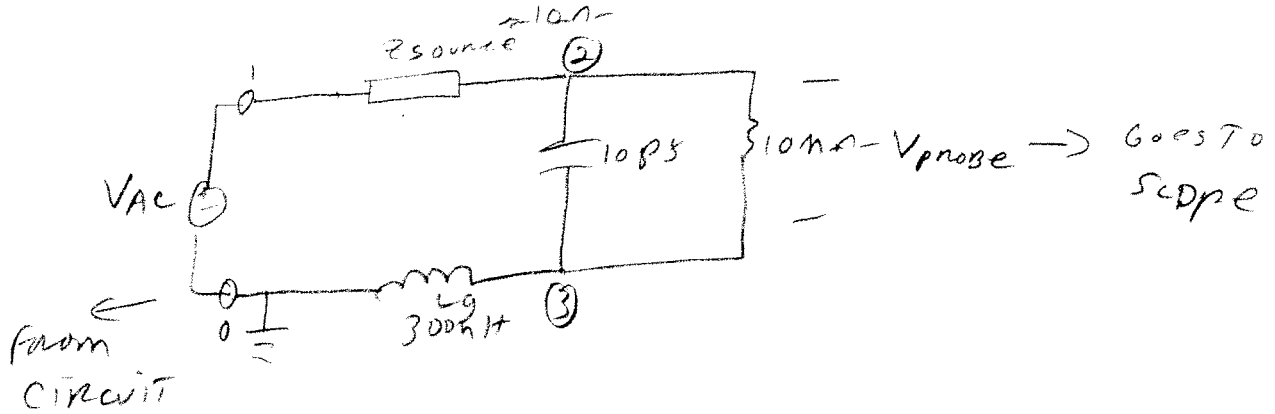*
* DISPLAY OF VOLTAGE RESPONSE ENTERING SCOPE
VIN 1 0 10 AC 1
F 1 2 10
C 3 10P
LG 3 0 300N
RL 2 3 10MEG
*SCOPE INPUT Z IS PARALLEL COMBO OF C1 AND RL
.AC DEC 10 0.1MEG 10G
.PLOT AC VDB(2,3)
.WIDTH OUT=80
.END
    
```




$$\frac{V_{out}}{V_{in}} = \frac{V_{probe}}{V_{AC}} \text{ in dB}$$

10:1 HIGH Z PROBE OUTPUT VSCOPE/VIN

Date: Time run: 12/08/94 14:43:44

Temperature: 77.0

Plot 1

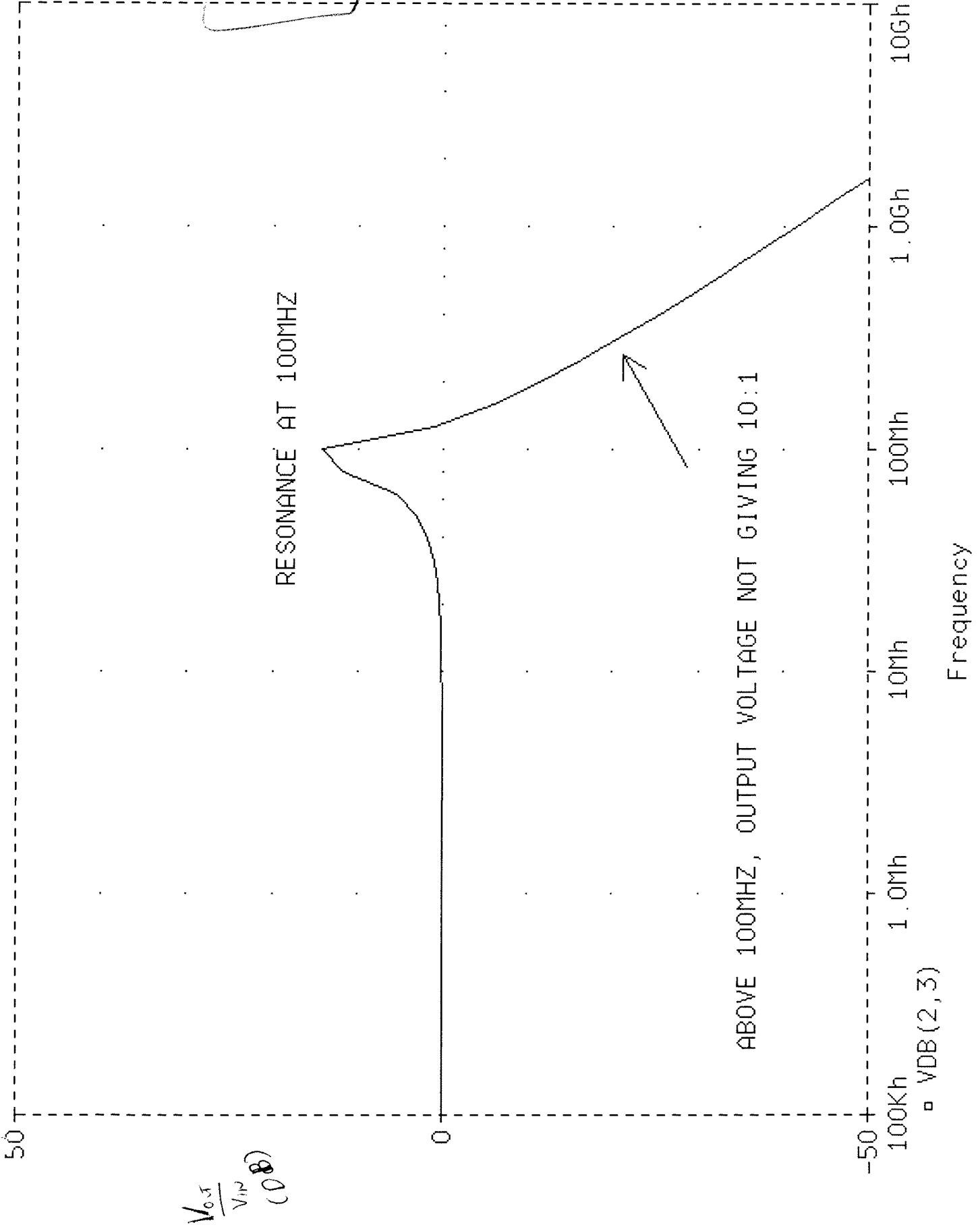

SECTION 14: PROBES - PROBLEM 10

\* [REDACTED]

\*DISPLAY OF VOLTAGE RESPONSE ENTERING SCOPE

VIN 1 0 10 AC 1

R 1 2 10

R 3 100

\*RD IS ADDED SERIES RESISTANCE TO DAMPEN RESPONSE - DECREASE Q

C1 3 4 10P

LG 4 0 300N

RL 3 4 10MEG

\*SCOPE INPUT Z IS PARALLEL COMBO OF C1 AND RL

.AC DEC 10 0.1MEG 10G

.PLOT AC VDB(2,3)

.WIDTH OUT=80

.END




10:1 HIGH Z PROBE - ADDED 100OHM SERIES RESISTANCE

Date/Time run: 12/08/94 14:53:27

Temperature: 27.0

Ken Kaiser

Plot 2

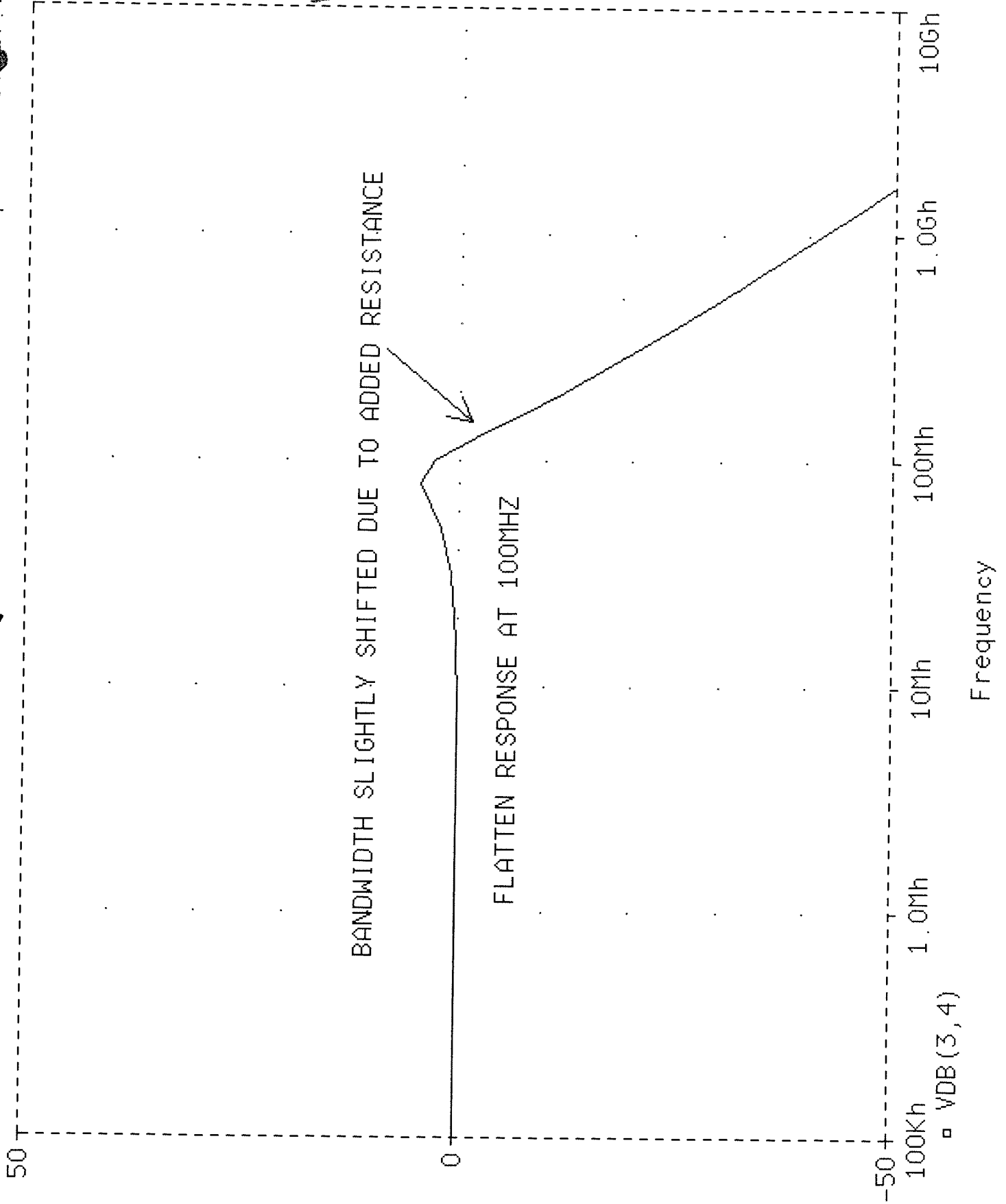

□ VDB (3,4)

SECTION 14: PROBES - PROBLEM 10


```
*  
*DISPLAY OF VOLTAGE RESPONSE ENTERING SCOPE  
VIN 1 0 10 AC 1  
R1 1 2 10  
R2 3 300  
*RD IS ADDED SERIES RESISTANCE TO DAMPEN RESPONSE - DECREASE Q  
*HOWEVER, THIS COMBINATION CAUSES OVERDAMPING - BANDWIDTH LOST  
C1 3 4 10P  
LG 4 0 300N  
RL 3 4 10MEG  
*SCOPE INPUT Z IS PARALLEL COMBO OF C1 AND RL  
.AC DEC 10 0.1MEG 10G  
.PLOT AC VDB(2,3)  
.WIDTH OUT=80  
.END
```

Date: 12/08/94 15:01:26  
Time run: 10:1 HIGH Z PROBE - ADDED 100OHM SERIES RESISTANCE

Temperature: 77.0

Ken Kaiser

Plot 3

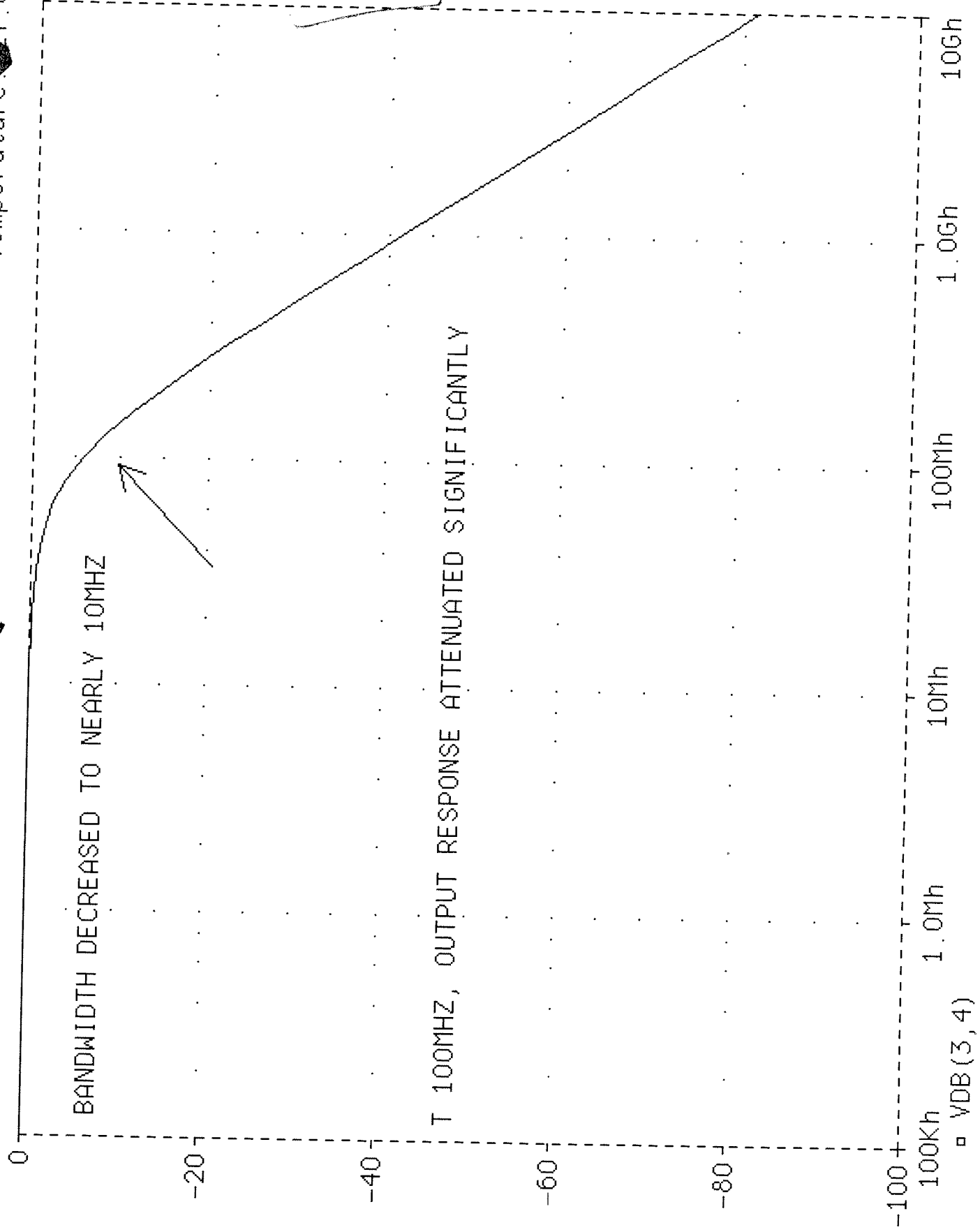

BANDWIDTH DECREASED TO NEARLY 10MHZ


T 100MHZ, OUTPUT RESPONSE ATTENUATED SIGNIFICANTLY

VDB(3,4)

Frequency

old problem addin's Ken Kaiser extra in lead!

SECTION 14 PROBLEM 10

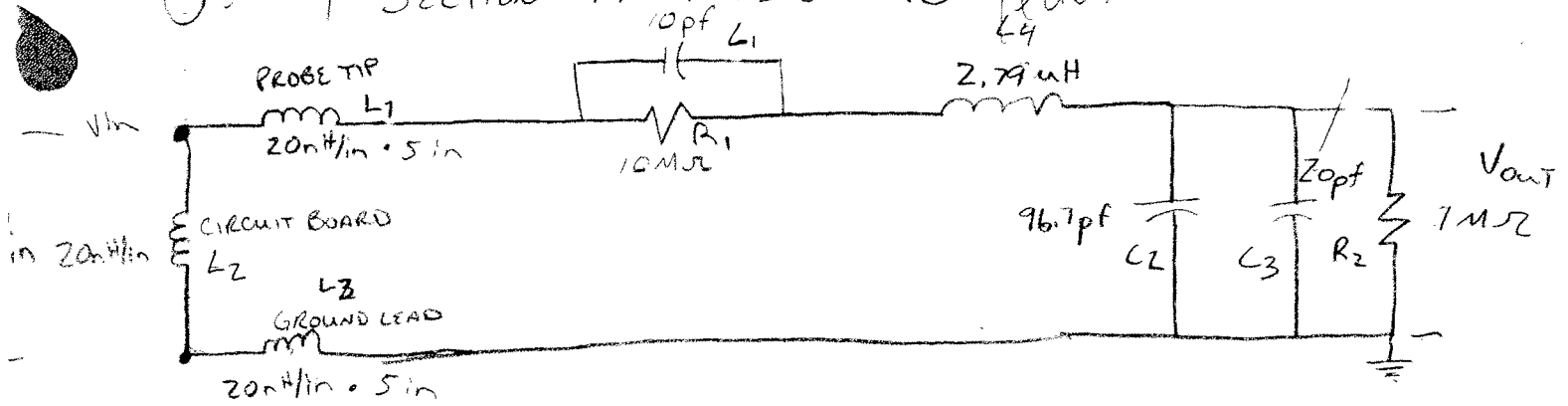

1 meter of cable is electrically small for frequencies less than:

$$f = \frac{v}{\lambda} = \frac{1}{\lambda} \text{ meter}$$

characteristic impedance =  $170 \Omega$      $Z_0 = \sqrt{L/C}$      $L = C Z_0^2$  }  
 CAPACITANCE OF LINE =  $96.7 \text{ pF/m}$

$L = 2.79 \text{ μH/m}$      $v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{6.510^{-7}}} \text{ m/sec}$

$f = \frac{60 \times 10^6}{1} = 60 \text{ MHz}$

\* ELECTRICALLY SMALL FOR FREQUENCIES LESS THAN 6 MHz

~~$\lambda = \frac{1}{\sqrt{LC}}$~~      $\lambda = \frac{1}{\sqrt{LC}}$

$$\frac{V_{out}}{V_{in}} = \frac{1 \text{ M}\Omega \parallel \frac{1}{j\omega C_3} \parallel \frac{1}{j\omega C_2}}{j\omega L_2 + 10 \text{ M}\Omega \parallel \frac{1}{j\omega C_1} + j\omega L_4 + 1 \text{ M}\Omega \parallel \frac{1}{j\omega C_3} \parallel \frac{1}{j\omega C_2}}$$

ON SCOPE SIDE USE NETWORK THAT CONTAINS TIME CONSTANT ADJUSTMENTS WITH INDUCTIVE PEAKING.

$$R1 := 10 \cdot 10^6$$

$$C1 := 10 \cdot 10^{-12}$$

$$L1 := 100 \cdot 10^{-9}$$

$$j := \sqrt{-1}$$

$$R2 := 1 \cdot 10^6$$

$$C2 := 96.7 \cdot 10^{-12}$$

$$L2 := 100 \cdot 10^{-9}$$

$$x := 10, 10.1 \dots 80$$

$$C3 := 20 \cdot 10^{-12}$$


$$L3 := 2.79 \cdot 10^{-6}$$

$$\omega(x) := \left[ (x + 1) - 10 \cdot \text{floor} \left( \frac{x}{10} \right) \right] \cdot 10^{\text{floor} \left( \frac{x}{10} \right)}$$

$$Z_{\text{par}}(\omega) := \frac{1}{\left( \frac{1}{R2} \right) + j \cdot \omega(x) \cdot C3 + j \cdot \omega(x) \cdot C2}$$

$$Z_{\text{probe}}(\omega) := \frac{R1 \cdot \frac{1}{j \cdot \omega(x) \cdot C1}}{R1 + \frac{1}{j \cdot \omega(x) \cdot C1}}$$
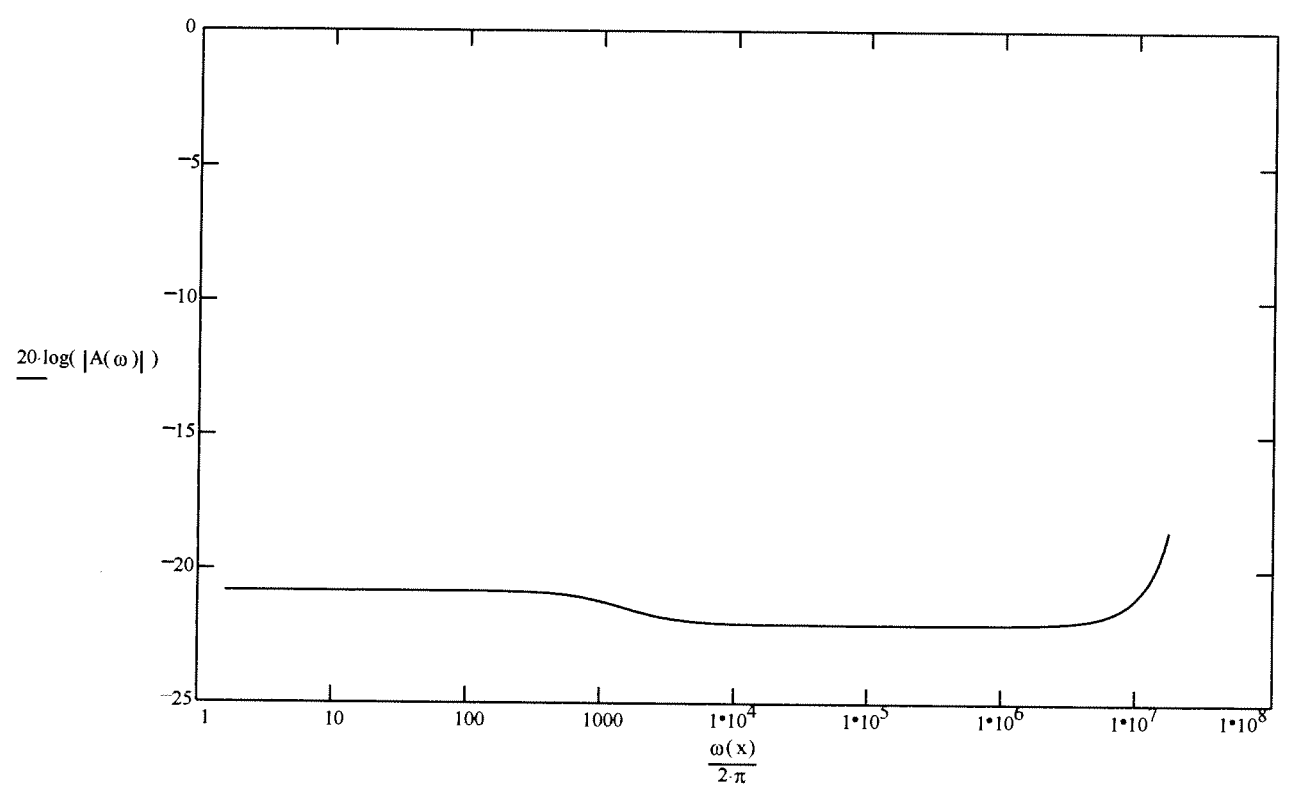
$$A(\omega) = \frac{Z_{\text{par}}(\omega)}{j \cdot \omega(x) \cdot L1 + Z_{\text{probe}}(\omega) + j \cdot \omega(x) \cdot L3 + Z_{\text{par}}(\omega) + j \cdot \omega(x) \cdot L2}$$



$$R1 := 10 \cdot 10^6$$

$$C1 := 10 \cdot 10^{-12}$$

$$L1 := 100 \cdot 10^{-9}$$

$$j := \sqrt{-1}$$

$$R2 := 1 \cdot 10^6$$

$$C2 := 96.7 \cdot 10^{-12}$$

$$L2 := 100 \cdot 10^{-9}$$

$$x := 20, 20.1 \dots 80$$

$$C3 := 20 \cdot 10^{-12}$$


$$L3 := 2.79 \cdot 10^{-6}$$

$$Lcomp := 0.256 \cdot 10^{-6} \quad \omega(x) := \left[ (x + 1) - 10 \cdot \text{floor} \left( \frac{x}{10} \right) \right] \cdot 10^{\text{floor} \left( \frac{x}{10} \right)}$$

$$Zpar(\omega) := \frac{1}{\left( \frac{1}{R2} \right) + j \cdot \omega(x) \cdot C3 + j \cdot \omega(x) \cdot C2} + j \cdot \omega(x) \cdot Lcomp$$

$$Zprobe(\omega) := \frac{R1 \cdot \frac{1}{j \cdot \omega(x) \cdot C1}}{R1 + \frac{1}{j \cdot \omega(x) \cdot C1}}$$
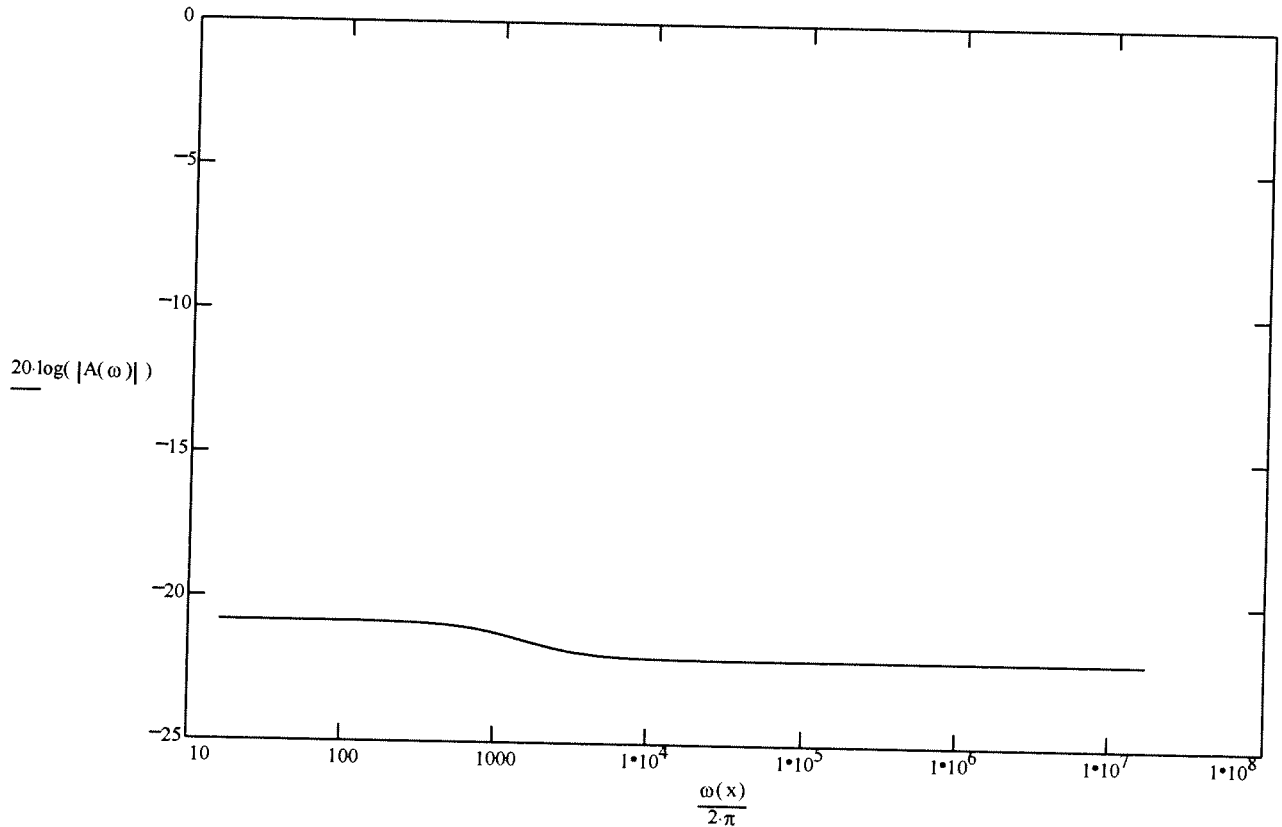
$$A(\omega) := \frac{Zpar(\omega)}{j \cdot \omega(x) \cdot L1 + Zprobe(\omega) + j \cdot \omega(x) \cdot L3 + Zpar(\omega) + j \cdot \omega(x) \cdot L2}$$



$$R1 := 10 \cdot 10^6$$

$$C1 := 10 \cdot 10^{-12}$$

$$L1 := 100 \cdot 10^{-9} \quad \text{Ken Kaiser}$$

$$j := \sqrt{-1}$$

$$R2 := 1 \cdot 10^6$$

$$C2 := 96.7 \cdot 10^{-12}$$

$$L2 := 100 \cdot 10^{-9}$$

$$x := 20, 20.1 \dots 80$$

$$C3 := 3 \cdot 10^{-12}$$


$$L3 := 2.79 \cdot 10^{-6}$$

$$L_{\text{comp}} := 0.3 \cdot 10^{-6} \quad \omega(x) := \left[ (x+1) - 10 \cdot \text{floor}\left(\frac{x}{10}\right) \right] \cdot 10^{\text{floor}\left(\frac{x}{10}\right)}$$

$$Z_{\text{par}}(\omega) := \frac{1}{\left(\frac{1}{R2}\right) + j \cdot \omega(x) \cdot C3 + j \cdot \omega(x) \cdot C2} + j \cdot \omega(x) \cdot L_{\text{comp}}$$

$$Z_{\text{probe}}(\omega) := \frac{R1 \cdot \frac{1}{j \cdot \omega(x) \cdot C1}}{R1 + \frac{1}{j \cdot \omega(x) \cdot C1}}$$
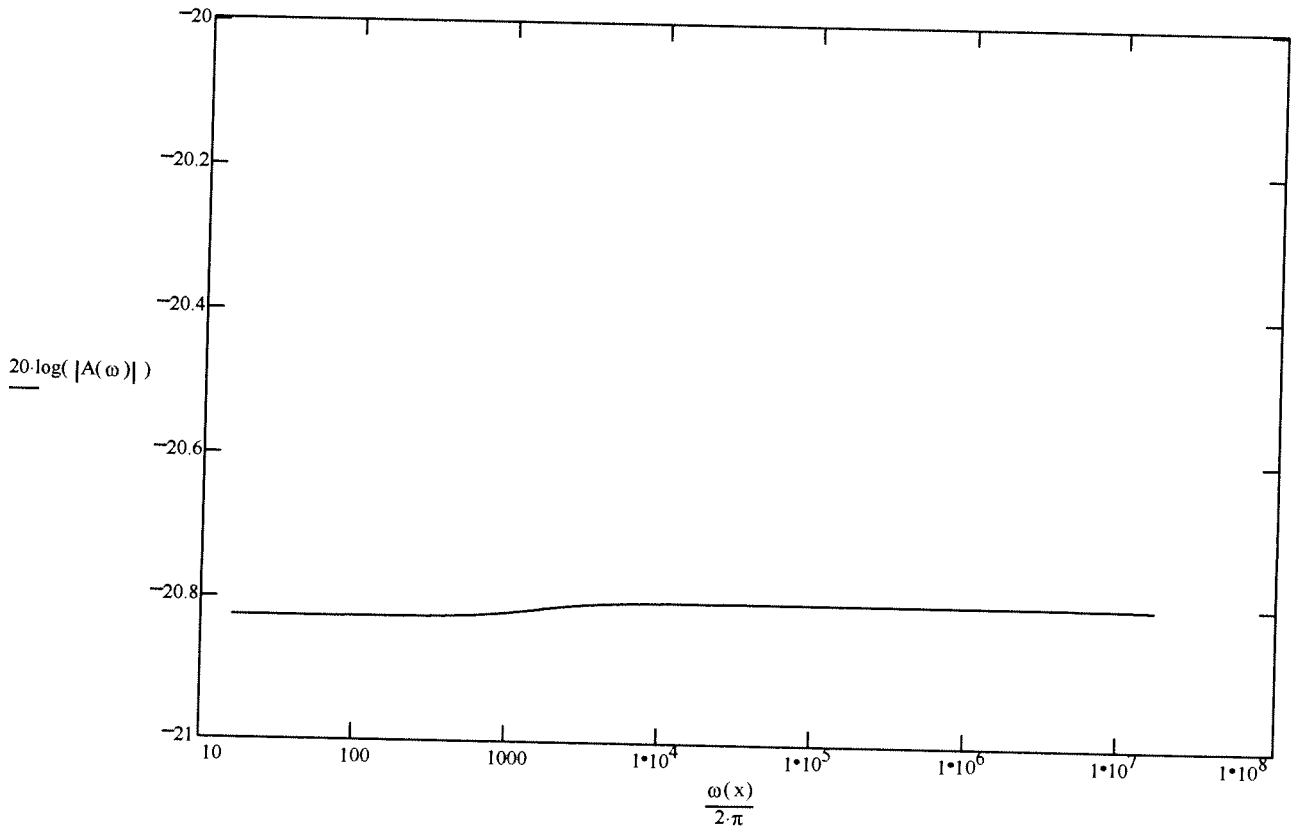
$$A(\omega) := \frac{Z_{\text{par}}(\omega)}{j \cdot \omega(x) \cdot L1 + Z_{\text{probe}}(\omega) + j \cdot \omega(x) \cdot L3 + Z_{\text{par}}(\omega) + j \cdot \omega(x) \cdot L2}$$




*old  
preher  
preher*

Section 14  
Problem # 9


$R_{50} := 50 \quad R_{250} := 250 \quad C_p := 10 \cdot 10^{-12} \quad j := \sqrt{-1} \quad L_p := 1 \cdot 10^{-9} \quad f := 1, 1.1, \dots, 110$
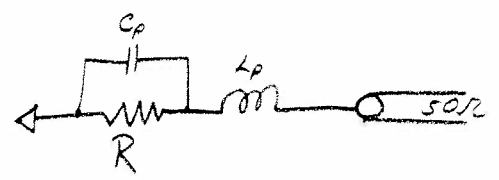
$$\omega(f) := 2 \cdot \pi \cdot \left( 1 + f - 10 \cdot \text{floor} \left( \frac{f}{10} \right) \right) \cdot 10^{\text{floor} \left( \frac{f}{10} \right)}$$



$$H_{1\_50}(\omega) := \frac{R_{50}}{R_{50} \cdot j \cdot \omega(f) \cdot C_p + 1 + L_p \cdot j \cdot \omega(f)}$$
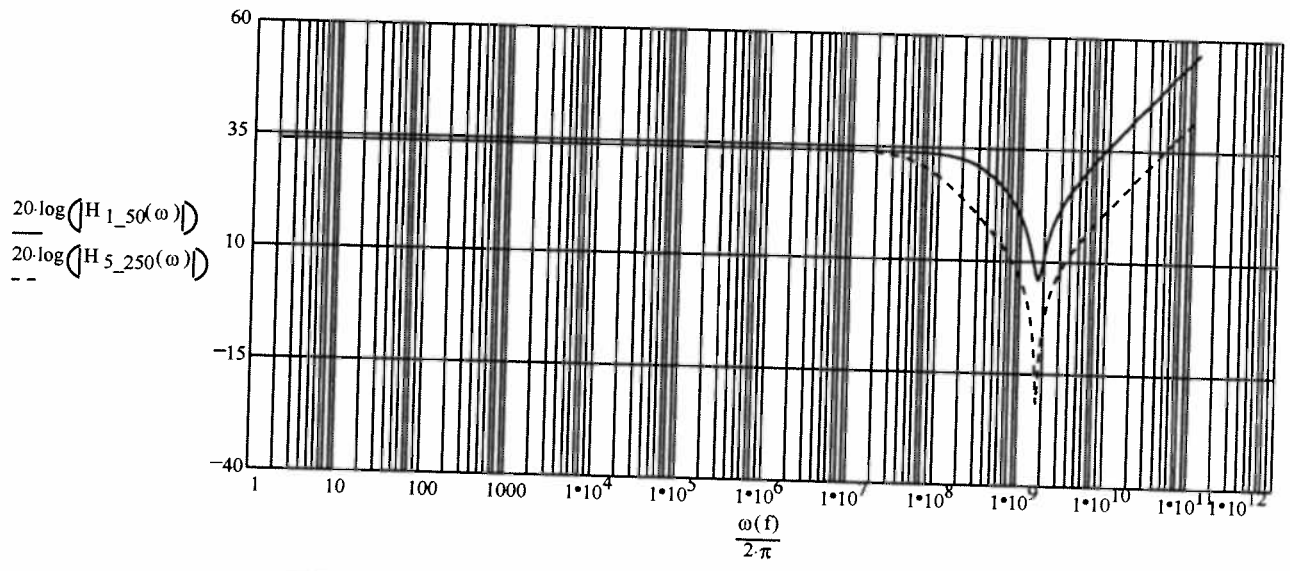
$$H_{5\_250}(\omega) := \frac{1}{5} \cdot \left( \frac{R_{250}}{R_{250} \cdot j \cdot \omega(f) \cdot C_p + 1 + L_p \cdot j \cdot \omega(f)} \right)$$



Putting the five resistors in parallel has no real affect on the frequency response of the system.

The magnitude of the impedance does decrease a little faster when the five resistors are put in parallel, but it is not a significant amount.