

(16) equation

Ken Kaiser

Given

$$j\omega \cdot L_s \cdot I_{ss} - j\omega \cdot M \cdot I_{cs} + R_s \cdot I_{ss} + V_{CMs} = 0 \quad \dots \dots \dots 1^{st} \text{ loop}$$

$$\text{Find}(j\omega \cdot M \cdot I_{cs}) \rightarrow j\omega \cdot L_s \cdot I_{ss} + R_s \cdot I_{ss} + V_{CMs} \quad \dots \dots \dots \text{solve for } j\omega M I_{cs}$$

Given

$$R_d \cdot I_{cs} + R_c \cdot I_{cs} + j\omega \cdot L_c \cdot I_{cs} + j\omega \cdot M \cdot I_{ss} + R_L \cdot I_{cs} - V_{CMs} = 0 \quad \dots \dots \dots 2^{nd} \text{ loop}$$

$$\text{Find}(R_L \cdot I_{cs}) \rightarrow R_d \cdot I_{cs} + R_c \cdot I_{cs} + j\omega \cdot L_c \cdot I_{cs} + j\omega \cdot M \cdot I_{ss} + V_{CMs} \quad \dots \dots \dots \text{solve for } R_L I_{cs}$$

$$-R_d \cdot I_{cs} - R_c \cdot I_{cs} - j\omega \cdot L_s \cdot I_{ss} + R_s \cdot I_{ss} + V_{CMs} - j\omega \cdot L_s \cdot I_{ss} + V_{CMs} \quad \dots \dots \dots \text{sub } j\omega M I_{cs} \text{ from } 1^{st} \text{ into}$$

$$-R_d \cdot I_{cs} - R_c \cdot I_{cs} - 2j\omega \cdot L_s \cdot I_{ss} + R_s \cdot I_{ss} + 2V_{CMs} \quad \dots \dots \dots 2^{nd} \text{ } \frac{1}{s} \text{ replace all } M \text{ w/ } k_c$$

← simplify w/ k_s

$$\frac{\frac{R_s \cdot R_L}{R_s \cdot (R_c + R_d + R_L)} \cdot V_{CMs}}{1 + \left[\frac{j\omega}{\frac{R_s \cdot (R_c + R_d + R_L)}{L_s \cdot (R_s + R_c + R_d + R_L)}} \right]}$$

Now I took equation #16 and simplified it.

$$R_s \cdot V_{CMs} \cdot \frac{R_L}{(R_s \cdot R_c + R_s \cdot R_d + R_s \cdot R_L + j\omega \cdot L_s \cdot R_s + j\omega \cdot L_s \cdot R_c + j\omega \cdot L_s \cdot R_d + j\omega \cdot L_s \cdot R_L)}$$

M = Ls = Lc / Req and M and Lc w/ Ls

Given

sqrt(-1) * w * Ls * Is - sqrt(-1) * w * Ls * Ic + Rs * Is + Vcm = 0

Rd * Ic + Rc * Ic + sqrt(-1) * w * Ls * Ic - sqrt(-1) * w * Ls * Is + RL * Ic - Vcm = 0

Ken Kaiser

Find(Ic, Is) -> [i * Rs * (-Rd * Ls * w - Rc * Ls * w - RL * Ls * w + i * Rs * Rd + i * Rs * Rc - Rs * w * Ls + i * Rs * RL) / (Rd + Rc + RL) ; -i * Vcm * (-Rd * Ls * w - Rc * Ls * w - RL * Ls * w + i * Rs * Rd + i * Rs * Rc - Rs * w * Ls + i * Rs * RL)] / Vcm

Vc = RL * Ic ; Vcm = (i * Rd * w * Ls + i * w * Ls * Rs + i * RL * w * Ls + Rd * Rs + i * Rc * w * Ls + Rc * Rs + RL * Rs) / Rs

Insert into eqn

1 + [(Rs * RL) / (Rs * (Rc + Rd + RL)) * Vcm] / [(Rs * (Rc + Rd + RL)) / (Ls * (Rs + Rc + Rd + RL))]

$$V_{cm} \frac{R_s}{(i \cdot R_d \cdot w \cdot L_s + i \cdot w \cdot L_s R_s + i \cdot R_L \cdot w \cdot L_s + R_d R_s + i \cdot R_e \cdot w \cdot L_s + R_e R_s + R_L R_s)} \cdot R_L$$

Σ Modified Expression

$$\left[\frac{R_s \cdot R_L}{R_s \cdot (R_c + R_d + R_L)} \cdot V_{cm} \right]$$

$$1 + \frac{\sqrt{-1 \cdot w}}{\left[\frac{R_s \cdot (R_c + R_d + R_L)}{L_s \cdot (R_s + R_c + R_d + R_L)} \right]}$$

Imaginary part

1 *let ch-1*

From Method, (page 1)

$$V_L = R_L I_c = \frac{R_L R_S \cdot V_{cm}}{(j R_d \omega L_S + j \omega L_S R_S + j R_L \omega L_S + R_d R_S + j R_c \omega L_S + R_c R_S + R_L R_S)}$$

$$= \frac{R_L R_S \cdot V_{cm}}{j [R_d \omega L_S + \omega L_S R_S + R_L \omega L_S + R_c \omega L_S] + \underbrace{R_d R_S + R_c R_S + R_L R_S}_{R_S (R_d + R_c + R_L)}}$$

$$= \frac{V_{cm} (R_L R_S)}{R_S (R_d + R_c + R_L) + j \omega L_S [R_d + R_S + R_L + R_c]}$$

$$= \frac{V_{cm} (R_L R_S)}{R_S (R_d + R_c + R_L) \left[1 + \frac{j \omega L_S [R_d + R_S + R_L + R_c]}{R_S (R_d + R_c + R_L)} \right]}$$

$$= \left(\frac{R_L R_S}{R_S (R_c + R_d + R_L)} \right) V_{cm}$$

$$1 + \frac{j \omega}{\left[\frac{R_S (R_c + R_d + R_L)}{L_S (R_d + R_S + R_L + R_c)} \right]}$$

✓ 2nd Check

$$\omega = 0$$

Ken Kaiser

$$V_L \approx \frac{\left[\frac{R_s R_L}{R_s (R_c + R_d + R_L)} \right] V_{cm}}{1 + \frac{j(0) \frac{R_s (R_c + R_d + R_L)}{L_s (R_s + R_c + R_d + R_L)}}{1}}$$

$$= \left[\frac{R_s R_L}{R_s (R_c + R_d + R_L)} \right] V_{cm} \quad \checkmark$$

$$\omega \gg 1$$

$$V_L \approx \frac{\left(\frac{R_s R_L}{R_s (R_c + R_d + R_L)} \right) V_{cm}}{\frac{j\omega \frac{R_s (R_c + R_d + R_L)}{L_s (R_s + R_c + R_d + R_L)}}{1}}$$

$$= \frac{R_s R_L \cdot V_{cm}}{j\omega (L_s (R_s + R_c + R_d + R_L))} \quad \checkmark$$

Given

$$-V_{D_s} + R_d \cdot I_{C_s} + R_c \cdot I_{C_s} + \sqrt{-1} \cdot w \cdot L \cdot I_{C_s} - \sqrt{-1} \cdot w \cdot L \cdot I_{S_s} + 0 + R_L \cdot I_{C_s} = 0$$

$$\sqrt{-1} \cdot w \cdot L \cdot I_{S_s} - \sqrt{-1} \cdot w \cdot L \cdot I_{C_s} + R_s \cdot I_{S_s} = 0$$

$$\text{Find}(I_{C_s}, I_{S_s}) \rightarrow \left[\begin{array}{l} \frac{V_{D_s}}{(-R_d \cdot w \cdot L + i \cdot R_d \cdot R_s - R_c \cdot w \cdot L + i \cdot R_c \cdot R_s - w \cdot L \cdot R_s - R_L \cdot w \cdot L + i \cdot R_L \cdot R_s)} \cdot (-w \cdot L + i \cdot R_s) \\ -V_{D_s} \cdot w \cdot \frac{L}{(-R_d \cdot w \cdot L + i \cdot R_d \cdot R_s - R_c \cdot w \cdot L + i \cdot R_c \cdot R_s - w \cdot L \cdot R_s - R_L \cdot w \cdot L + i \cdot R_L \cdot R_s)} \end{array} \right]$$

$$w := 3.54 \quad L := 4.56 \quad R_s := 0.45 \quad R_c := 8.94 \quad R_d := 2.67 \quad R_L := 7.98 \quad V_{D_s} := 0.45$$

$$-V_{D_s} \cdot w \cdot \frac{L}{(-R_d \cdot w \cdot L + i \cdot R_d \cdot R_s - R_c \cdot w \cdot L + i \cdot R_c \cdot R_s - w \cdot L \cdot R_s - R_L \cdot w \cdot L + i \cdot R_L \cdot R_s)} = 0.022 + 6.115i \times 10^{-4}$$

$$\frac{\sqrt{-1} \cdot \frac{w \cdot L}{R_s \cdot (R_d + R_c + R_L)} \cdot V_{D_s}}{1 + \sqrt{-1} \cdot \frac{w}{\frac{R_s \cdot (R_d + R_c + R_L)}{L \cdot (R_d + R_c + R_s + R_L)}}} = 0.022 + 6.115i \times 10^{-4}$$

$$I_{CS} (R_d + j\omega L + R_L) = V_{OS} + j\omega L I_{SS}$$

$$I_{CS} = \frac{V_{OS}}{R_s + R_d + R_L + j\omega L} + \frac{j\omega L I_{SS}}{R_s + R_d + R_L + j\omega L}$$

~~$$j\omega L I_{SS} = j\omega L$$~~

$$(j\omega L + R_s) I_{SS} = j\omega L \left[\frac{V_{OS}}{R_s + R_d + R_L + j\omega L} \right]$$

$$+ j\omega L \left[\frac{j\omega L I_{SS}}{R_s + R_d + R_L + j\omega L} \right]$$

$$(j\omega L + R_s) I_{SS} = \frac{V_{OS} j\omega L}{R_s + R_d + R_L + j\omega L} - \frac{\omega^2 L^2 I_{SS}}{R_s + R_d + R_L + j\omega L}$$

$$\left(j\omega L + R_s + \frac{\omega^2 L^2}{R_s + R_d + R_L + j\omega L} \right) I_{CS} = \frac{V_{OS} j\omega L}{R_s + R_d + R_L + j\omega L}$$

$$I_{SS} = \frac{V_{DS} j\omega L}{R_s R_d + R_c + j\omega L}$$

$$\frac{j\omega L + R_s + \frac{\omega^2 L^2}{R_s R_d + R_c + j\omega L}}$$

$$= \frac{V_{DS} j\omega L}{j\omega L R_c + j\omega L R_d + j\omega L R_c - \omega^2 L^2 + R_s R_d + R_s R_c + j\omega R_s L + \omega^2 L^2 + R_c R_s}$$

$$= \frac{V_{DS} j\omega L}{j\omega (L R_d + L R_s + L R_c) + R_s (R_d + R_c)}$$

$$= \frac{V_{DS} j\omega L}{R_s (R_d + R_c + R_c)}$$

$$\frac{j\omega}{R_s (R_d + R_c + R_c)} + 1$$

$$\frac{j\omega}{L (R_d + R_s + R_c + R_c)}$$

Section 22.10 Keeping Noise off the Shield

Loop equations:

Loop 1

$$V_{cm} + R_s \cdot I_s + (\sqrt{-1}) \cdot \omega \cdot L_s \cdot I_s - (\sqrt{-1}) \cdot \omega \cdot M \cdot I_c = 0$$

$$V_{cm} + R_s \cdot I_s + i \cdot \omega \cdot L_s \cdot I_s - i \cdot \omega \cdot M \cdot I_c = 0$$

Loop 2

$$R_d \cdot I_c + R_c \cdot I_c + (\sqrt{-1}) \cdot \omega \cdot L_c \cdot I_c - (\sqrt{-1}) \cdot \omega \cdot M \cdot I_s + V_L - V_{cm} = 0$$

$$R_d \cdot I_c + R_c \cdot I_c + i \cdot \omega \cdot L_c \cdot I_c - i \cdot \omega \cdot M \cdot I_s + V_L - V_{cm} = 0$$

 $I_c = 0$, so this equation simplifies to:

$$-(\sqrt{-1}) \cdot \omega \cdot M \cdot I_s + V_L - V_{cm} = 0$$

 V_L is found from these two equations:

$$V_{cm} + R_s \cdot I_s + i \cdot \omega \cdot L_s \cdot I_s = 0$$

$$-R_s \cdot I_s - i \cdot \omega \cdot L_s \cdot I_s$$

$$-(\sqrt{-1}) \cdot \omega \cdot M \cdot I_s + V_L - V_{cm} = 0$$

$$i \cdot \omega \cdot M \cdot I_s + V_{cm}$$

$$i \cdot \omega \cdot M \cdot I_s + (-R_s \cdot I_s - i \cdot \omega \cdot L_s \cdot I_s)$$

$$-I_s \cdot (-i \cdot \omega \cdot M + R_s + i \cdot \omega \cdot L_s)$$

$$M = L_s$$

$$-I_s \cdot (-i \cdot \omega \cdot L_s + R_s + i \cdot \omega \cdot L_s)$$

$$V_L =$$

$$-R_s \cdot I_s$$

For a load resistance of R_L , the loop equations are:

$$V_{cm} + R_s \cdot I_s + i \cdot \omega \cdot L_s \cdot I_s - i \cdot \omega \cdot M \cdot I_c = 0$$

$$R_d \cdot I_c + R_c \cdot I_c + i \cdot \omega \cdot L_c \cdot I_c - i \cdot \omega \cdot M \cdot I_s + V_L - V_{cm} = 0$$

$$R_d \cdot I_c + R_c \cdot I_c + i \cdot \omega \cdot L_c \cdot I_c - i \cdot \omega \cdot M \cdot I_s - V_{cm} + R_L \cdot I_c = 0$$

if $M = L_c = L_s$

$$V_{cm} + R_s \cdot I_s + i \cdot \omega \cdot L_s \cdot I_s - i \cdot \omega \cdot L_s \cdot I_c = 0$$

$$I_s =$$

$$\frac{-(V_{cm} - i \cdot \omega \cdot L_s \cdot I_c)}{(R_s + i \cdot \omega \cdot L_s)}$$

$$R_d \cdot I_c + R_c \cdot I_c + i \cdot \omega \cdot L_s \cdot I_c - i \cdot \omega \cdot L_s \cdot \left[\frac{-(V_{cm} - i \cdot \omega \cdot L_s \cdot I_c)}{(R_s + i \cdot \omega \cdot L_s)} \right] - V_{cm} + R_L \cdot I_c = 0$$

$$I_c =$$

$$\frac{- \left[\omega^2 \cdot \frac{L_s^2}{(R_s^2 + \omega^2 \cdot L_s^2)} \cdot V_{cm} - V_{cm} + i \cdot \omega \cdot L_s \cdot \frac{R_s}{(R_s^2 + \omega^2 \cdot L_s^2)} \cdot V_{cm} \right]}{\left[R_d + R_c + \omega^2 \cdot L_s^2 \cdot \frac{R_s}{(R_s^2 + \omega^2 \cdot L_s^2)} + R_L + i \cdot \omega \cdot L_s - i \cdot \omega^3 \cdot \frac{L_s^3}{(R_s^2 + \omega^2 \cdot L_s^2)} \right]} \cdot (-R_s + i \cdot \omega \cdot L_s)$$

$$- V_{cm} \cdot R_s \cdot \frac{(-R_s + i \cdot \omega \cdot L_s)}{(R_d \cdot R_s^2 + R_d \cdot \omega^2 \cdot L_s^2 + R_c \cdot R_s^2 + R_c \cdot \omega^2 \cdot L_s^2 + \omega^2 \cdot L_s^2 \cdot R_s + R_L \cdot R_s^2 + R_L \cdot \omega^2 \cdot L_s^2 + i \cdot \omega \cdot L_s \cdot R_s^2)}$$

$$R_L I_c =$$

$$- V_{cm} \cdot R_s \cdot \frac{(-R_s + i \cdot \omega \cdot L_s)}{(R_d \cdot R_s^2 + R_d \cdot \omega^2 \cdot L_s^2 + R_c \cdot R_s^2 + R_c \cdot \omega^2 \cdot L_s^2 + \omega^2 \cdot L_s^2 \cdot R_s + R_L \cdot R_s^2 + R_L \cdot \omega^2 \cdot L_s^2 + i \cdot \omega \cdot L_s \cdot R_s^2)} \cdot R_L$$


$$R_s := 1000 \quad L_s := 1 \cdot 10^{-9} \quad R_c := 1000$$

$$R_L := 1000 \quad \omega := .1, 100 \dots 1 \cdot 10^7 \quad R_d := 1000$$

$$V_{cm} := 1$$

$$V(\omega) := \frac{\left[\frac{R_s \cdot R_L}{R_s \cdot (R_c + R_d + R_L)} \right] \cdot V_{cm}}{1 + \frac{(\sqrt{-1}) \cdot \omega}{\left[\frac{R_s \cdot (R_c + R_d + R_L)}{L_s \cdot (R_s + R_c + R_d + R_L)} \right]}}$$

- same
all
my
result!

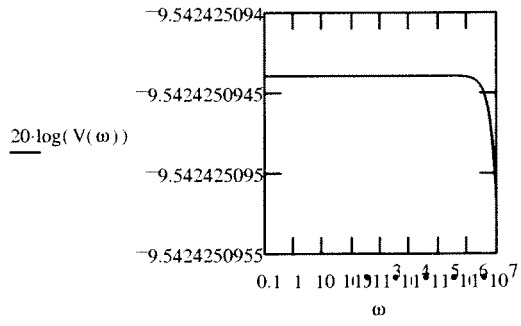


Section 22.17 Long Lines vs Close Lines

h = Height
 d = trace separation
 l = length

h := .0005, .0006... .01
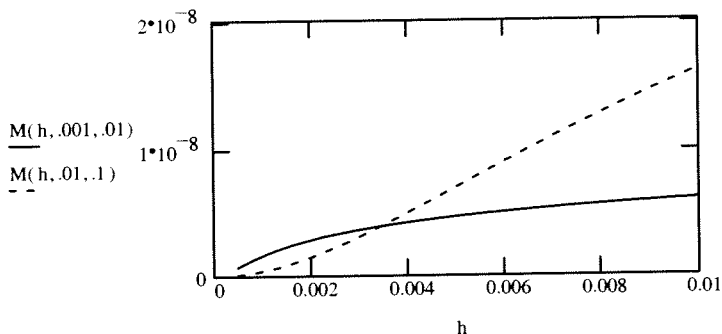
$$M(h, d, l) := 10^{-7} \cdot l \cdot \ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]$$




Mistake in my expression!


$$\epsilon_0 := 8.854 \cdot 10^{-12}$$

$$w := .0004$$
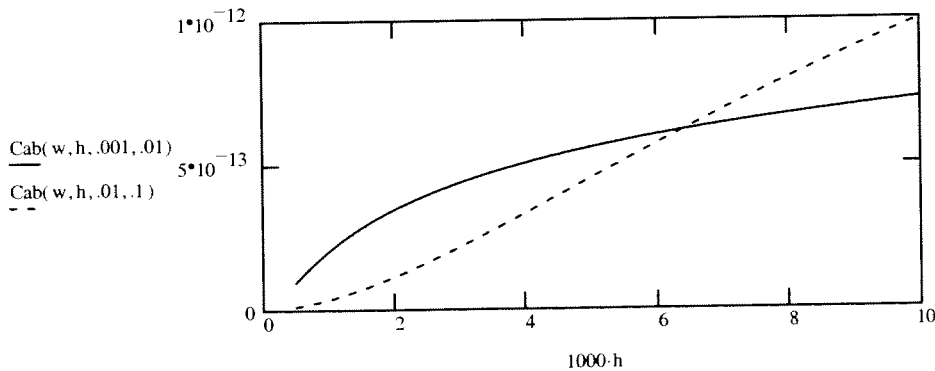
$$C_{ab}(w, h, d, l) := 4 \cdot \pi \cdot \epsilon_0 \cdot l \cdot \frac{\ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]}{\ln \left[\left[1 + \frac{32 \cdot h^2}{w^2} \cdot \left[1 + \sqrt{1 + \left(\frac{\pi \cdot w^2}{8 \cdot h^2} \right)^2} \right]^2 \right] \right] - \ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]^2}$$



w := .0008

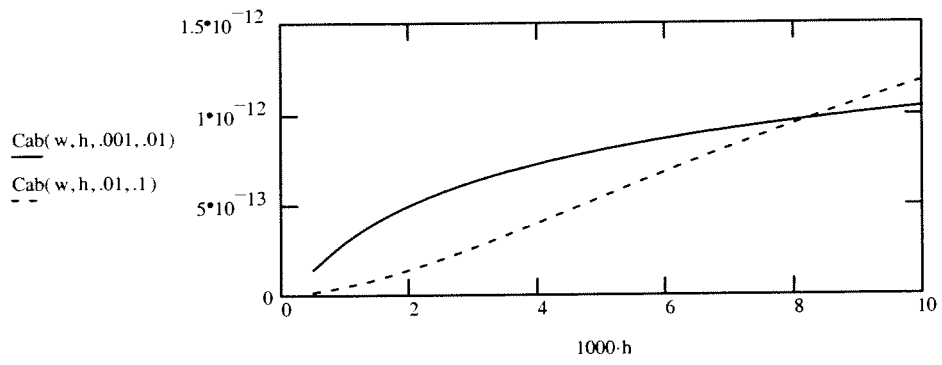

$$w = 15.254 \cdot 10^{-5} \quad \text{lgt} = 0.01 \quad \epsilon_0 = 8.851 \cdot 10^{-12} \quad A = 0.01 \quad R_{bc} = 100$$

$$x = 1, 2, \dots, 120$$


There should be a squared in the equation matches so that the one on page 588 is correct.

$$\omega(x) = \left(x + 1 - 10 \cdot \text{floor} \left(\frac{x}{10} \right) \right) \cdot 10^{\text{floor} \left(\frac{x}{10} \right)}$$

$$C_{ab}(w, h, d) = 4 \cdot \pi \cdot \epsilon_0 \cdot \text{lgt} \cdot \frac{\ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]^2}{\ln \left[1 + \frac{32 \cdot h^2}{w^2} \right] \cdot \sqrt{1 + \left[\frac{\pi \cdot w^2}{8 \cdot h^2} \right]^2} - \ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]^2}$$

$$C_{bc}(w, h, d) = 4 \cdot \pi \cdot \epsilon_0 \cdot \text{lgt} \cdot \frac{\ln \left[1 + \frac{32 \cdot h^2}{w^2} \right] \cdot \sqrt{1 + \left[\frac{\pi \cdot w^2}{8 \cdot h^2} \right]^2}}{\ln \left[1 + \frac{32 \cdot h^2}{w^2} \right] \cdot \sqrt{1 + \left[\frac{\pi \cdot w^2}{8 \cdot h^2} \right]^2} - \ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]^2} \cdot C_{ab}(w, h, d)$$
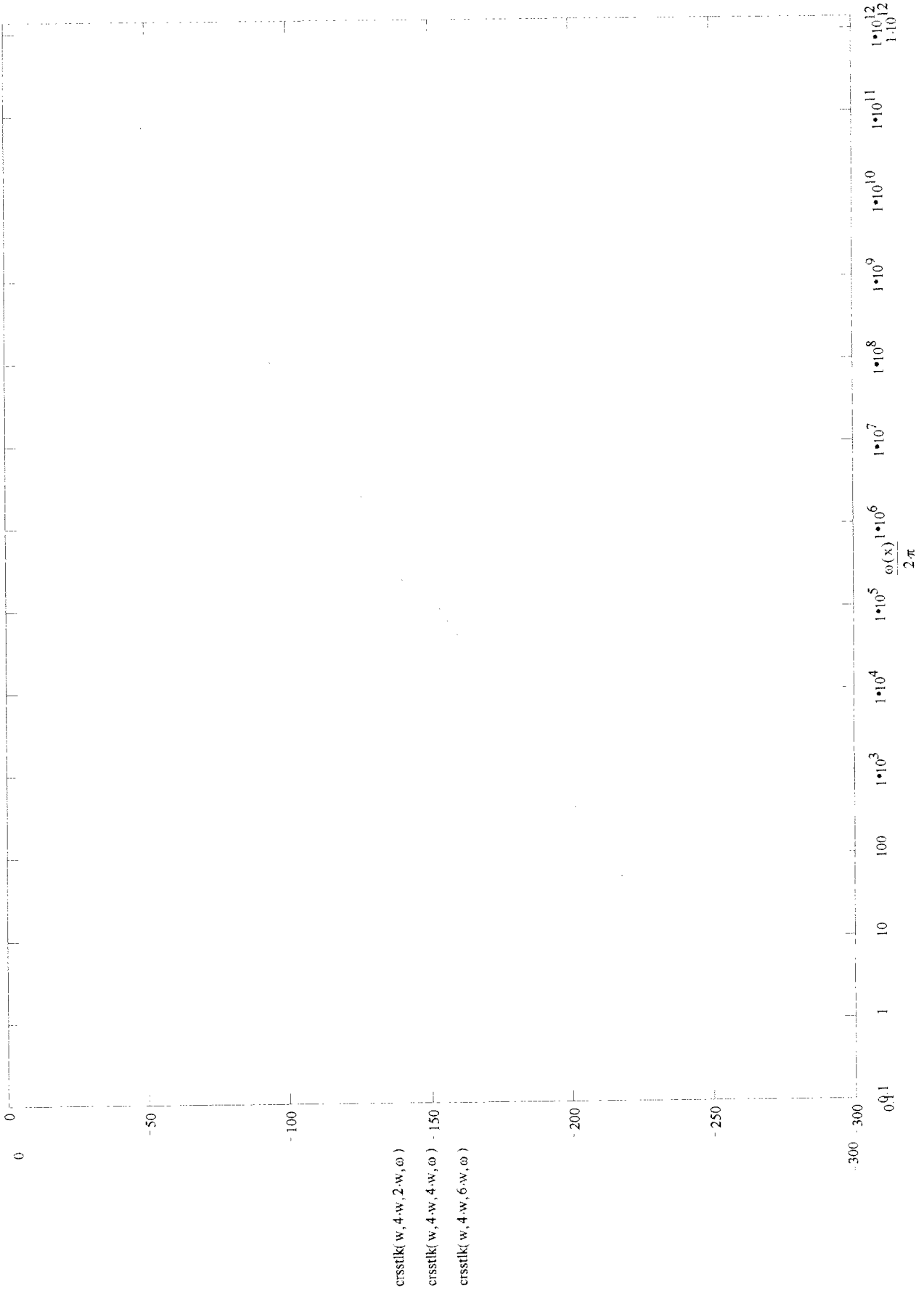
$$\text{crsstk}(w, h, d, \omega) = 20 \cdot \log \left[\frac{\omega(x) \cdot C_{ab}(w, h, d) \cdot R_{bc} \cdot A}{1 + \left[\omega(x) \cdot R_{bc} \cdot (C_{ab}(w, h, d) + C_{bc}(w, h, d)) \right]^2} \right]$$




$$w = 1 \quad \epsilon_0 = 8.854 \cdot 10^{-12} \quad lgt = 1 \quad d = 2, 2.1, \dots, 10$$

$$C_{ab}(w, h, d) = 4 \cdot \pi \cdot \epsilon_0 \cdot lgt \cdot \frac{\ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]}{\ln \left[1 + \frac{32 \cdot h^2}{w^2} \right] \cdot \sqrt{1 + \frac{\pi \cdot w^2}{8 \cdot h^2}} - \ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]}$$

$$C_{bc}(w, h, d) = 4 \cdot \pi \cdot \epsilon_0 \cdot lgt \cdot \frac{\ln \left[1 + \frac{32 \cdot h^2}{w^2} \right] \cdot \sqrt{1 + \frac{\pi \cdot w^2}{8 \cdot h^2}}}{\ln \left[1 + \frac{32 \cdot h^2}{w^2} \right] \cdot \sqrt{1 + \frac{\pi \cdot w^2}{8 \cdot h^2}} - \ln \left[1 + \left(\frac{2 \cdot h}{d} \right)^2 \right]} - C_{ab}(w, h, d)$$

$$\text{flux}\%(w, h, d) = 100 \cdot \frac{C_{ab}(w, h, d)}{C_{bc}(w, h, d)}$$

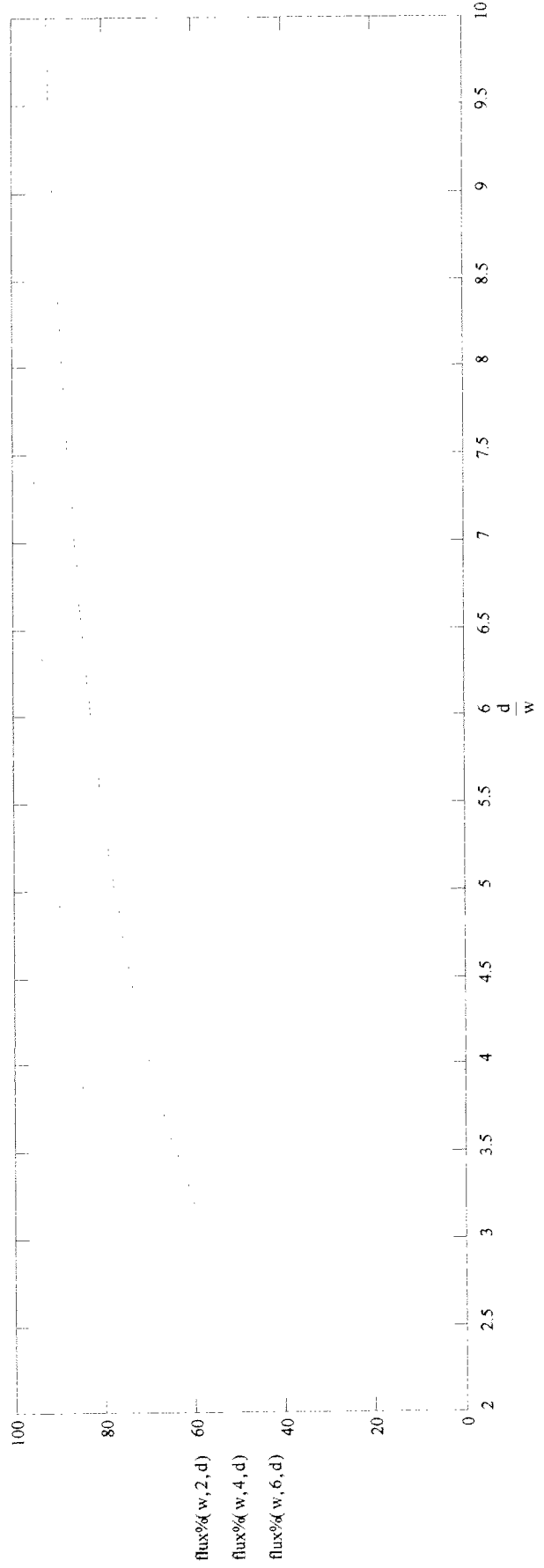Flux should be a squared term here
So the equations match up with page 588



$$\operatorname{erf}\left(\frac{-1}{0.56}\right)$$

-98844272033567473730

$$\operatorname{erf}(\infty)$$

1

$$t \geq 0$$

$$* v(t) = \frac{\Delta V}{2} + \frac{\Delta V}{2} \operatorname{erf}\left(\frac{t-\tau}{k\tau}\right)$$

$$t = 0,$$

$$= \frac{\Delta V}{2} + \frac{\Delta V}{2} \operatorname{erf}\left(\frac{-1}{\underbrace{k}_{0.56}\tau}\right) \approx \frac{\Delta V}{2} + \frac{\Delta V}{2} \underbrace{(-0.9874)}_{\text{approx} = 1}$$

$$\approx \frac{\Delta V}{2} - \frac{\Delta V}{2} = 0 \quad \checkmark$$

$$t = \infty,$$

$$= \frac{\Delta V}{2} + \frac{\Delta V}{2} \operatorname{erf}\left(\frac{\infty-\tau}{k\tau}\right) \approx \frac{\Delta V}{2} + \frac{\Delta V}{2} \underbrace{\operatorname{erf}(\infty)}_1$$

$$\approx \frac{\Delta V}{2} + \frac{\Delta V}{2} = \frac{\cancel{2}\Delta V}{\cancel{2}} = \Delta V$$

$$x \sim \lambda$$

$$t \sim \alpha$$

$$f(\lambda, t) = e^{-\lambda^2} = f(u_1, \alpha)$$

$$f(u_2, \alpha) = e^{-\alpha^2}$$

$$u_1 = \frac{t-\tau}{k\lambda}$$

$$u_2 = 0$$

$$\frac{du_1}{dt} = \frac{1}{k\lambda}$$

$$\frac{du_2}{dt} = 0$$

$$\frac{dv}{dt} = 0 + \frac{\Delta V \cdot 2}{2 \sqrt{\pi}} \left[\underbrace{-\left(\frac{t-\tau}{k\lambda}\right)^2}_{f(u_1, \alpha)} \cdot \underbrace{\frac{1}{k\lambda}}_{\frac{du_1}{dt}} - \underbrace{e^{-\alpha^2}}_{f(u_2, \alpha)} \cdot \underbrace{0}_{\frac{du_2}{dt}} + \int_0^{\frac{t-\tau}{k\lambda}} 0 \, dx \right]$$

$\frac{d}{dt} \frac{\Delta V}{2} = 0$

$$\frac{dv}{dt} = \frac{\Delta V}{\sqrt{\pi}} \cdot \frac{1}{k\lambda} e^{-\left(\frac{t-\tau}{k\lambda}\right)^2} \quad \checkmark$$

$$\frac{dV}{dt} = \frac{\Delta V}{k\tau\sqrt{\pi}} e^{-\left(\frac{t-\tau}{k\tau}\right)^2}$$

$$\frac{d^2V}{dt^2} = \frac{\Delta V}{k\tau\sqrt{\pi}} e^{-\left(\frac{t-\tau}{k\tau}\right)^2}$$

$$\frac{d}{dx} e^x = e^x$$

$$-2\left(\frac{t-\tau}{k\tau}\right) \cdot \frac{d}{dt}\left(\frac{t-\tau}{k\tau}\right)$$

$\frac{d}{dt}\left(\frac{t}{k\tau}\right) = \frac{1}{k\tau}$
 $\frac{d}{dt}\left(\frac{-\tau}{k\tau}\right) = 0$

$$\frac{d}{dt}\left(-\left[\frac{t-\tau}{k\tau}\right]\right)$$

$$\frac{d^2V}{dt^2} = \frac{\Delta V}{k\tau\sqrt{\pi}} e^{-\left[\frac{t-\tau}{k\tau}\right]^2} \left[\frac{-2(t-\tau)}{(k\tau)^2} \right]$$

$$\frac{d^2V}{dt^2} = \frac{-2\Delta V(t-\tau)}{(k\tau)^3\sqrt{\pi}} e^{-\left[\frac{t-\tau}{k\tau}\right]^2}, \quad (t-\tau) = -(\tau - t)$$

$$\frac{d^2V}{dt^2} = \frac{2\Delta V(\tau-t)}{(k\tau)^3\sqrt{\pi}} e^{-\left(\frac{t-\tau}{k\tau}\right)^2}$$

$$\frac{d}{dt} \frac{2 \cdot \Delta V \cdot (\tau - t)}{(k \cdot \tau)^3 \cdot \sqrt{\pi}} \cdot e^{-\left(\frac{t-\tau}{k \cdot \tau}\right)^2} = 0$$

solve for t

$$\left[\begin{array}{l} \left(1 + \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau \\ \left(1 - \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau \end{array} \right] = \tau \left(1 \pm \frac{k}{\sqrt{2}}\right)$$

$$\left(1 + \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau$$

$$\left. \frac{d^2 V}{dt^2} \right|_{t = \tau \left[1 + \frac{k}{\sqrt{2}}\right]} = \frac{2 \cdot \Delta V \cdot \left[\tau - \left(1 + \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau\right]}{(k \cdot \tau)^3 \cdot \sqrt{\pi}} \cdot e^{-\left[\frac{\left(1 + \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau - \tau}{k \cdot \tau}\right]^2}$$

$$\frac{-\Delta V \cdot \sqrt{2}}{\tau^2 \cdot k^2} \cdot \frac{\exp\left(\frac{-1}{2}\right)}{\frac{1}{\pi^2}} = \frac{-2 \Delta V}{(k \tau)^2 \sqrt{2} \pi} e^{-1/2}$$

$\pi^2 = \sqrt{\pi}$

$$\left. \frac{d^2 V}{dt^2} \right|_{t = \tau \left[1 - \frac{k}{\sqrt{2}}\right]} = \frac{2 \cdot \Delta V \cdot \left[\tau - \left(1 - \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau\right]}{(k \cdot \tau)^3 \cdot \sqrt{\pi}} \cdot e^{-\left[\frac{\left(1 - \frac{1}{2} \cdot \sqrt{2} \cdot k\right) \cdot \tau - \tau}{k \cdot \tau}\right]^2}$$

$$\frac{\Delta V \cdot \sqrt{2}}{\tau^2 \cdot k^2} \cdot \frac{\exp\left(\frac{-1}{2}\right)}{\frac{1}{\pi^2}} = \frac{2 \Delta V}{(k \tau)^2 \sqrt{2} \pi} e^{-1/2}$$

$$\left. \frac{di(t)}{dt} \right|_{\max} < \frac{1}{R} \frac{dv}{dt} + C \frac{d^2 i}{dt^2}$$

$$< \frac{1}{R} \frac{\Delta V}{k\tau\sqrt{\pi}} e^{-\frac{(t-\tau)^2}{k\tau^2}} + C \frac{2\Delta V}{(k\tau)^2 \sqrt{2\pi}} e^{-1/2}$$

max when $t = \tau$

max when $t = \tau \pm \frac{k\tau}{\sqrt{2}}$

$$< \frac{1}{R} \frac{\Delta V}{k\tau\sqrt{\pi}} + C \frac{2\Delta V}{(k\tau)^2 \sqrt{2\pi}} e^{-1/2}$$




$$< \frac{1}{R} \frac{\Delta V}{\tau} \cdot \frac{1}{k\sqrt{\pi}} + C \cdot \frac{\Delta V}{\tau^2} \left[e^{-1/2} \cdot \frac{2}{k^2 \cdot \sqrt{2\pi}} \right]$$

$$\frac{1}{(0.56) \cdot \sqrt{\pi}} \approx 0.9921$$

$$\frac{e^{-1/2} \cdot 2}{(0.56)^2 \sqrt{2\pi}} \approx 1.54 \approx 1.5$$

$$< \frac{1}{R} \frac{\Delta V}{\tau} + C \frac{\Delta V}{\tau^2} [1.5] \quad \checkmark$$

L.R. Paul, Solution of transmission line equations for 3-cond lines in homogeneous media, IEEE Trans. on Electromag. Compatibility, EMC-20, 216-222 (1978)

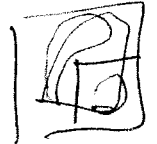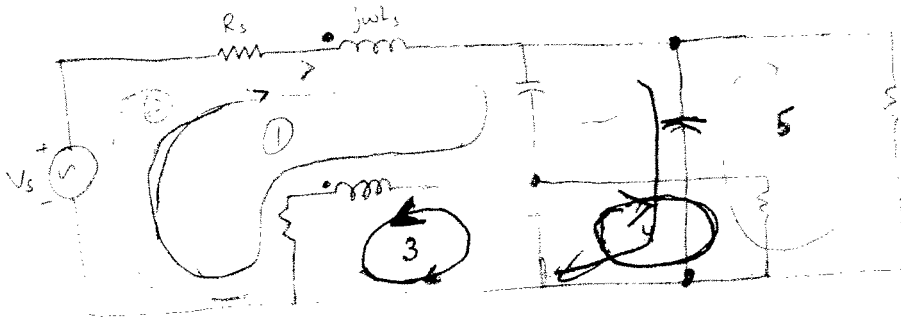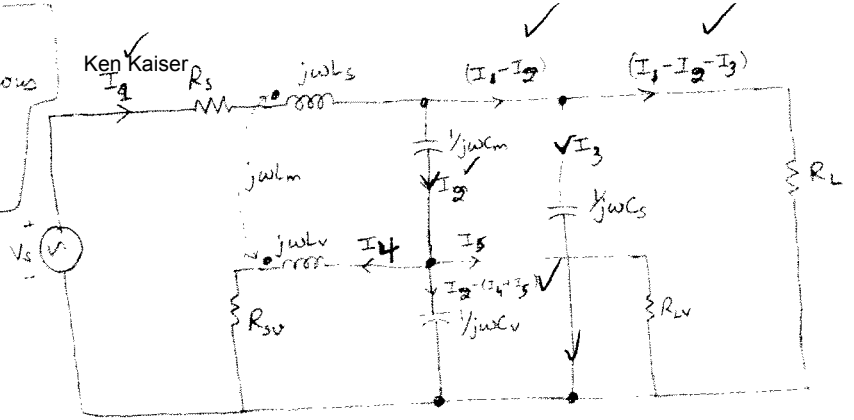

Loop 1:

$$-V_s + (R_s + j\omega L_s)I_1 - j\omega L_m I_4 + \frac{1}{j\omega C_m} I_2 + (R_{sv} + j\omega L_v)I_4 - j\omega L_m I_1 = 0$$

$$\Rightarrow (R_s + j\omega L_s - j\omega L_m)I_1 + (R_{sv} + j\omega L_v - j\omega L_m)I_4 + \frac{1}{j\omega C_m} I_2 = V_s \quad \text{--- (1)}$$

Loop 2:

$$-V_s + (R_s + j\omega L_s)I_1 - j\omega L_m I_4 + \frac{1}{j\omega C_s} I_3 = 0$$

$$(R_s + j\omega L_s)I_1 + \frac{1}{j\omega C_s} I_3 - j\omega L_m I_4 = V_s \quad \text{--- (2)}$$

Loop 3:

$$(R_{sv} + j\omega L_v)I_4 - j\omega L_m I_1 - \frac{1}{j\omega C_v} (I_2 - I_4 - I_5) = 0$$

$$-j\omega L_m I_1 + (R_{sv} + j\omega L_v + \frac{1}{j\omega C_v})I_4 - \frac{1}{j\omega C_v} I_2 + \frac{1}{j\omega C_v} I_5 = 0 \quad \text{--- (3)}$$

Loop 4:

$$R_{lv} I_5 - \frac{1}{j\omega C_v} (I_2 - I_4 - I_5) = 0$$

$$-\frac{1}{j\omega C_v} I_2 + \frac{1}{j\omega C_v} I_4 + (R_{lv} + \frac{1}{j\omega C_v})I_5 = 0 \quad \text{--- (4)}$$

Loop 5:

$$R_L(I_1 - I_2 - I_3) - \frac{1}{j\omega C_s} I_3 = 0$$

$$\Rightarrow R_L I_1 - R_L I_2 - (R_L + \frac{1}{j\omega C_s}) I_3 = 0 \quad \text{--- (5)}$$

Given

Ken Kaiser

$$(R_s + j\omega L_s - j\omega L_m) \cdot I_1 + \frac{1}{j\omega C_m} \cdot I_2 + [(R_{sv} + j\omega L_v) - j\omega L_m] \cdot I_4 = V_s$$

$$(R_s + j\omega L_s) \cdot I_1 + \frac{1}{j\omega C_s} \cdot I_3 - j\omega L_m \cdot I_4 = V_s$$

$$-j\omega L_m \cdot I_1 - \frac{1}{j\omega C_v} \cdot I_2 + \left(R_{sv} + j\omega L_v + \frac{1}{j\omega C_v} \right) \cdot I_4 + \frac{1}{j\omega C_v} \cdot I_5 = 0$$

$$-\frac{1}{j\omega C_v} \cdot I_2 + \frac{1}{j\omega C_v} \cdot I_4 + \left(R_{Lv} + \frac{1}{j\omega C_v} \right) \cdot I_5 = 0$$

$$R_L \cdot I_1 - R_L \cdot I_2 - \left(R_L + \frac{1}{j\omega C_s} \right) \cdot I_3 = 0$$

my
check
Maybe one
eqn is essential
for a repeat
of another

Find $(I_1, I_2, I_3, I_4, I_5) \rightarrow$

No Symbolic result

$$C_m \ll C_v$$

$$C_m \ll C_m$$

Using $C \cong 1$ for $L \ll 1$

Ken Kaiser

$\beta \cong 1$

$\beta R \ll 1$

$$\therefore \text{Den} = 1 - \omega^2 \tau_a \tau_r [1 - \beta] + j\omega(\tau_a + \tau_r) \\ = 1 - \omega^2 \tau_a \tau_r + j\omega(\tau_a + \tau_r)$$

on factorising

$$\text{Den} = (1 + j\omega\tau_a)(1 + j\omega\tau_r) \quad \text{Hence verified}$$

Cross check \rightarrow

$$(1 + j\omega\tau_a)(1 + j\omega\tau_r)$$

$$= 1 + j\omega\tau_r + j\omega\tau_a - \omega^2 \tau_a \tau_r$$

$$= 1 - \omega^2 \tau_a \tau_r + j\omega(\tau_a + \tau_r)$$

Hence verified

$$\Delta \hat{V}_{NE} = \frac{1}{\text{Den}} \left[\frac{R_{NE}}{R_{NE} + R_{FE}} j\omega L m d (1 + \beta) \hat{I}_{GDC} + \frac{R_{NE} R_{FE}}{R_{NE} + R_{FE}} j\omega L m d (1 + \beta) \hat{V}_{GDC} \right]$$


$$= \frac{1}{\text{Den}} \left[\frac{R_{NE}}{R_{NE} + R_{FE}} j\omega L m d \hat{I}_{GDC} + \frac{R_{NE} R_{FE}}{R_{NE} + R_{FE}} j\omega L m d \hat{V}_{GDC} \right] \quad \text{Hence verified}$$

$$\text{ii) } \hat{V}_{FE} = \frac{1}{\text{Den}} \left[-\frac{R_{FE}}{R_{NE} + R_{FE}} j\omega L m d \hat{I}_{GDC} + \frac{R_{NE} R_{FE}}{R_{NE} + R_{FE}} j\omega L m d \hat{V}_{GDC} \right]$$

Now if freq of excitation is also small then $\omega \ll 1$

$$\therefore \text{Den} = 1$$

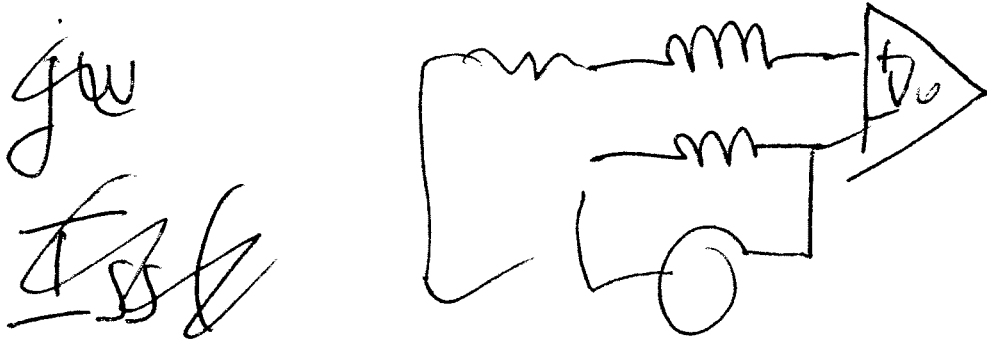~~$I_{cs} / (R_d + R_c + R_L + j\omega L_c)$~~ Crosstalk
Chapter



$$I_{SS} (j\omega L + R_s) = -V_{cms} + j\omega L I_o$$

$$I_{SS} = \frac{-V_{cms}}{j\omega L + R_s} + \frac{j\omega L I_o}{j\omega L + R_s}$$

$$I_{CS} = V_{CM1} \left[\frac{j\omega L + R_1 - j\omega L}{j\omega L + R_1} \right]$$

$$R_d + R_c + R_L + j\omega L + \frac{\omega^2 L^2}{j\omega L + R_1}$$

$$= \frac{V_{CM1} R_1}{(R_d + R_c + R_L + j\omega L) (j\omega L + R_1) + \omega^2 L^2}$$

$$= \frac{V_{CM1} R_1}{j\omega L (R_d + R_c + R_L) - \omega^2 L^2 + R_1 (R_d + R_c + R_L) + j\omega L R_1 + \omega^2 L^2}$$

$$= \frac{V_{CM1} R_1}{j\omega L (R_d + R_c + R_L) - \omega^2 L^2 + R_1 (R_d + R_c + R_L) + j\omega L R_1 + \omega^2 L^2}$$

$$= \frac{V_{CM1} R_1}{j\omega L (R_d + R_c + R_L) - \omega^2 L^2 + R_1 (R_d + R_c + R_L) + j\omega L R_1 + \omega^2 L^2}$$

$$= \frac{V_{CM1} R_1}{j\omega L (R_d + R_c + R_L) - \omega^2 L^2 + R_1 (R_d + R_c + R_L) + j\omega L R_1 + \omega^2 L^2}$$



$$= \frac{V_{CM1} R_1}{j\omega L (R_d + R_c + R_L) + R_1 (R_d + R_c + R_L)}$$

$$= \frac{V_{CM1} R_1}{j\omega L (R_d + R_c + R_L) + R_1 (R_d + R_c + R_L)}$$

$$I_{CS} = \frac{V_{CM} \beta}{R_d + R_{ct} + R_L}$$


$$\frac{j\omega L (R_d + R_{ct} + R_c + R_L)}{R_s (R_d + R_{ct} + R_c)}$$

From Paul or

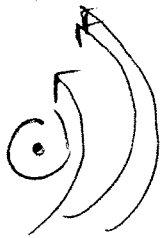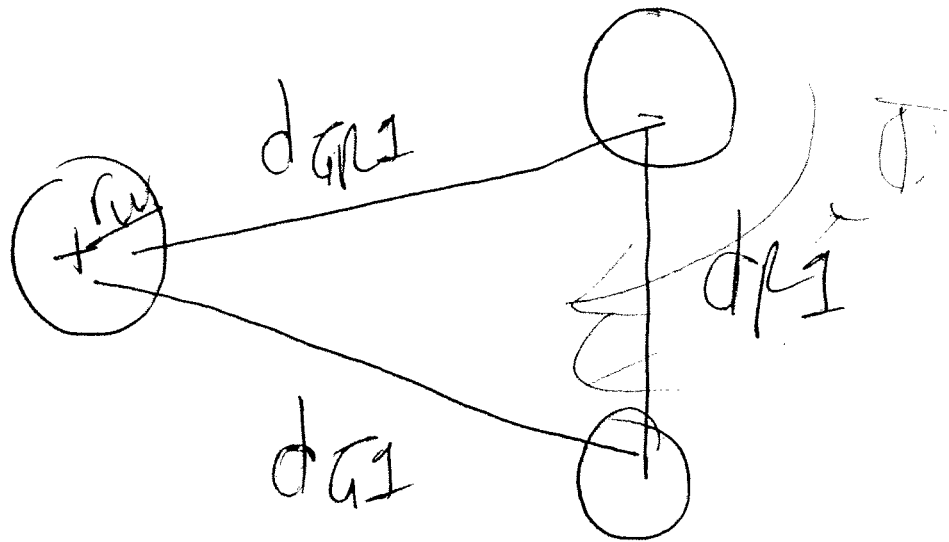

$$L_{M1} = \frac{\mu_0}{2\pi} \ln \left(\frac{d_{gr2}}{d_{gr1} r_w} \right)$$

return current

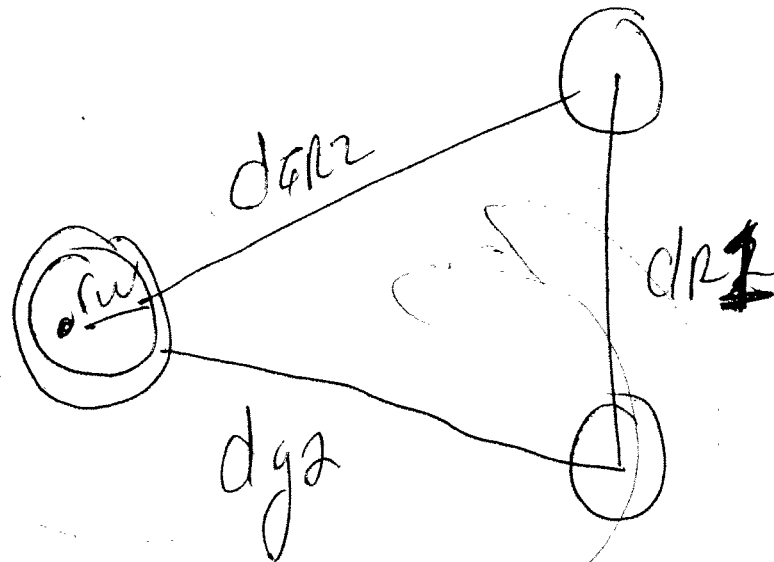

$$L_{M2} = \frac{\mu_0}{2\pi} \ln \left(\frac{d_{gr2} d_{r1}}{d_{gr1} r_w} \right)$$



If current
 flow 2 "w" in opposite direction ²
 the fluxes subtract and


$$l_{m2} \equiv l_{m1} - l_{m2}$$

$$= \frac{\mu_0}{2\pi} I_N \left[\frac{d_{g1} d_{r1}}{d_{gr2} l_w} \times \frac{d_{gr2} l_w}{d_{gz} d_{r1}} \right]$$

$$= \frac{\mu_0}{2\pi} I_N \left[\frac{d_{g1} d_{gr2}}{d_{gr1} d_{gz}} \right] = 2 \times 10^{-7} I_N \left[\frac{d_{13} d_{23}}{d_{13} d_{24}} \right]$$

agrees with ✓
 Wolker ✓

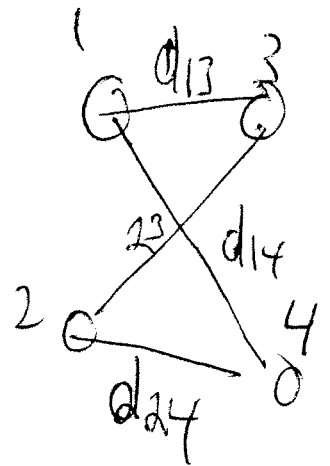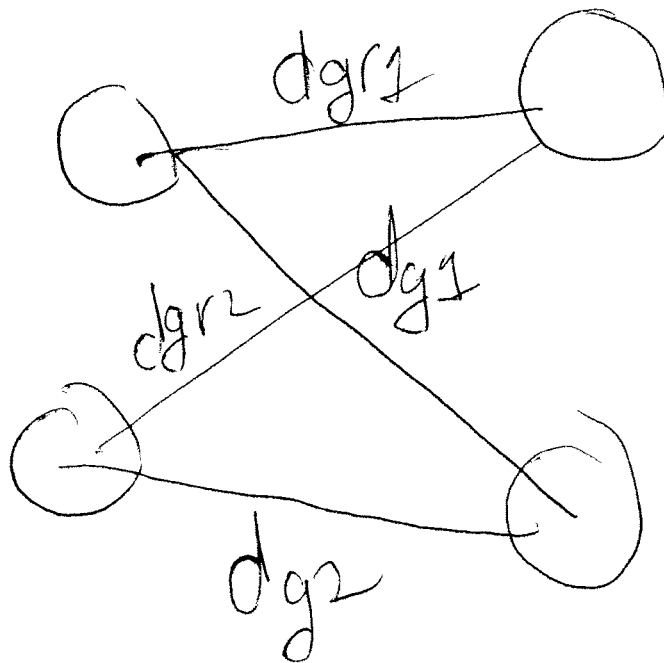

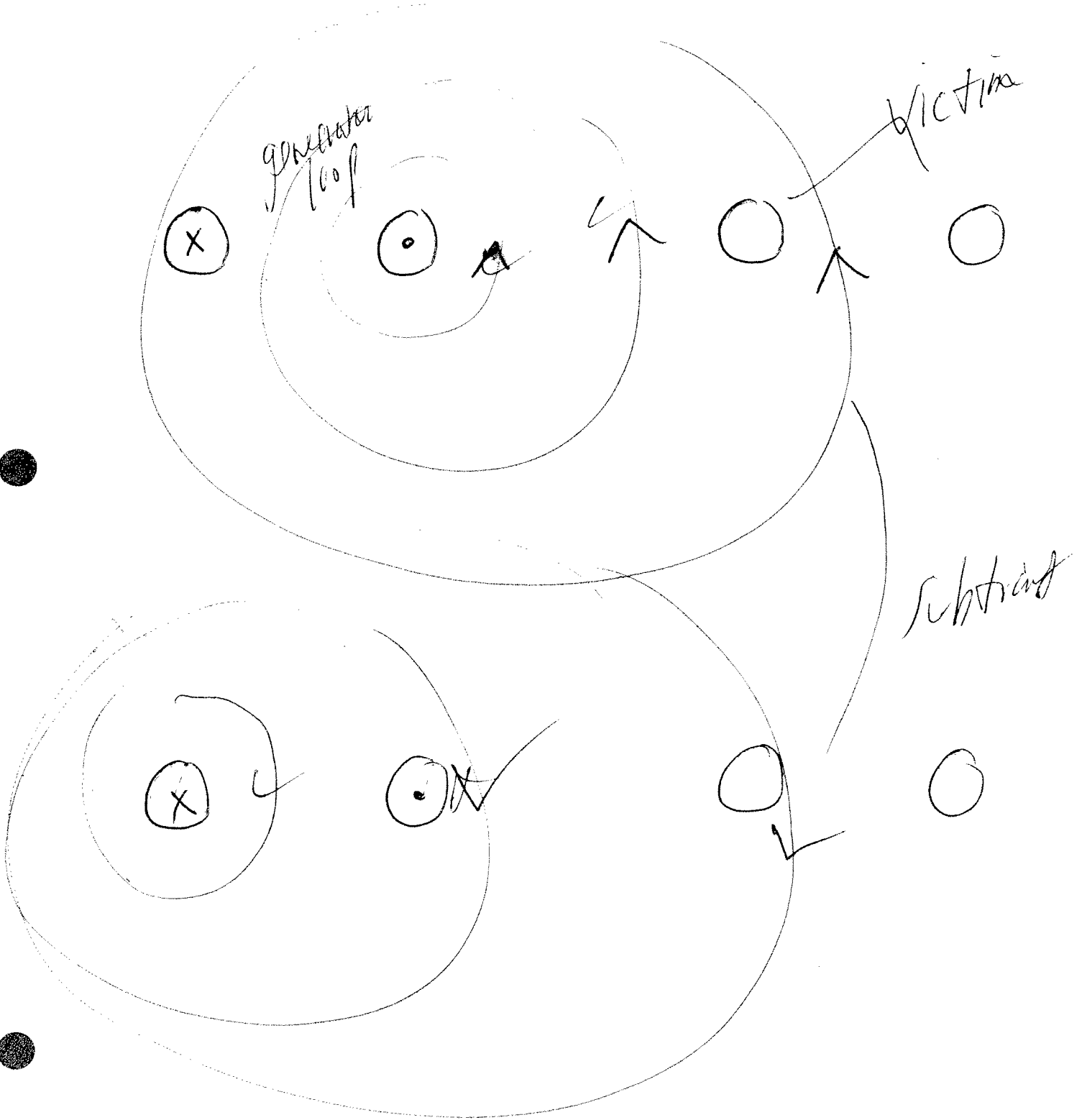

Schellkoeff

Ken Kaiser

b = outer radius
 a = inner radius

$$\sigma^2 = 2\pi\sigma_0 f_j$$

$$\sigma = \sqrt{2\pi\sigma_0 f_j} = \frac{1}{f} + \frac{f}{f}$$

$$Z_t = \frac{1}{2\pi\sigma_0 b D}$$

$$D = I_1(\sigma b) K_1(\sigma a) - I_1(\sigma a) K_1(\sigma b)$$

let $\delta = \sigma$ to avoid confusion
 $\sigma_c = \delta$

$$Z_t = \frac{1}{2\pi\sigma a b D}$$

also from other eqn

$$n \equiv \frac{\delta}{\sigma}$$

$$Z_t \approx \frac{n}{2\pi r_{ab}} \text{ (sch } \sigma t = \frac{\delta}{2\pi r_{ab} \sigma} \frac{1}{\sinh \delta t}$$

if $r_{ab} \approx a$ for thin shield

$$= \frac{\delta}{2\pi a \sigma} \frac{1}{\sinh \delta t}$$

✓
agrees with common used result

$$D = I_1(\delta b) K_1(\delta a) - I_1(\delta a) K_1(\delta b)$$

large argument approx

$$K_1(x) \approx \frac{e^{-x}}{\sqrt{\frac{2x}{\pi}}}$$

$$I_1(x) \approx \frac{e^x}{\sqrt{2\pi x}}$$

$$D \approx \frac{e^{\delta b}}{\sqrt{2\pi\delta b}} \frac{e^{-\delta a}}{\sqrt{\frac{2\delta a}{\pi}}} - \frac{e^{\delta a}}{\sqrt{2\pi\delta a}} \frac{e^{-\delta b}}{\sqrt{\frac{2\delta b}{\pi}}}$$

$$= \frac{e^{\delta(b-a)}}{2\delta\sqrt{ab}} - \frac{e^{-\delta(b-a)}}{2\delta\sqrt{ab}}$$

$$= \frac{1}{\delta\sqrt{ab}} \frac{e^{\delta(b-a)} - e^{-\delta(b-a)}}{2}$$

$$D \doteq \frac{1}{\sigma \sqrt{ab}} \sinh(\sigma(b-a)) \quad \text{let } b-a = t \quad 2$$

$$D \doteq \frac{1}{\sigma \sqrt{ab}} \sinh \sigma t$$

$$\begin{aligned} \therefore Z_t &= \frac{1}{2\pi \cancel{ab} \frac{1}{\sigma \sqrt{ab}} \sinh \sigma t} \\ &= \frac{\sigma}{2\pi \sqrt{ab} \cancel{\sigma} \sinh \sigma t} \\ &= \frac{\sigma}{2\pi \sqrt{ab} \sigma \sinh \sigma t} \quad \checkmark \end{aligned}$$

3

Let's \approx Tsalkovich's eqn

$$Z_{it} \equiv \frac{\gamma}{2\pi\sigma\sqrt{ab}D}$$

$$D = I_1(\gamma b) K_1(\gamma a) - K_1(\gamma b) I_1(\gamma a)$$

Same D as before

$$\therefore D \approx \frac{1}{\gamma\sqrt{ab}} \sinh \gamma t$$

$$Z_t \approx \frac{\gamma}{2\pi\sigma \frac{\sqrt{ab}}{\gamma\sqrt{ab}} \sinh \gamma t}$$

=

DELPHIEnergy & Engine
Management Systems

Prob 23.24

ECE-640

SENSIVITY TO 60HZ NOISE —

① Why are low-level analog instrumentation extra sensitive to low freq. noise?

- low frequency noise (e.g. 60Hz) is in the range of operation of these devices, therefore it cannot be filtered.
- low levels can be affected by induced low frequency voltages

② Should shielded twisted pair be grounded \rightarrow one or both ends?

If the source and measurement instrument are both grounded
then the shield should be grounded \rightarrow both ends.

③ Is the shield acting as an electric or magnetic field shield?

The shield is acting as a magnetic field "shield"
by reducing the area of the ground loop.



A system or transmission line is balanced when the impedance seen by each line to ground is the same.

Twisted pair is usually balanced but not always depending on how it is terminated it can be unbalanced.



Grounded at only one end to avoid ground loops.

In this configuration it is unbalanced in the sense that the impedances seen between each wire and ground are not the same. One wire of the twisted pair is connected to the reference conductor at the near end, while the other end is not connected to the reference conductor in order to avoid ground loops between the wire and reference conductor, which will allow flow of circulating currents in that loop.



This is unbalanced in the sense that impedances seen by each wire and the reference conductor are equal and is due to center-tapped transformers.

Some radio is usually balanced, but not always. A double loop antenna, two loop antenna in parallel, is a balanced device.

Center feed dipole antenna is a balanced device, i.e., they are electrically symmetrical with respect to the feed point.

A balanced antenna should be fed by a balanced feeder system to preserve this electrical symmetry with respect to ground, thereby avoiding any difficulties with unbalanced currents on the line and undesirable radiation from the transmission line itself.



at loop antenna fed at the center through central wire then one side of the antenna is connected to the shield while the other is connected to the inner conductor. On the side

connected to the shield, current can be directed from flowing into the antenna and instead can flow through the outside of the coaxial shield. The field from this set up cannot be canceled by the field from the inner conductor because the field inside cable cannot escape through the shielding of the outer conductor. Hence outside current flow can cause some radiation.

A system is balanced when the impedances seen by each line to ground is same but to every other conductor may not be same



W/O of self inductance in a balanced mode with ground of both conductors, so that volt of the signal wire and volt of return wire to common and 180° out of phase

I/P to output is balanced since no imbalance between signal wire and common mode of the line implies both signal wires 2 times faster

The system eliminates any common mode noise

So have the impedance both to 2 lines = 2Z/2

Double coax pseudo balanced line




A balanced shielded pair can be achieved as a set of two coaxial cables. Each outer conductor becomes the shield of the other with the shields are tied to a common ground plane. In this case the shield of each coax is no longer the return path.

Advantage of shielded pair is of a coaxial cable - each with its own shielded structure from which a common mode is considered to be the ground plane. This choice impedes both common mode radiation and higher frequency.

Advantage of shielded pair is of a coaxial cable - each with its own shielded structure from which a common mode is considered to be the ground plane. This choice impedes both common mode radiation and higher frequency.

Problem 23.18

ECE-640

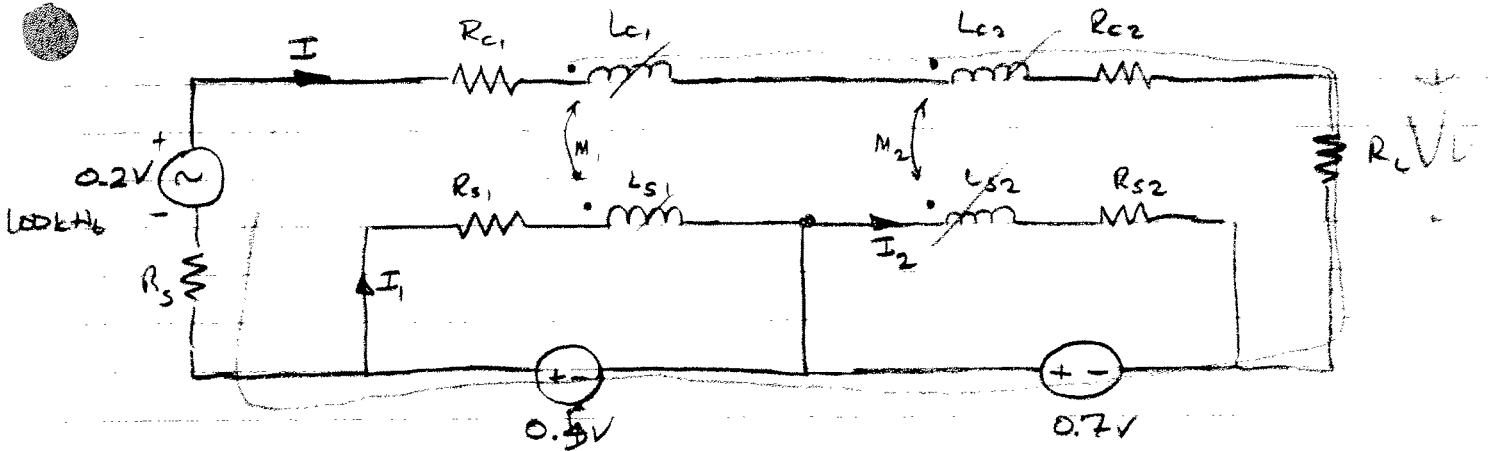

$$0.4 + 0.7 =$$

$$① \quad 0.2 = I(R_3 + R_{c1} + j\omega L_{c1} + j\omega L_{c2} + R_{c2} + R_L) + I_1 j\omega M_1 + I_2 j\omega M_2$$

$$② \quad 0.4 = I_1(R_{s1} + j\omega L_{s1}) + I j\omega M_1$$

$$③ \quad 0.7 = I_2(R_{s2} + j\omega L_{s2}) + I j\omega M_2$$

$f = 100 \text{ kHz}$, Let $\omega L_{s1} \gg R_{s1}$ and $\omega L_{s2} \gg R_{s2}$

Let $M_1 = L_{c1}$ and $M_2 = L_{c2}$

Let $R_3 + R_L \gg R_{c1} + R_{c2}$

$$① \quad 1.3 = I[(R_3 + R_L) + j\omega(L_{c1} + L_{c2})] + j\omega L_{c1} I_1 + j\omega L_{c2} I_2$$

$$② \quad 0.4 = I j\omega L_{c1} + I_1 j\omega L_{s1} \Rightarrow I_1 = \frac{0.4 - I j\omega L_{c1}}{j\omega L_{s1}}$$

$$③ \quad 0.7 = I j\omega L_{c2} + I_2 j\omega L_{s2} \Rightarrow I_2 = \frac{0.7 - I j\omega L_{c2}}{j\omega L_{s2}}$$

$$\begin{aligned} 1.3 &= I[(R_3 + R_L) + j\omega(L_{c1} + L_{c2})] + j\omega L_{c1} \left(\frac{0.4 - I j\omega L_{c1}}{j\omega L_{s1}} \right) + j\omega L_{c2} \left(\frac{0.7 - I j\omega L_{c2}}{j\omega L_{s2}} \right) \\ &= I \left[(R_3 + R_L) + j\omega \left(L_{c1} + L_{c2} - \frac{L_{c1}^2}{L_{s1}} - \frac{L_{c2}^2}{L_{s2}} \right) \right] + 0.4 \frac{L_{c1}}{L_{s1}} + 0.7 \frac{L_{c2}}{L_{s2}} \end{aligned}$$

Let $L_{c1} = L_{s1} = L_1$ and $L_{c2} = L_{s2} = L_2$

$$1.3 = I \left[(R_3 + R_L) + j\omega \left(L_1 + L_2 - \frac{L_1^2}{L_1} - \frac{L_2^2}{L_2} \right) \right] + 0.4 \frac{L_1}{L_1} + 0.7 \frac{L_2}{L_2}$$

$$I = \frac{0.2}{R_3 + R_L}$$

Problem 23.18 cont.

ECE-LAO


$$I = \frac{0.2}{R_s + R_L}$$

$$\text{Voltage across load} = V_L = IR_L = R_L \frac{0.2}{R_s + R_L} = \frac{0.2}{1 + R_s/R_L}$$

$$\text{If } R_L \gg R_s \rightarrow V_L = 0.2 \text{ V} = V_s$$

This result implies that the voltage induced on the center conductor must be equal to the voltage on the shield conductor.

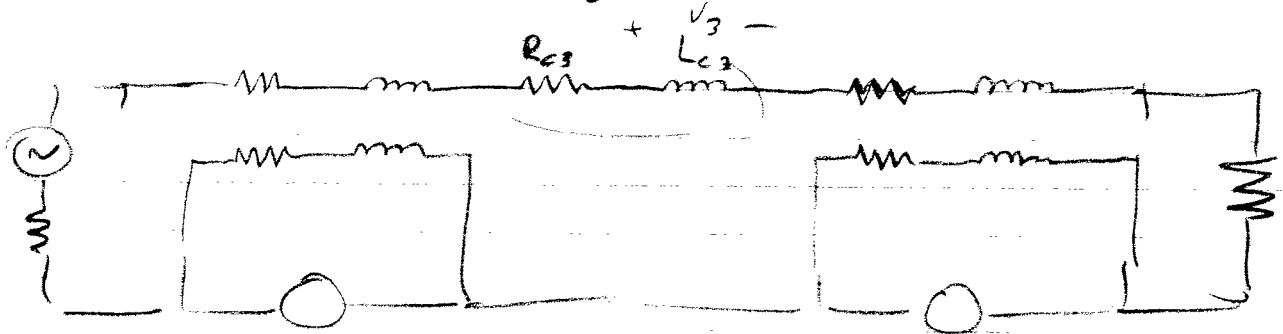if part of the center conductor between the 2 shields is exposed w/ R_{c3} and L_{c3} .



$$1.3 = I \left[(R_s + R_L + R_{c3} + R_{c2} + R_{c1}) + j\omega(L_{c1} + L_{c2} + L_{c3}) \right] + j\omega L_{c1} I_1 + j\omega L_{c2} I_2$$

$$\therefore \text{If } R_s + R_L \gg R_{c1} + R_{c2} + R_{c3}$$

$$1.3 = I \left[(R_s + R_L) + j\omega L_{c3} \right] + 0.4 + 0.7$$

$$I = \frac{0.2}{R_s + R_L + j\omega L_{c3}}$$

$$\therefore V_L = R_L \frac{0.2}{R_s + R_L + j\omega L_{c3}}$$

$$\text{or } V_L = V_{in} - V_3$$

Common mode choke does not affect DM currents

JustHoltz


ECE-640 WEEK 9

23-17

COAX W/ SHIELD GROUNDED 3 PLACES & NOISE ON SHIELD



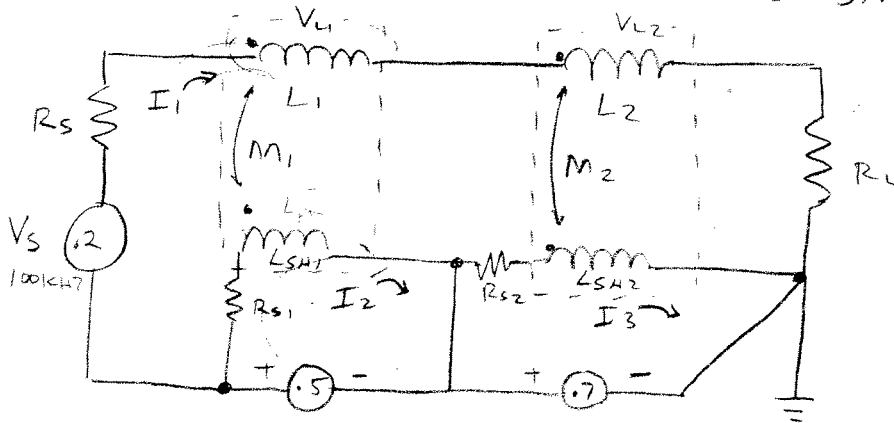TRANSFORMER MODEL FOR COUPLING SHIELD NOISE



AS COAX & SHIELD GROUNDED MIDWAY, CAN ASSUME;

$$L_{SH1} = L_1 = M_1 \quad L_{SH2} = L_2 = M_2$$

A) DETERMINE VOLTAGE INDUCED ACROSS CENTER CONDUCTOR

MATHCAD FOR EQUATIONS

$$V_{INDUCED} = \frac{1.2 R_S + 1.2 R_L + .2 Z_{L1} + .2 Z_{L2}}{(R_S + R_L)}$$

IF $Z_{L1} = Z_{L2}$,

$$= \frac{1.2(R_S + R_L) + .4 Z_L}{(R_S + R_L)}$$

B) DETERMINE VOLTAGE AT LOAD (MATHCAD)

$$V_{LOAD} = \frac{.2 R_L}{(R_S + R_L)}$$

VOLTAGE DIVIDER
SHIELD NOISE CANCELS OUT

7. MATHCAD

ECE-640 Homework 23.17 Coax Cable Modeled with Transformers

$$j := \sqrt{-1} \quad \omega := 10^5 \cdot 2 \cdot \pi \quad V_s := .2$$

$$V_{i1} := .5 \quad V_{i2} := .7$$

Outer Current Loop

$$.7 + .5 + .2 = I_1 \cdot R_S + I_1 \cdot Z_{L1} + I_2 \cdot Z_{M1} + I_1 \cdot Z_{L2} + I_3 \cdot Z_{M2} + I_1 \cdot R_L$$

$$1.4 = I_1 \cdot R_S + I_1 \cdot Z_{L1} + I_2 \cdot Z_{M1} + I_1 \cdot Z_{L2} + I_3 \cdot Z_{M2} + I_1 \cdot R_L$$

$$1.4 = I_1 \cdot R_S + I_1 \cdot Z_{L1} + I_2 \cdot Z_{L1} + I_1 \cdot Z_{L2} + I_3 \cdot Z_{L2} + I_1 \cdot R_L$$

Substitute L1 for M1
& L2 for M2

Current Loop on Shield, Near Source

$$.5 = I_2 \cdot R_{s1} + I_2 \cdot Z_{Lsh1} + I_1 \cdot Z_{M1} \quad \text{Substitute L1 for M1 \& Lsh1 Impedances}$$

$$.5 = I_2 \cdot R_{s1} + I_2 \cdot Z_{L1} + I_1 \cdot Z_{L1}$$

$$I_2 = 1 \cdot \frac{(.5 - 1 \cdot I_1 \cdot Z_{L1})}{(-1 \cdot R_{s1} - 1 \cdot Z_{L1})}$$

Current Loop on Shield, Near Load

$$.7 = I_3 \cdot R_{s2} + I_3 \cdot Z_{Lsh2} + I_1 \cdot Z_{M2}$$

Substitute L2 for M2 & Lsh2
Impedances

$$.7 = I_3 \cdot R_{s2} + I_3 \cdot Z_{L2} + I_1 \cdot Z_{L2}$$

$$I_3 = 1 \cdot \frac{(.7 - 1 \cdot I_1 \cdot Z_{L2})}{(-1 \cdot R_{s2} - 1 \cdot Z_{L2})}$$

Substitute I2 & I3 & Solve for I1

$$1.4 = I_1 \cdot R_S + I_1 \cdot Z_{L1} + I_2 \cdot Z_{L1} + I_1 \cdot Z_{L2} + I_3 \cdot Z_{L2} + I_1 \cdot R_L$$

$$1.4 = I_1 \cdot R_S + I_1 \cdot Z_{L1} + \left[-1 \cdot \frac{(.5 - 1 \cdot I_1 \cdot Z_{L1})}{(-1 \cdot R_{s1} - 1 \cdot Z_{L1})} \right] \cdot Z_{L1} + I_1 \cdot Z_{L2} + \left[-1 \cdot \frac{(.7 - 1 \cdot I_1 \cdot Z_{L2})}{(-1 \cdot R_{s2} - 1 \cdot Z_{L2})} \right] \cdot Z_{L2} + I_1 \cdot R_L$$

$$I_1 = 1 \cdot \frac{\left[1.4 + \frac{.5}{(-1 \cdot R_{s1} - 1 \cdot Z_{L1})} \cdot Z_{L1} + \frac{.7}{(-1 \cdot R_{s2} - 1 \cdot Z_{L2})} \cdot Z_{L2} \right]}{\left[-1 \cdot R_S - 1 \cdot Z_{L1} - \frac{1}{(-1 \cdot R_{s1} - 1 \cdot Z_{L1})} \cdot Z_{L1}^2 - 1 \cdot Z_{L2} - \frac{1}{(-1 \cdot R_{s2} - 1 \cdot Z_{L2})} \cdot Z_{L2}^2 - 1 \cdot R_L \right]}$$

At High Frequencies, Impedance of Shield & Conductor Inductances \gg shield resistances

$$I_1 = 1 \cdot \frac{\left[1.4 + \frac{-5}{(Z_{L1})} \cdot Z_{L1} + \frac{-7}{(Z_{L2})} \cdot Z_{L2} \right]}{\left[-1 \cdot R_S - 1 \cdot Z_{L1} - \frac{-1}{(Z_{L1})} \cdot Z_{L1}^2 - 1 \cdot Z_{L2} - \frac{-1}{(Z_{L2})} \cdot Z_{L2}^2 - 1 \cdot R_L \right]} \quad \text{Ignore R shield at High Frequency}$$

$$I_1 = \frac{.2}{R_S + R_L} \quad \text{High Frequency Simplification}$$

$$I_2 = \frac{\left(.5 + \frac{.2}{R_S + R_L} \cdot Z_{L1} \right)}{(Z_{L1})}$$

$$I_3 = \frac{\left(.7 + \frac{.2}{R_S + R_L} \cdot Z_{L2} \right)}{(Z_{L2})}$$

$$I_2 = 1 \cdot \frac{(5 \cdot R_S + 5 \cdot R_L + 2 \cdot Z_{L1})}{[(R_S + R_L) \cdot Z_{L1}]}$$

$$I_3 = 1 \cdot \frac{(7 \cdot R_S + 7 \cdot R_L + 2 \cdot Z_{L2})}{[(R_S + R_L) \cdot Z_{L2}]}$$

Voltage Across Center Conductor Inductance L1

$$V_{L1 \text{ induced}} = (I_2) \cdot Z_{M1}$$

$$V_{L1 \text{ induced}} = I_2 \cdot Z_{L1}$$

$$V_{L1 \text{ induced}} = 1 \cdot \frac{(5 \cdot R_S + 5 \cdot R_L + 2 \cdot Z_{L1})}{[(R_S + R_L) \cdot Z_{L1}]} \cdot Z_{L1}$$

$$V_{L1 \text{ induced}} = 1 \cdot \frac{(5 \cdot R_S + 5 \cdot R_L + 2 \cdot Z_{L1})}{(R_S + R_L)}$$

Voltage Across Center Conductor Inductance L2

$$V_{L2 \text{ induced}} = I_3 \cdot Z_{M2}$$

$$V_{L2 \text{ induced}} = I_3 \cdot Z_{L2}$$

$$V_{L2 \text{ induced}} = 1 \cdot \frac{(7 \cdot R_S + 7 \cdot R_L + 2 \cdot Z_{L2})}{[(R_S + R_L) \cdot Z_{L2}]} \cdot Z_{L2}$$

$$V_{L2 \text{ induced}} = 1 \cdot \frac{(7 \cdot R_S + 7 \cdot R_L + 2 \cdot Z_{L2})}{(R_S + R_L)}$$

Total Voltage Induced Across Center Conductor

$$V_{\text{ induced}} = V_{L1 \text{ induced}} + V_{L2 \text{ induced}}$$

$$V_{\text{ induced}} = 1 \cdot \frac{(5 \cdot R_S + 5 \cdot R_L + 2 \cdot Z_{L1})}{(R_S + R_L)} + 1 \cdot \frac{(7 \cdot R_S + 7 \cdot R_L + 2 \cdot Z_{L2})}{(R_S + R_L)}$$

$$V_{\text{ induced}} = 2 \cdot \frac{(6 \cdot R_S + 6 \cdot R_L + Z_{L1} + Z_{L2})}{(R_S + R_L)}$$

Total Voltage Across Center Conductor (Induced + Signal)

$$V_{\text{center}} = .2 + .5 + .7 - R_S \left(\frac{.2}{R_S + R_L} \right) - R_L \left(\frac{.2}{R_S + R_L} \right)$$

$$V_{\text{center}} = .2 \cdot \frac{(-7 \cdot R_S - 6 \cdot R_L + R_S)}{(R_S + R_L)}$$

Voltage at Load

$$V_{\text{Load}} = I_1 \cdot R_L$$

$$V_{\text{Load}} = \left(\left(\frac{.2}{R_S + R_L} \right) \right) \cdot R_L$$

$$V_{\text{Load}} = .2 \cdot \frac{R_L}{(R_S + R_L)}$$