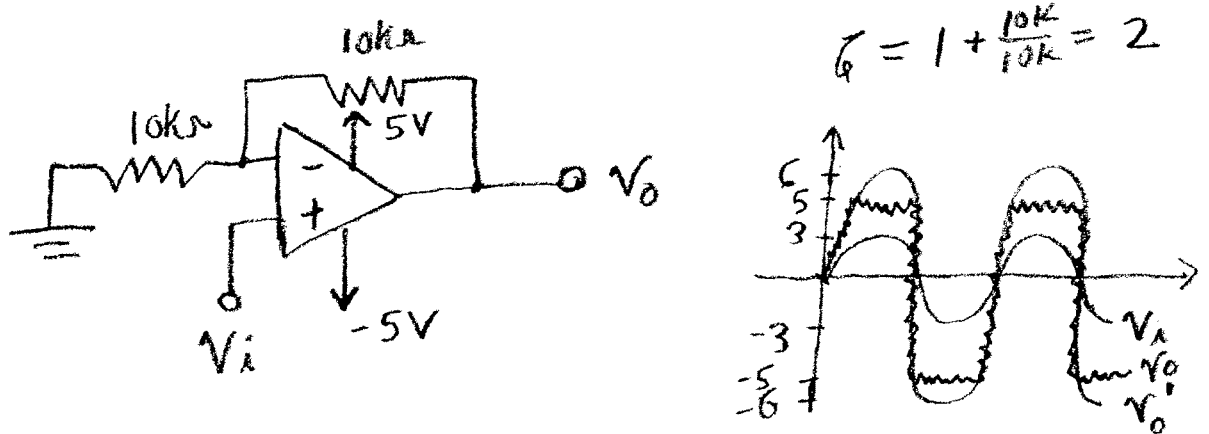



11. Name one characteristic of an ideal op-amp.

12. The input signal for the following ideal op-amp circuit is $v_i(t) = 3 \sin(\omega t)$ V. Sketch the output signal, clearly indicating the maximum and minimum values of the amplitude.



13. For the following circuit involving an ideal-op, determine the relationship

$$\frac{I_C(\omega)}{V_i(\omega)}$$

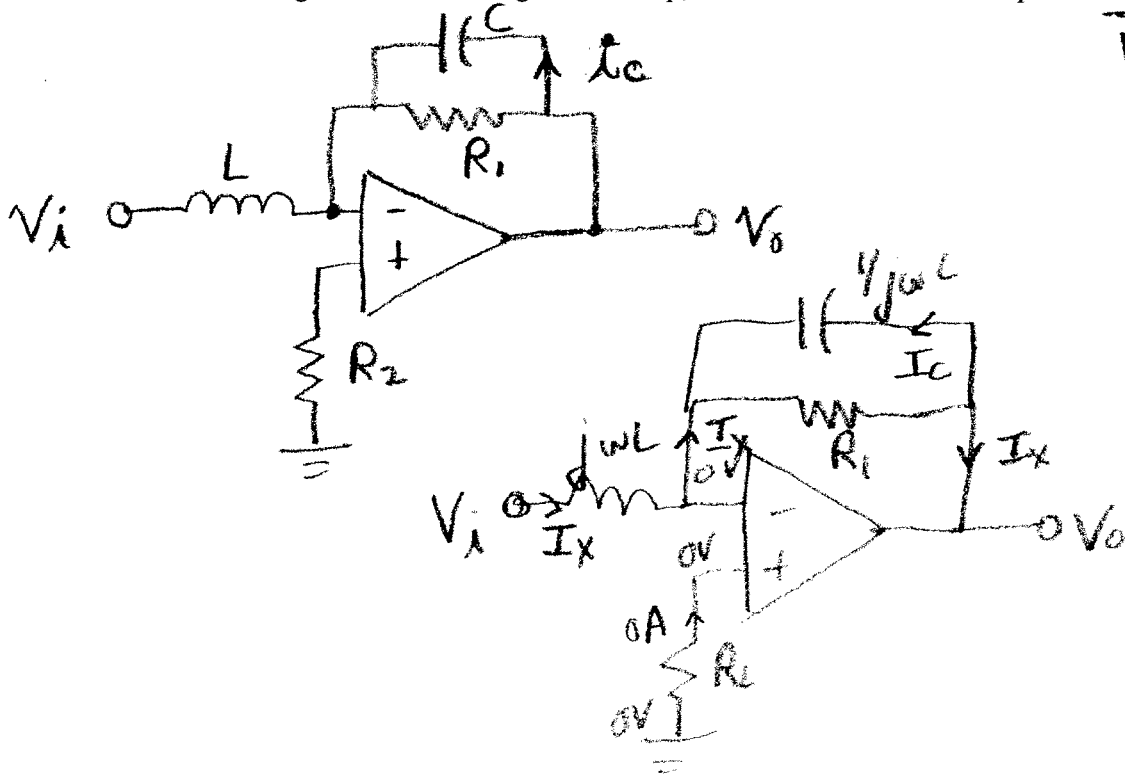


$$-V_i + I_X j\omega L + 0 = 0 \Rightarrow I_X = \frac{V_i}{j\omega L}$$

$$I_C = -I_X \frac{R_1}{R_1 + \frac{1}{j\omega C}}$$

$$1 \quad 9. \quad \frac{V_2}{V_1} = \frac{-1}{4}$$

$$4 \quad 10. \quad \frac{-2A}{3} \frac{1}{\sqrt{(\omega L)^2 + \left(\frac{R}{3A}\right)^2}} \cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R/(3A)}\right)\right) A$$


1 11. infinite input resistance

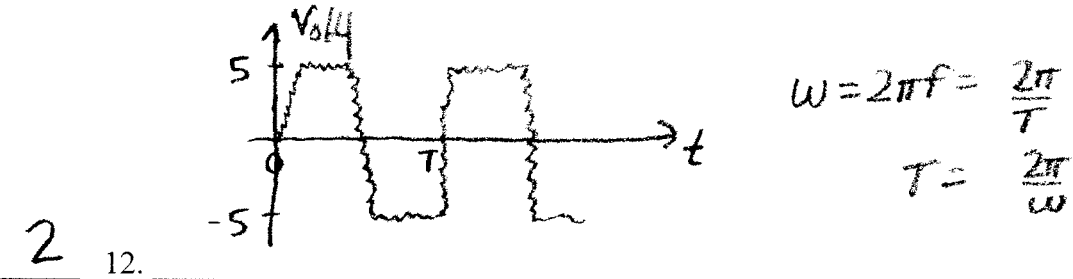


$$4 \quad 13. \quad \frac{-R_1}{j\omega L (R_1 + \frac{1}{j\omega C})} = \frac{-R_1 C}{L(j\omega C R_1 + 1)}$$

11. Name one characteristic of an ideal op-amp.

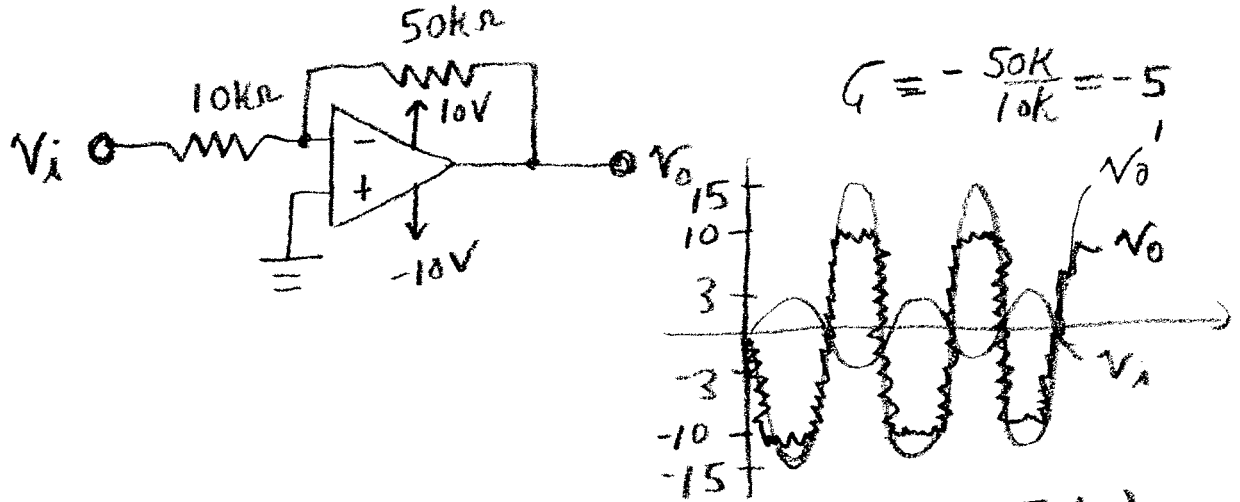12. The input signal for the following ideal op-amp circuit is $v_i(t) = 3 \sin(\omega t)$ V. Sketch the output signal, clearly indicating the maximum and minimum values of the amplitude.



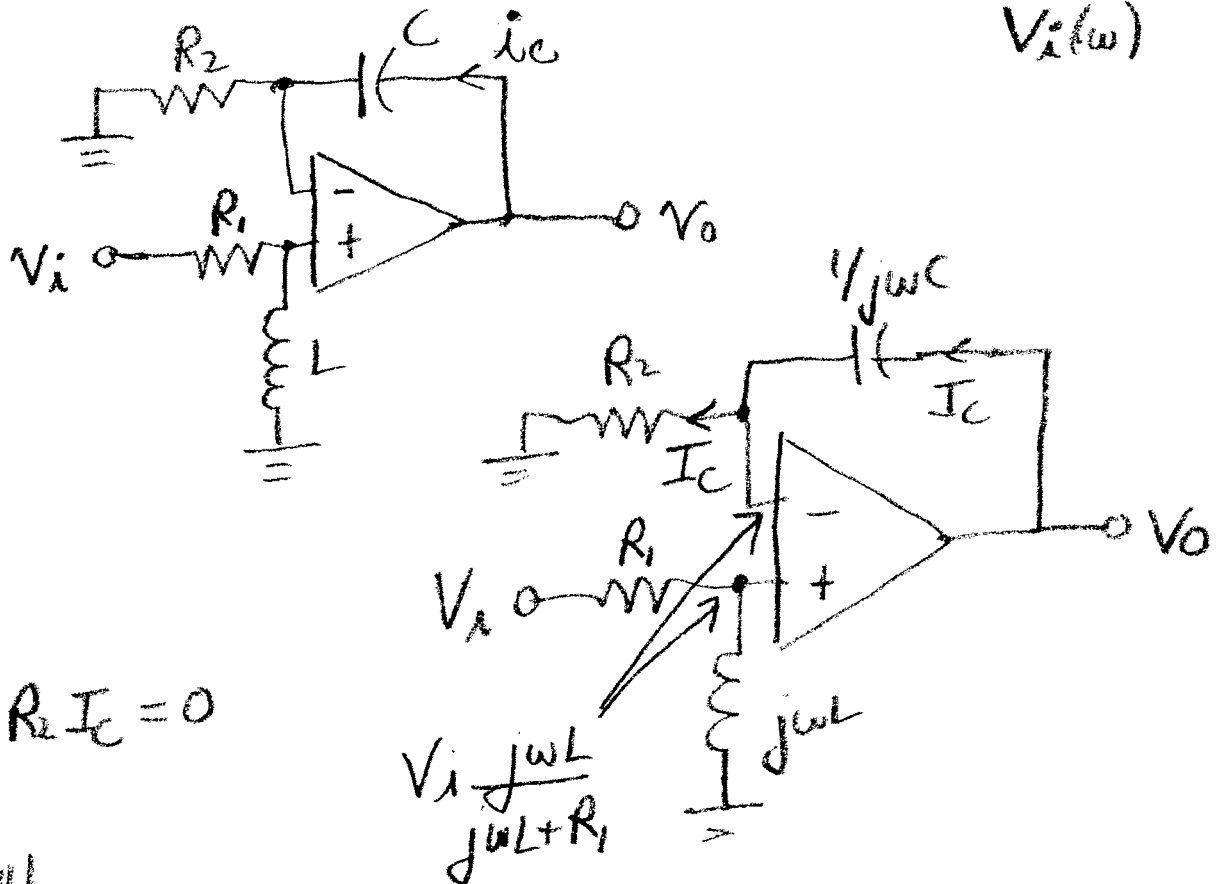13. For the following circuit involving an ideal op-amp, determine the relationship $\frac{I_C(\omega)}{V_i(\omega)}$




$$-\frac{V_i j\omega L}{j\omega L + R_1} + R_2 I_C = 0$$

$$\frac{I_C}{V_i} = \frac{j\omega L}{R_2(j\omega L + R_1)}$$

1 9. $\frac{v_2}{v_1} = \frac{7}{3}$

4 10. $\left(\frac{3}{2} A \sqrt{\frac{(-1)^2}{(\omega C)^2} + \left(\frac{R}{(4/3)^2} \right)^2} \right) \cos\left(\omega t - \tan^{-1} \frac{1/\omega C}{R/(4/3)^2}\right) A$

1 11. infinite open-loop gain

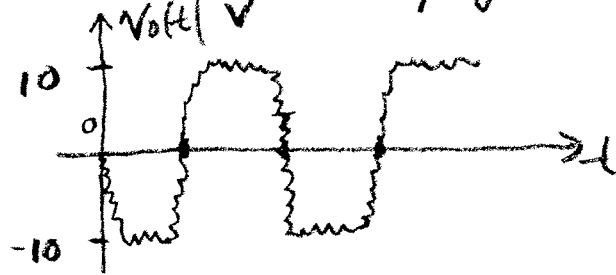


$$\omega = 2\pi f = \frac{2\pi}{T}$$

$$T = \frac{2\pi}{\omega}$$


2 12.

4 13. $\frac{j\omega L}{R_2(j\omega L + R_1)}$

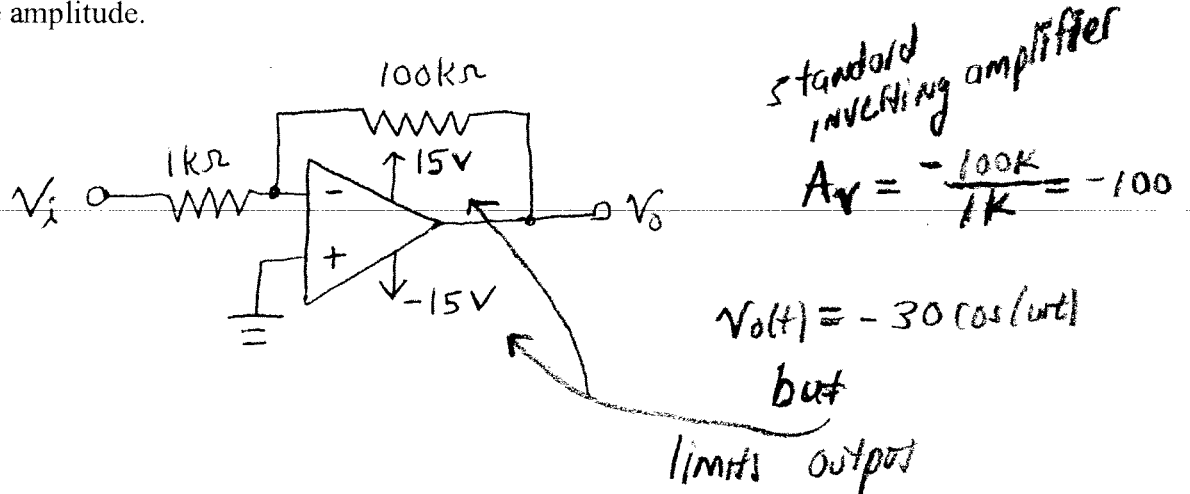11. Name one characteristic of an ideal op-amp.
12. The input signal for the following ideal op-amp circuit is $v_i(t) = 0.3 \cos(\omega t)$ V. Sketch the output signal, clearly indicating the maximum and minimum values of the amplitude.



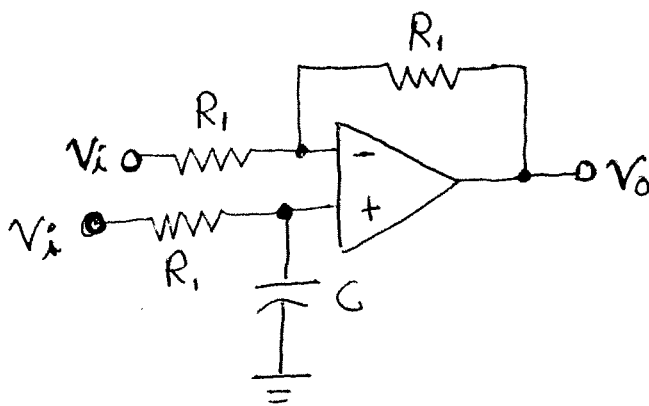13. For the following circuit involving an ideal-op, determine the relationship $\frac{V_o(\omega)}{V_i(\omega)}$




$$\begin{aligned}
 V_o &= V_i \times \frac{1}{\frac{j\omega C}{j\omega C + R_i}} \times \left(1 + \frac{R_i}{R_i}\right) + V_i \times \left(-\frac{R_i}{R_i}\right) \\
 &= \frac{2V_i}{1 + j\omega RC} - V_i = \frac{2V_i - V_i - j\omega RC V_i}{1 + j\omega RC} \\
 &= \frac{V_i(1 - j\omega RC)}{1 + j\omega RC}
 \end{aligned}$$

1 9. $\frac{V_2}{V_1} = -\frac{9}{4}$


3 10. $-\frac{3}{8} \frac{A\omega C}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + 90^\circ - \tan^{-1}(\omega RC))$

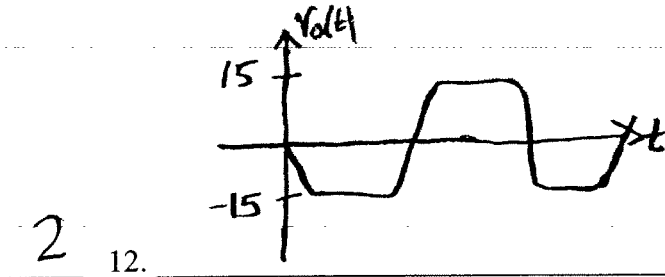1 11. infinite input resistance, zero input current, zero input Δ , ...



4 13. $\frac{V_o}{V_i} = \frac{1 - j\omega RC}{1 + j\omega RC} = \frac{2}{1 + j\omega RC} - 1$

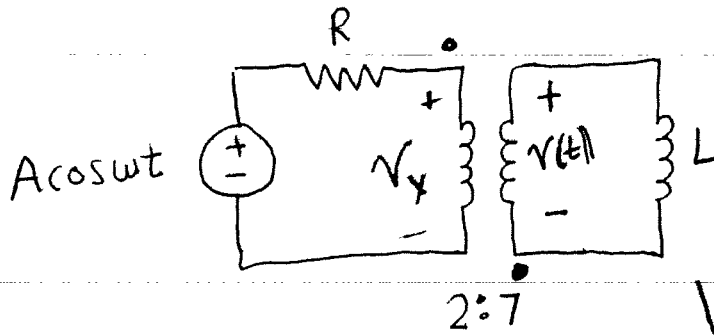16. For the following circuit involving an ideal transformer, determine $v(t)$ (in the time domain).




$$\frac{v}{v_x} = -\frac{7}{2}$$

$$v = -\frac{7}{2} v_x$$

$$v_x = A \times \frac{j\omega L / (\frac{7}{2})^2}{[j\omega L / (\frac{7}{2})^2] + R}$$

$$v_x(t) = \frac{A \times \frac{4}{49} \omega L}{\sqrt{R^2 + \left(\frac{\omega L 4}{49}\right)^2}} \left(\cos(\omega t + 90^\circ - \tan^{-1} \frac{\omega L 4}{49 R}) \right)$$

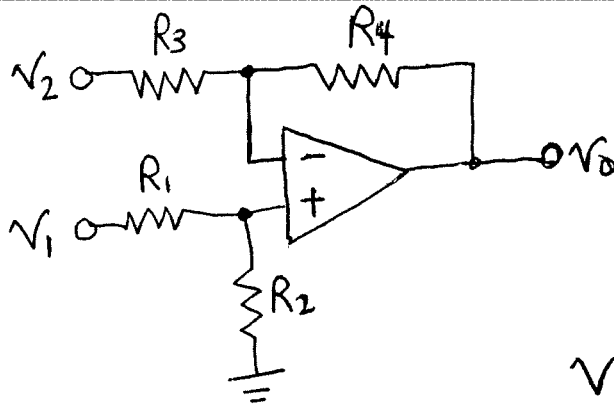17. For the following circuit involving an ideal op, determine the relationship for v_o as a function of v_1 , v_2 , and the R 's



$$v_o = v_1 \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3} \right) - v_2 \left(\frac{R_4}{R_3} \right)$$


$$2 \quad 15. \quad \frac{R}{\sqrt{1 + (\omega RC)^2} \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$2 \quad 16. \quad \frac{-7}{2} \frac{A \frac{4}{49} \omega L}{\sqrt{R^2 + \left(\frac{4\omega L}{49}\right)^2}} \cos\left(\omega t + 90^\circ - \tan^{-1} \frac{\omega L}{R}\right) V$$

$$3 \quad 17. \quad v_0 = v_1 \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3}\right) - v_2 \left(\frac{R_4}{R_3}\right)$$


11. Name one characteristic of an ideal op-amp.

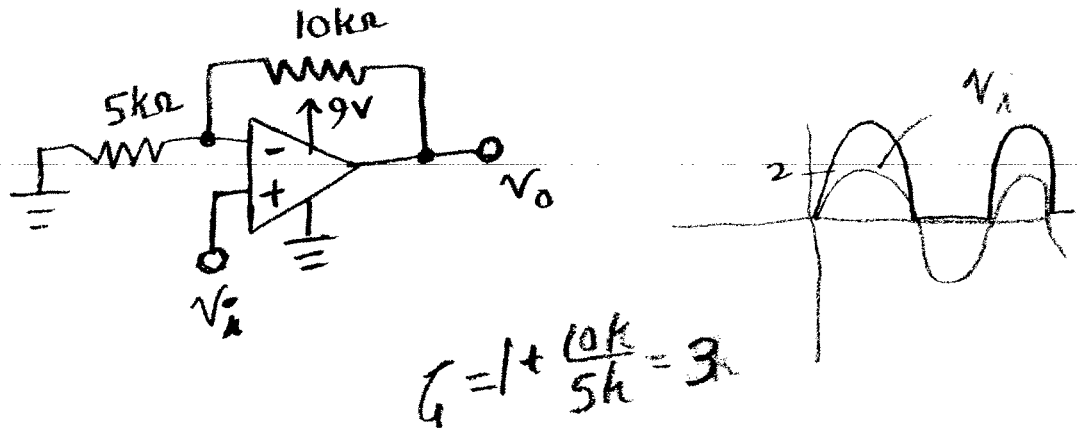12. The input signal for the following ideal op-amp circuit is $v_i(t) = 2 \sin(\omega t)$ V. Sketch the output signal, clearly indicating the maximum and minimum values of the amplitude.



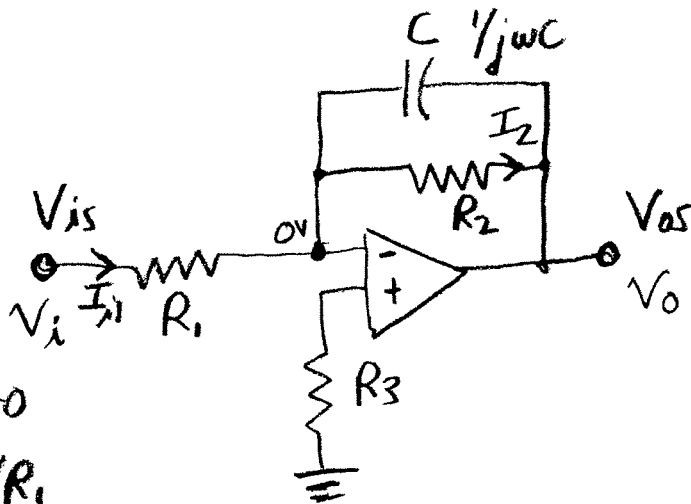13. For the following circuit involving an ideal op, determine the relationship

$$\frac{I_{25}(\omega)}{V_{i5}(\omega)}$$



$$-V_{i5} + R_1 I_{i5} = 0$$

$$I_{i5} = V_{i5} / R_1$$

$$0 + \left(\frac{1}{j\omega C} \parallel R_2 \right) I_{i5} + V_{o5} = 0$$

$$V_{o5} = - \frac{V_{i5}}{R_1} \left(\frac{1}{j\omega C} \parallel R_2 \right)$$

$$I_{25} R_2 + V_{o5} = 0$$


$$\frac{I_{25}}{R_2} = - \frac{V_{o5}}{R_2} = \frac{V_{i5}}{R_1 R_2} \left(\frac{1}{j\omega C} \parallel R_2 \right) = \frac{V_{i5}}{R_1 R_2} \frac{\frac{1}{j\omega C} R_2}{\frac{1}{j\omega C} + R_2}$$

$$= \frac{1}{R_1} \frac{1}{1 + j\omega C R_2}$$

1 9. $v_2/v_1 = -5/6$

3 10. $v(t) = \frac{2}{9} \frac{A}{\omega C} \cos(\omega t - 90^\circ) \text{ V}$


1 11. $V_- - V_+ = 0$ with feedback

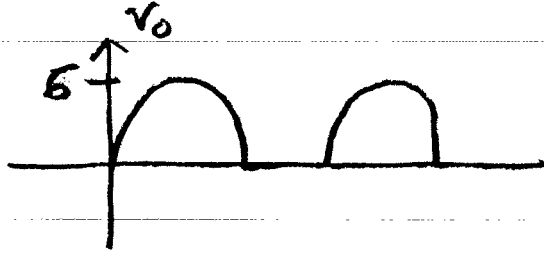

2 12.

5 13. $\frac{I_2}{V_i} = \frac{1}{R_1 R_2} \left(\frac{1}{j\omega C} \parallel R_2 \right) = \frac{1}{R_1} \frac{1}{1 + j\omega C R_2}$

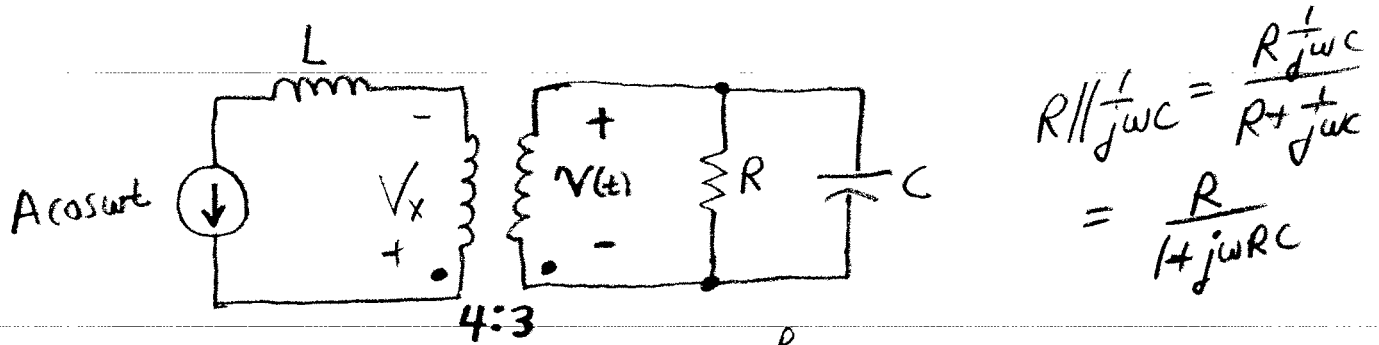16. For the following circuit involving an ideal transformer, determine $v(t)$ (in the time domain).



$$R \parallel \frac{1}{j\omega C} = \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$


$$V_x = (A L \theta) \frac{R}{(3/4)^2 (1 + j\omega RC)}$$

$$V/V_x = -3/4$$

$$V = -\frac{3}{4} V_x = -A \frac{R}{1 + j\omega RC} \left(\frac{4}{3}\right)$$

17. For the following circuit involving an ideal op-amp, determine the relationship

$$\frac{V_o(\omega)}{V_i(\omega)}$$

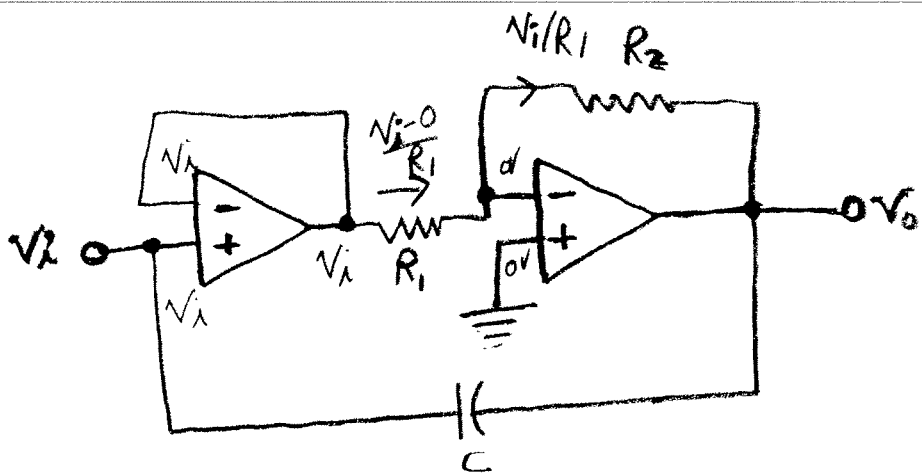

$$0 + \frac{V_i R_2}{R_1} + V_o = 0$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

$$3 \quad 15. \quad \frac{WLR}{\sqrt{R^2 + (\omega L)^2}} \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \cdot \frac{WLR}{\sqrt{\left(R^2 + \frac{L}{C}\right)^2 + \left(WLR - \frac{R}{\omega C}\right)^2}}$$

$\frac{R\omega L}{\sqrt{R^2 + (\omega C)^2}}$

$$5 \quad 16. \quad -\frac{4R}{3} \frac{1}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t - \tan^{-1} \omega RC)$$

$$3 \quad 17. \quad \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$