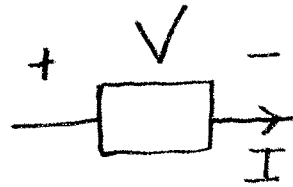


17. Determine the real power absorbed by the given "box" element. Provide the units.



$$V = 5 \angle 120^\circ \text{ V}_{\text{rms}}$$

$$I = 3 \angle 60^\circ \text{ A}_{\text{rms}}$$

$$S = VI^* = (5 \angle 120^\circ)(3 \angle -60^\circ) = 15 \angle 60^\circ$$

18. Determine the reactive power absorbed by the given "box" element. Provide the units.




$$V = 2 + j3 \text{ V}_{\text{rms}}$$

$$I = -3 + j5 \text{ A}_{\text{rms}}$$

$$S = -VI^* = -(2 + j3)(-3 - j5) = -[-6 - j10 - j9 + 15]$$

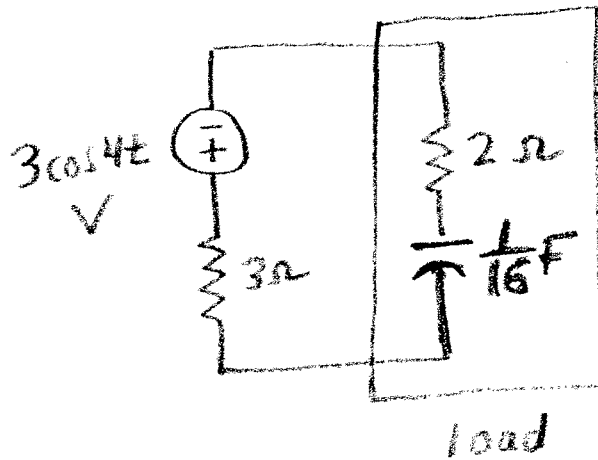19. For the given circuit, determine the complex power absorbed by the load and place it in the rectangular form $P + jQ$. Provide the units.




$$\frac{1}{j4 \frac{1}{16}} = \frac{1}{j\frac{1}{4}} = -j4$$

when rms not used


$$S = \frac{1}{2} VI^* = \frac{1}{2} 3 \frac{2 - j4}{3 + 2 - j4} \left(\frac{3}{3 + 2 - j4} \right)^*$$

$$= \frac{3}{2} \frac{2 - j4}{5 - j4} \frac{3}{5 + j4} = \frac{9}{2} \frac{2 - j4}{25 + 16}$$

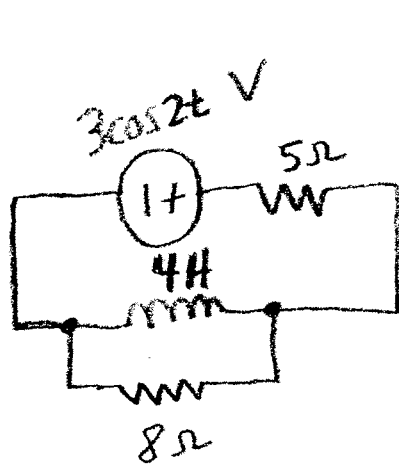20. For the given circuit, determine the power factor seen by the source. It is not necessary to evaluate the trigonometric functions, but no j 's should be present in the final answer.


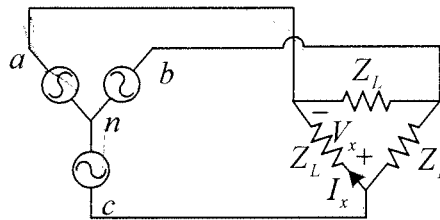
$$\begin{aligned}
 j2/4 &= j8 \\
 Z &= 5 + (j8 // 8) \\
 &= 5 + \frac{j64}{8+j8} \\
 &= \frac{40 + j40 + j64}{8+j8} \\
 &= \frac{40 + j104}{8+j8} \\
 &= \frac{40 + j104}{8+j8} \cdot \frac{8-j8}{8-j8} \dots
 \end{aligned}$$



21. For the balanced Y- Δ configuration shown above $\omega = 4$ rad/s, $V_{an} = 5\angle -240^\circ$ V rms, $V_{bn} = 5\angle -120^\circ$ V rms, $V_{cn} = 5\angle 0^\circ$ V rms, and each load, Z_L , consists of a $5\ \Omega$ resistor in series with a $1/4$ F capacitor, determine (using the concepts discussed in class, i.e., phasor diagrams, and simplify the expressions in the same manner as presented in class) the current I_x in the frequency domain

$$\begin{aligned}
 V_x + 5\angle -240^\circ - 5\angle 0^\circ &= 0 \\
 V_x &= 5\angle 0^\circ - 5\angle -240^\circ \\
 &= 5\sqrt{3}\angle -30^\circ
 \end{aligned}$$

$$\begin{aligned}
 Z_L &= 5 - \frac{j}{4(1/4)} = 5 - j \\
 I_x &= \frac{5\sqrt{3}\angle -30^\circ}{5 - j}
 \end{aligned}$$

$$1 \quad 17. \quad 15 \cos 60^\circ \text{ W}$$


$$1' \quad 18. \quad 19 \text{ VAR}$$

$$4 \quad 19. \quad \frac{9}{25+16} - j \frac{18}{25+16} \text{ VA}$$


$$2 \quad 20. \quad \cos \left[\tan^{-1} \frac{40}{40} - \tan^{-1} \frac{8}{8} \right]$$

$$6 \quad 21. \quad \frac{5\sqrt{3}}{\sqrt{5^2+1^2}} \angle -30^\circ - \tan^{-1} \frac{1}{5}$$

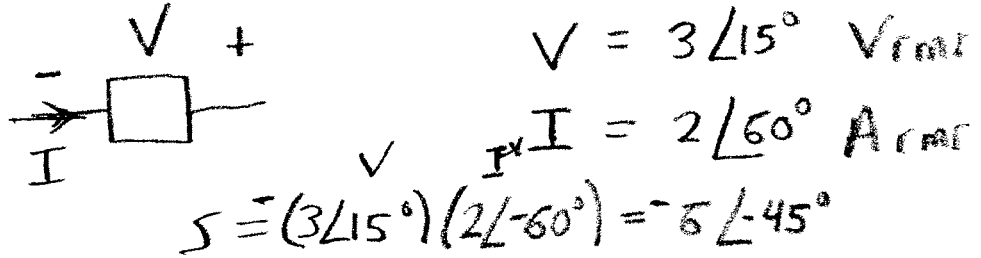
17. Determine the real power absorbed by the given "box" element. Provide the units.



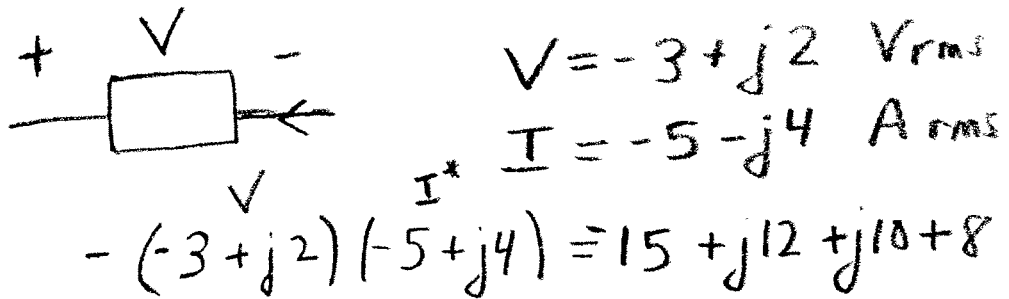18. Determine the reactive power absorbed by the given "box" element. Provide the units.



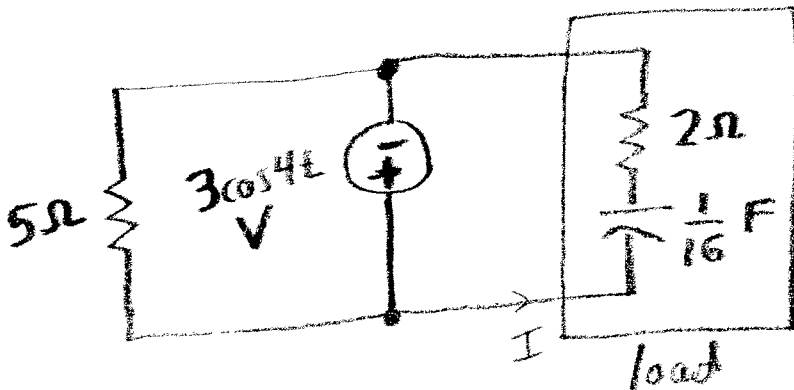19. For the given circuit, determine the complex power absorbed by the load and place it in the rectangular form $P + jQ$. Provide the units.




$\frac{1}{j4 + 8} = \frac{1}{j4} = -j4$

$S = \frac{1}{2} V I^*$
when rms
not used

$S = \frac{1}{2} 3 \angle 0^\circ \left(\frac{3 \angle 0^\circ}{2 - j4} \right)^*$
 $= \frac{3 \angle 0^\circ}{2} \frac{3 \angle 0^\circ}{2 + j4}$
 $= \frac{1}{2} \frac{9}{2 + j4} \frac{2 - j4}{2 - j4} = \frac{1}{2} \frac{18 - j36}{2^2 + 4^2}$

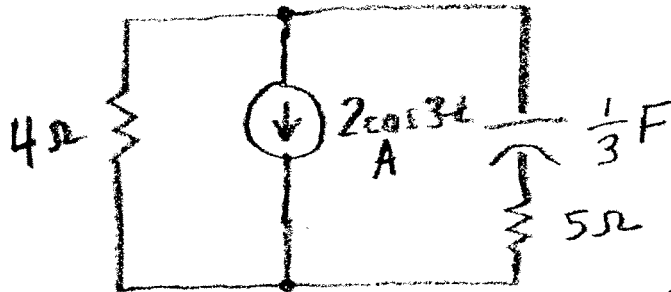20. For the given circuit, determine the power factor seen by the source. It is not necessary to evaluate the trigonometric functions, but no j 's should be present in the final answer.


$$\frac{1}{j^{3\frac{1}{2}}} = \frac{1}{j^{\frac{3}{2}}} = -j$$



$$Z = 4 \parallel (5 - j)$$

$$= \frac{20 - 4j}{9 - j}$$
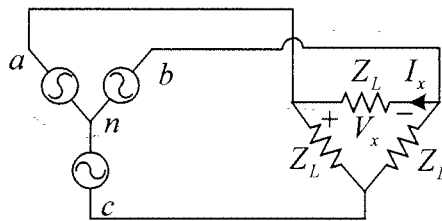
$$\angle Z = \tan^{-1} \frac{-4}{20} - \tan^{-1} \frac{-1}{9}$$



21. For the balanced Y- Δ configuration shown above $\omega = 4$ rad/s, $V_{an} = 5\angle 120^\circ$ V rms, $V_{bn} = 5\angle -120^\circ$ V rms, $V_{cn} = 5\angle 0^\circ$ V rms, and each load, Z_L , consists of a 3Ω resistor in series with a $1/2$ F capacitor, determine (using the concepts discussed in class, i.e., phasor diagrams, and simplify the expressions in the same manner as presented in class) the current I_x in the frequency domain


$$Z_L = 3 + \frac{1}{j4(\frac{1}{2})} = 3 - \frac{j}{2}$$

$$+V_x + 5\angle -120^\circ - 5\angle 120^\circ = 0$$

$$V_x = 5\angle 120^\circ - 5\angle -120^\circ$$

$$= 5\sqrt{3} \angle 90^\circ$$
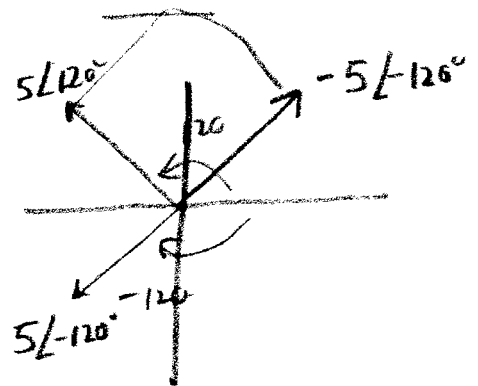
$$\underline{I}_x = \frac{-5\sqrt{3} \angle 90^\circ}{3 - \frac{j}{2}}$$



$$1 \quad 17. \quad -6 \cos(45^\circ) \text{ W}$$


$$1 \quad 18. \quad +22 \text{ VAR}$$

$$4 \quad 19. \quad \frac{9}{2^2+4^2} - j \frac{18}{2^2+4^2} \text{ VA}$$

$$2 \quad 20. \quad \cos \left[\tan^{-1} \frac{-4}{23} - \tan^{-1} \frac{-1}{9} \right]$$

$$6 \quad 21. \quad \frac{-5\sqrt{3}}{3^2 + \left(\frac{1}{2}\right)^2} \angle 90^\circ - \tan^{-1} \frac{1}{3} \text{ A rms}$$

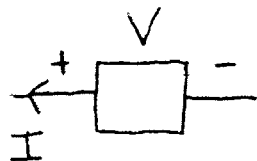17. Determine the real power absorbed by the given "box" element. Provide the units.




$$V = 4 \angle 20^\circ \text{ V}_{\text{rms}}$$

$$I = 3 \angle 15^\circ \text{ A}_{\text{rms}}$$

$$S = (4 \angle 20^\circ)(3 \angle -15^\circ) = -12 \angle 5^\circ = -12 \cos 5^\circ + j 12 \sin 5^\circ$$

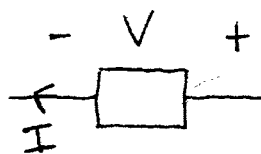18. Determine the reactive power absorbed by the given "box" element. Provide the units.




$$V = 3 - j8 \text{ V}_{\text{rms}}$$

$$I = 2 + j9 \text{ A}_{\text{rms}}$$

$$S = (3 - j8)(2 - j9) = 6 - 72 - j(16 + 27)$$

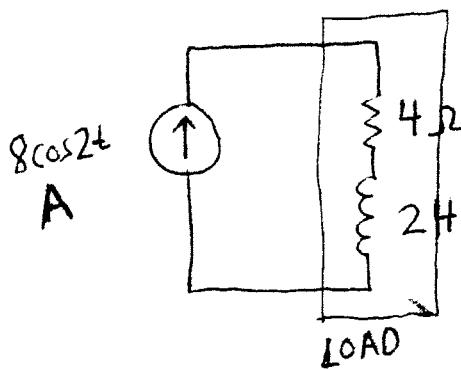19. For the given circuit, determine the complex power absorbed by the load. Provide the units.




$$V_L = (8 \angle 0^\circ)(4 + j4)$$


$$S = \frac{1}{2} (8 \angle 0^\circ)(4 + j4)(8 \angle 0^\circ)^*$$

$$= 32(4 + j4)$$

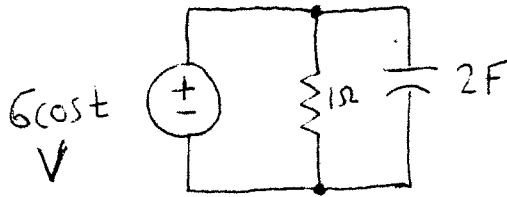20. For the given circuit, determine the power factor seen by the source. It is not necessary to evaluate the trigonometric functions, but no j 's should be present in the final answer.



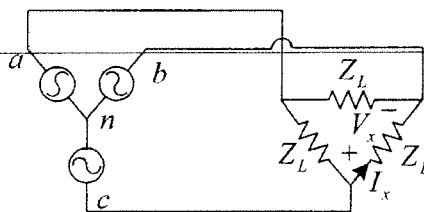
$$\begin{aligned}
 Z_L &= 1 \parallel \frac{1}{j2} \\
 &= \frac{1}{\frac{1}{1} + \frac{1}{j2}} = \frac{1}{1 + j2} \\
 &= \frac{1 \angle 0^\circ}{\sqrt{1+2^2} \angle \tan^{-1} \frac{2}{1}} \\
 &= \frac{1}{\sqrt{1+2^2}} \angle -\tan^{-1} \frac{2}{1}
 \end{aligned}$$



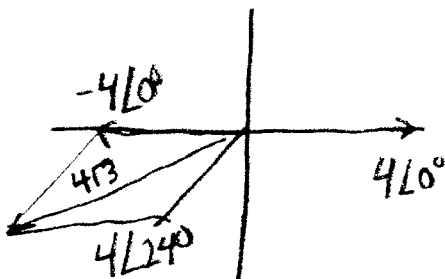21. For the balanced Y- Δ configuration shown above $\omega = 3$ rad/s, $V_{an} = 4 \angle 120^\circ$ V rms, $V_{bn} = 4 \angle 0^\circ$ V rms, $V_{cn} = 4 \angle 240^\circ$ V rms, and each load, Z_L , consists of a 5Ω resistor in series with a $1/6$ F capacitor, determine (using the concepts discussed in class, i.e., phasor diagrams, and simplify the expressions in the same manner as presented in class) the voltage V_x in the frequency domain

$$\begin{aligned}
 -V_x + 4 \angle 240^\circ - 4 \angle 0^\circ &= 0 \\
 V_x &= 4 \angle 240^\circ - 4 \angle 0^\circ
 \end{aligned}$$



1 17. $-12 \cos 5^\circ \text{ W}$

1 18. $-(16+27) \text{ VAR}$


1 19. $32(4+j4) \text{ VA}$

2 20. $\cos \left[-\tan^{-1} \frac{2}{1} \right]$


2 21. $4\sqrt{3} / 180+30^\circ = 4\sqrt{3} / \underline{240-30^\circ} \text{ V}_{\text{rms}}$

$$S = \frac{1}{2} \frac{j24}{5+j8} \times \frac{3}{5-j8} = \frac{j36}{5^2+8^2}$$

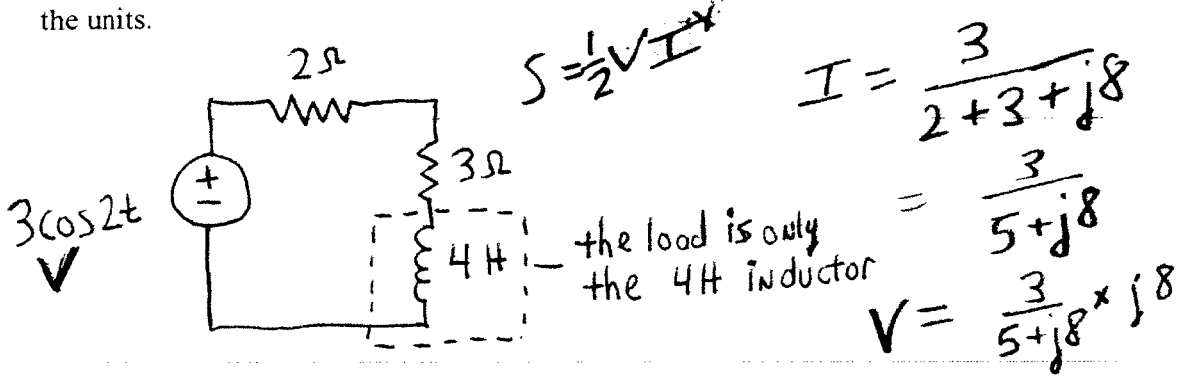10. For the given circuit, determine the complex power absorbed by the load. Provide the units.



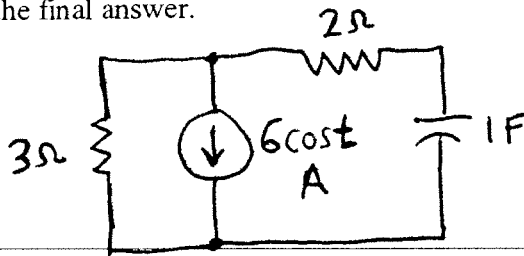
11. For the given circuit, determine the power factor seen by the source. It is not necessary to evaluate the trigonometric functions, but no j 's should be present in the final answer.




$$3 \parallel (2 + \frac{1}{j}) = 3 \parallel (2 - j)$$

$$\frac{3(2-j)}{3+2-j} = \frac{3(2-j)}{5-j}$$
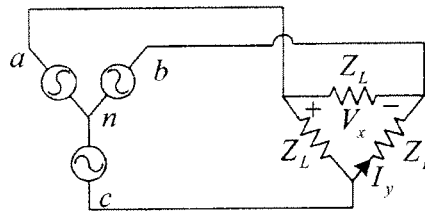
$$= \frac{3\sqrt{2^2+1^2} \angle \tan^{-1} \frac{-1}{2}}{\sqrt{5^2+1^2} \angle \tan^{-1} \frac{-1}{5}}$$



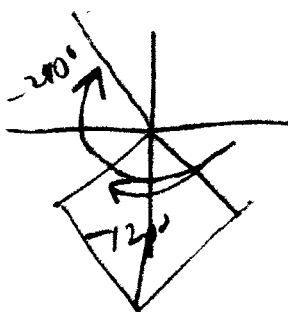12. For the balanced Y- Δ configuration shown above $\omega = 2$ rad/s, $V_{an} = 4\angle -120^\circ$ V rms, $V_{bn} = 4\angle -240^\circ$ V rms, $V_{cn} = 4\angle 0^\circ$ V rms, and each load, Z_L , consists of a $6\ \Omega$ resistor in series with a $1/2$ F capacitor, determine (using the concepts discussed in class, i.e., phasor diagrams, and simplify the expressions in the same manner as presented in class) the voltage V_x in the frequency domain



$$+V_x + V_{bn} - V_{an} = 0$$

$$V_x = V_{an} - V_{bn}$$

$$= 4\angle -120^\circ - 4\angle -240^\circ$$

$$= 4\sqrt{3} \angle -90^\circ$$

$$2 \quad 7. \quad \frac{A}{R+j\omega L} + B \times \frac{R}{R+j\omega L}$$

$$V_3 - 0 = -A, \quad \frac{V_4 - 0}{j\omega L} + \frac{V_4 - V_3}{R_b} = 0$$

$$2 \quad 8. \quad \frac{V_2 - V_3}{\frac{1}{j\omega C}} - B = 0, \quad \frac{V_1 - 0}{R_a} + B = 0$$

$$I_1 = -B$$

$$1 \quad 9. \quad R_b I_2 + j\omega L (I_2 + I_1) + \frac{1}{j\omega C} I_2 - A = 0$$

$$2 \quad 10. \quad S = \frac{j36}{5^2 + 8^2} \text{ VA (since purely reactive, VAR)}$$


$$2 \quad 11. \quad \cos \left[\tan^{-1} \left(\frac{1}{2} \right) - \tan^{-1} \left(\frac{1}{5} \right) \right]$$

$$1 \quad 12. \quad 4\sqrt{3} \angle -90^\circ \text{ V}_{\text{rms}}$$

$$1 \quad 13. \quad \text{BPF}$$

$$1 \quad 14. \quad \frac{R_b \parallel \frac{1}{j\omega C}}{(R_b \parallel \frac{1}{j\omega C}) + R_a + j\omega L}$$

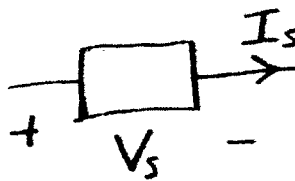17. Determine the real power absorbed by the given "box" element. Provide the units.




$$V_s = 3 + j8 \quad V_{rms}$$

$$I_s = 4 \angle 18^\circ \quad A_{rms}$$

$$(3 + j8)(4 \angle -18^\circ)$$

$$= (3 + j8)(4 \cos 18^\circ - j4 \sin 18^\circ)$$

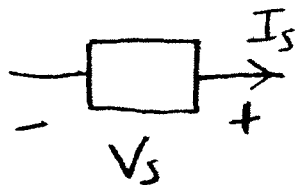18. Determine the reactive power absorbed by the given "box" element. Provide the units.




$$V_s = 2 \angle 126^\circ \text{ V}$$

$$I_s = 3 \angle 15^\circ \text{ A}$$

$$-\frac{1}{2}(2 \angle 126^\circ)(3 \angle -15^\circ)$$

$$= -\frac{3}{2} \angle 120 - 15^\circ$$

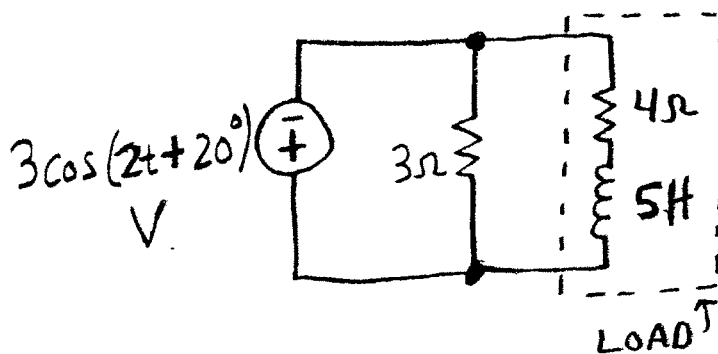19. For the given circuit, determine the complex power absorbed by the load and place it in the rectangular form $P + jQ$. Provide the units.





$$S = \frac{1}{2} V I^* = (3 \angle 20^\circ) \left(\frac{3 \angle 20^\circ}{4 + j10} \right)^*$$

$$= \frac{1}{2} (3 \angle 20^\circ) \left(\frac{3 \angle -20^\circ}{4 - j10} \right) = \frac{1}{2} \frac{9}{4 - j10} \frac{4 + j10}{4 + j10}$$

$$= \frac{1}{2} \frac{9}{24^2 + 10^2} (4 + j10)$$

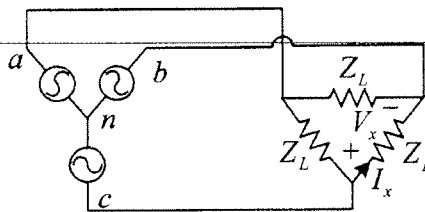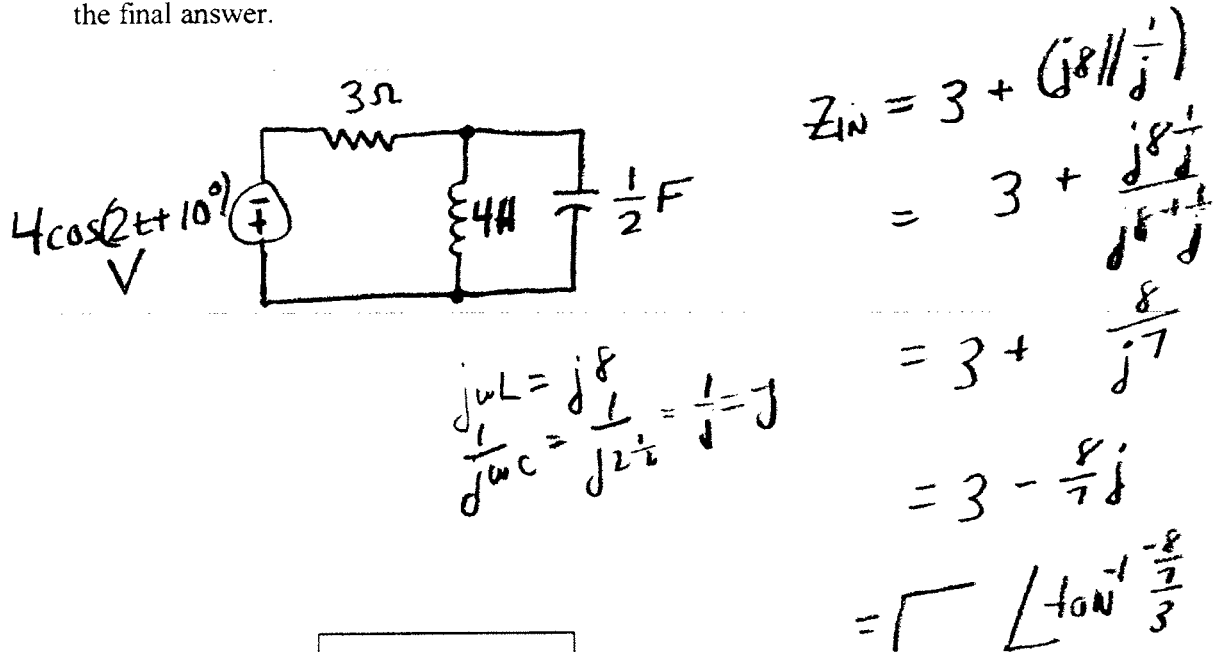20. For the given circuit, determine the power factor seen by the source. It is not necessary to evaluate the trigonometric functions, but no j 's should be present in the final answer.



21. For the balanced Y- Δ configuration shown above $\omega = 4$ rad/s, $V_{an} = 5 \angle -120^\circ$ V rms, $V_{bn} = 5 \angle 120^\circ$ V rms, $V_{cn} = 5 \angle 0^\circ$ V rms, and each load, Z_L , consists of a 5Ω resistor in series with a 2 H inductor, determine (using the concepts discussed in class, i.e., phasor diagrams, and simplify the expressions in the same manner as presented in class) the current I_x in the frequency domain

$$+V_x + 5 \angle 120^\circ - 5 \angle 0^\circ = 0$$

$$V_x = 5 \angle 0^\circ - 5 \angle 120^\circ$$

$$= 5\sqrt{3} \angle -30^\circ$$

$$I_x = \frac{5\sqrt{3} \angle -30^\circ}{5 + j8}$$

$$2 \quad 17. \quad 12 \cos 18^\circ + 32 \sin 18^\circ \quad \text{W}$$


$$2 \quad 18. \quad -\frac{1}{2} 6 \sin (120 - 15^\circ) \quad \text{VAR}$$

$$2 \quad 19. \quad \frac{1 \times 9}{2 \times 4 \times 10^2} (4 + j10) \quad \text{VA}$$


$$2 \quad 20. \quad \cos \left(\tan^{-1} \frac{8}{3} \right)$$

$$3 \quad 21. \quad \frac{5\sqrt{3}}{\sqrt{5^2 + 8^2}} \angle -30^\circ - \tan^{-1} \frac{8}{5} \quad \text{A rms}$$

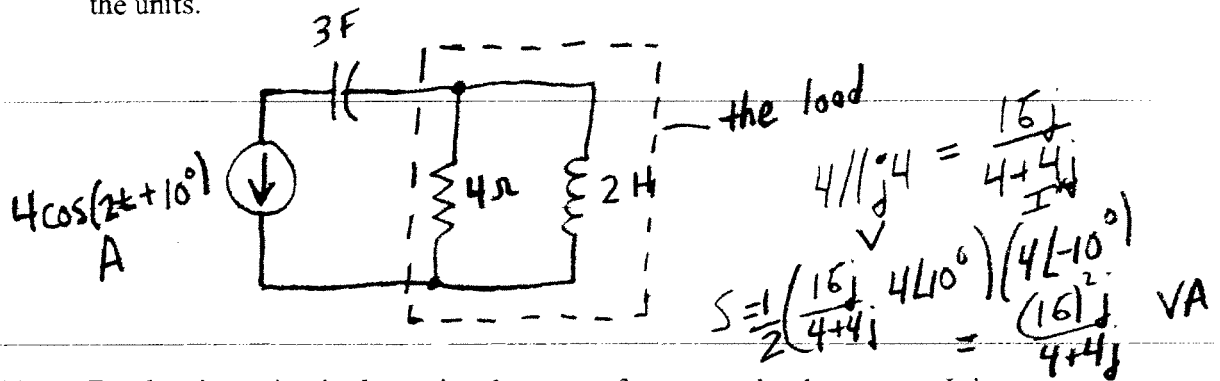10. For the given circuit, determine the complex power absorbed by the load. Provide the units.



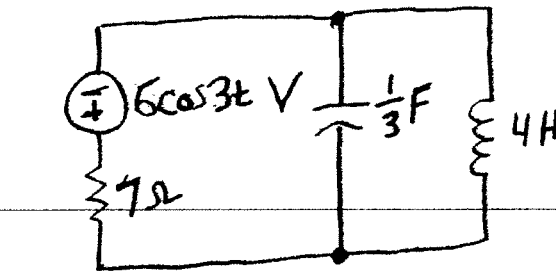11. For the given circuit, determine the power factor seen by the source. It is not necessary to evaluate the trigonometric functions, but no j 's should be present in the final answer.



$$\frac{1}{j33} = \frac{1}{j}$$

$$= \frac{256 \angle 90^\circ}{2\sqrt{32} \angle 100^\circ}$$


$$-j \parallel j12 + 7$$

$$\frac{-j \cdot j12}{j11} + 7$$

$$\frac{12}{j11} + 7$$

$$-\frac{12j}{11} + 7$$

$$= \frac{-12j + 77}{11}$$

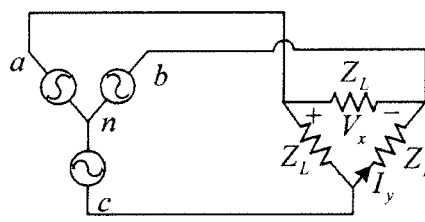

12. For the balanced Y- Δ configuration shown above $\omega = 3 \text{ rad/s}$, $V_{an} = 2 \angle 120^\circ \text{ V rms}$, $V_{bn} = 2 \angle 240^\circ \text{ V rms}$, $V_{cn} = 2 \angle 0^\circ \text{ V rms}$, and each load, Z_L , consists of a 2Ω resistor in parallel with a $1/6 \text{ F}$ capacitor, determine (using the concepts discussed in class, i.e., phasor diagrams, and simplify the expressions in the same manner as presented in class) the voltage V_x in the frequency domain

$$+V_x + 2 \angle 240^\circ - 2 \angle 120^\circ = 0$$

$$V_x = 2 \angle 120^\circ - 2 \angle 240^\circ$$

4 7.
$$-B\angle 0^\circ \times \frac{1/j\omega C}{R + \frac{1}{j\omega C}} + \frac{A\angle 0^\circ}{R + \frac{1}{j\omega C}}$$

(1) $V_1 - V_2 = A\angle 0^\circ$

(3) $\frac{V_2 - V_3}{R_a} + \frac{V_1 - 0}{1/j\omega C} = 0$

(2) $\frac{V_3 - 0}{j\omega L} + \frac{V_3 - 0}{R_b} - B\angle 0^\circ + \frac{V_5 - V_2}{R_a} = 0$

3

(1) $R_a I_1 - A\angle 0^\circ + I_1 \frac{1}{j\omega C} + \underset{\text{OR}}{(I_2 + I_3)R_b} = 0$

(2) $I_1 - I_2 = B\angle 0^\circ$

$-I_3 j\omega L$

(3) $I_3 j\omega L + (I_2 + I_3)R_b = 0$

3

4 10. $\frac{256}{2\sqrt{32}} \angle 45^\circ = \frac{256}{2\sqrt{32}} \left(\frac{1}{\sqrt{2}} + \frac{j}{\sqrt{2}} \right) \text{ VA}$, $\cos 45^\circ = \frac{1}{\sqrt{2}}$, $\sin 45^\circ = \frac{1}{\sqrt{2}}$

$\frac{\sqrt{32}\sqrt{2}}{\sqrt{86}\sqrt{2}} = 4 \cdot 2 = 8$

3

11. $\cos\left(\tan^{-1} \frac{1 - 12/11}{7}\right)$

2

12. $2\sqrt{3} \angle 90^\circ \text{ V rms}$

1

13. L'PF

2

14. $\frac{j\omega L_2}{j\omega L_2 + (R // \frac{1}{j\omega C})}$