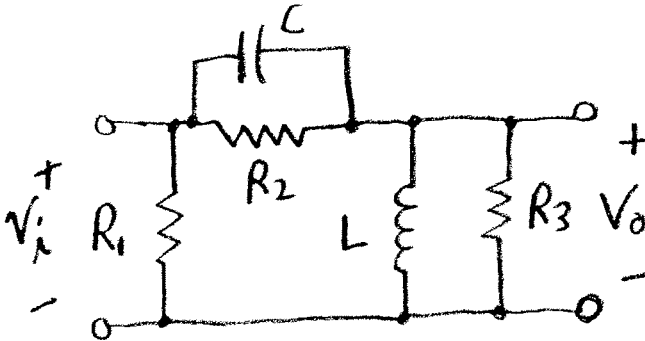


4. Determine the transfer function $H(\omega) = V_o(\omega)/V_i(\omega)$ for the given using voltage division, current division, and/or Ohm's law. Do not simplify the expression. If needed, the symbol for two elements in parallel (e.g., $R_s \parallel R_L$) may be used.



5. Determine the magnitude of the given transfer function as done in class.


$$H(\omega) = \frac{\frac{1}{j\omega C}}{R + (j\omega L \parallel R)}$$

OR $\frac{\frac{L}{C} - \frac{jR}{\omega C}}{R^2 + j2\omega LR}$


$$\frac{\frac{1}{j\omega C}}{R + \frac{j\omega LR}{j\omega L + R}} = \frac{\frac{j\omega L + R}{j\omega C}}{j\omega LR + R^2 + j\omega LR}$$

$$= \frac{j\omega L + R}{- \omega^2 LC R + j\omega C R^2 - \omega^2 LC R}$$

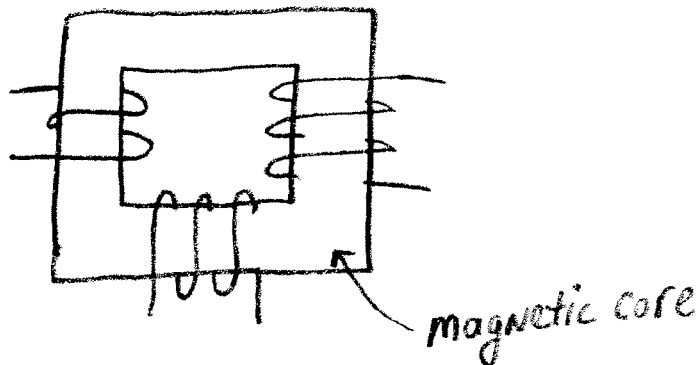
6. The physical construction of several coupled coils is shown. Carefully redraw this diagram on the solution sheet and then show one possible location for the dot marking on each coil. Clearly show the direction of the flux in the magnetic material if current is injected into each dot.



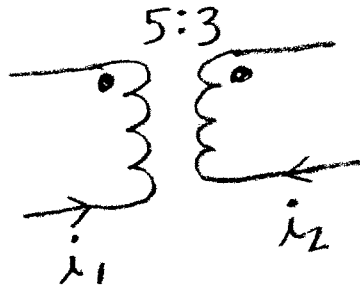
7. Name one property of ideal transformers, excluding the voltage, current, and impedance transformation relationships.
8. Determine the relationship between i_2 and i_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



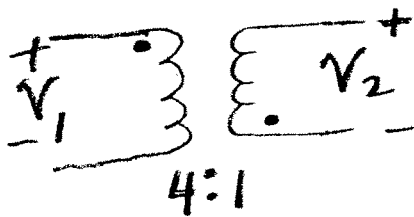9. Determine the relationship between v_2 and v_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.




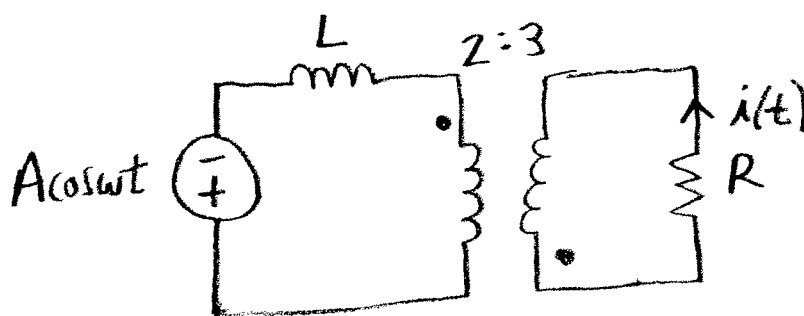10. For the following circuit involving an ideal transformer, determine $i(t)$ (in the time domain).



$$\frac{I}{I_X} = \frac{2}{3}$$

$$I_X = \frac{2}{3} I$$

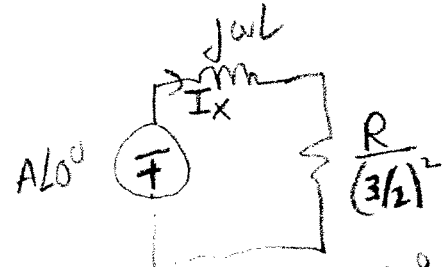

$$I_X = \frac{-A/3}{j\omega L + \frac{R}{(3/2)^2}}$$

Printed Name: SOLN24 pts
total

Signature: _____

Answer Sheet (Provide Units)


1 1. $\frac{1}{2\pi\sqrt{15}}$ Hz

1 2. R

2 3. LPF

2 4. $\frac{(j\omega L \parallel R_3)}{(j\omega L \parallel R_3) + (R_2 \parallel \frac{1}{j\omega C})}$

3 5. $\frac{\sqrt{(\omega L)^2 + R^2}}{\sqrt{(-2\omega^2 LCR)^2 + (\omega CR^2)^2}}$ OR $\frac{\sqrt{(\frac{L}{C})^2 + (\frac{-R}{\omega C})^2}}{\sqrt{(R^2)^2 + (2\omega LR)^2}}$

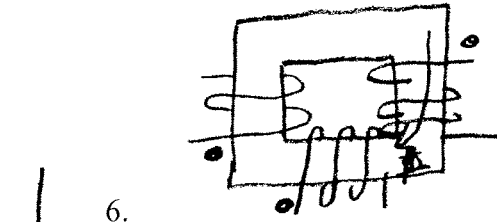
1 7. No leakage flux

1 8. $\frac{i_2}{i_1} = \frac{-5}{3}$

$$1 \quad 9. \quad \frac{V_2}{V_1} = \frac{-1}{4}$$


$$4 \quad 10. \quad \frac{-2A}{3} \frac{1}{\sqrt{(\omega L)^2 + \left(\frac{R}{3A}\right)^2}} \cos\left(\omega t - \tan^{-1}\left(\frac{\omega L}{R/(3A)}\right)\right) A$$

1 11. infinite input resistance

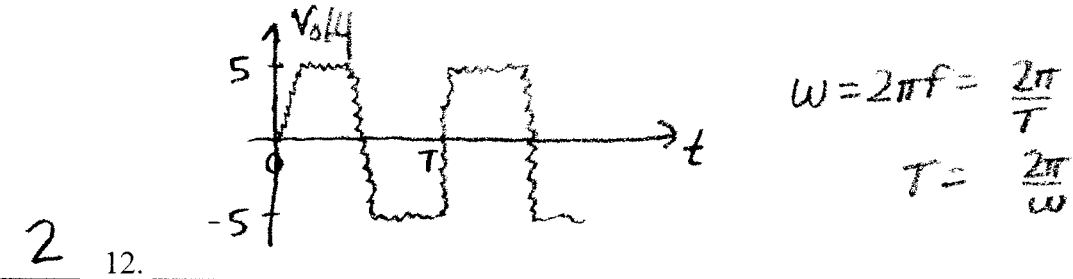

$$4 \quad 13. \quad \frac{-R_1}{j\omega L \left(R_1 + \frac{1}{j\omega C}\right)} = \frac{-R_1 C}{L(j\omega C R_1 + 1)}$$

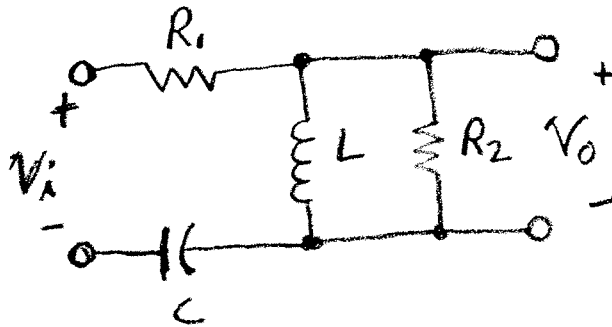4. Determine the transfer function $H(\omega) = V_o(\omega)/V_i(\omega)$ for the given using voltage division, current division, and/or Ohm's law. Do not simplify the expression. If needed, the symbol for two elements in parallel (e.g., $R_s \parallel R_L$) may be used.



5. Determine the magnitude of the given transfer function as done in class.


$$H(\omega) = \frac{j\omega L \parallel R}{\frac{1}{j\omega C} + R}$$

OR $\frac{j\omega LR}{\frac{1}{j\omega C} + j\omega L + R}$


FASTER
OR
 $\frac{\omega LR}{\sqrt{(\omega L)^2 + R^2} \sqrt{(\frac{1}{\omega C})^2 + R^2}}$

$$\frac{j\omega LR}{j\omega L + R} = \frac{j\omega LR}{\frac{1}{j\omega C} + R} = \frac{j\omega LR}{\frac{j\omega L + R}{j\omega C} + j\omega L + R^2} = \frac{j\omega LR}{\omega^2 LCR + j\omega R^2 C}$$

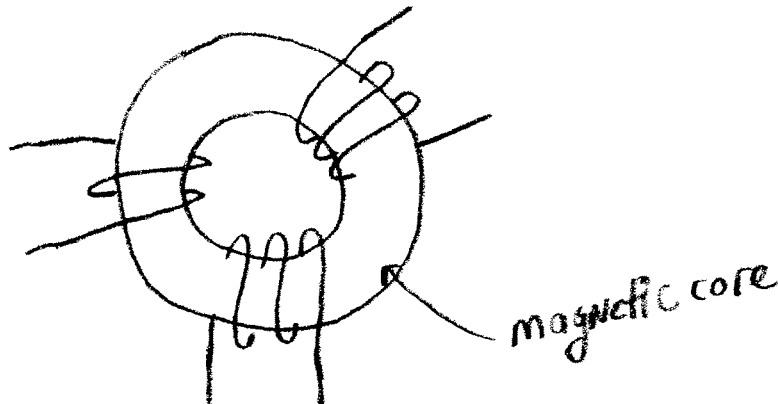
6. The physical construction of several coupled coils is shown. Carefully redraw this diagram on the solution sheet and then show one possible location for the dot marking on each coil. Clearly show the direction of the flux in the magnetic material if current is injected into each dot.



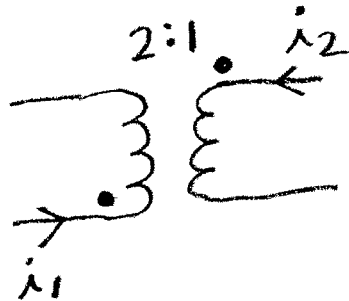
7. Name one property of ideal transformers, excluding the voltage, current, and impedance transformation relationships.
8. Determine the relationship between i_2 and i_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



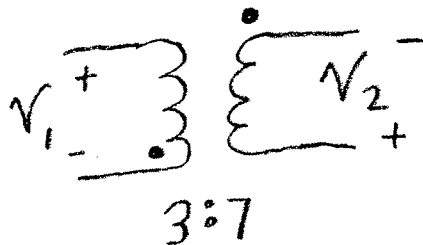9. Determine the relationship between v_2 and v_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



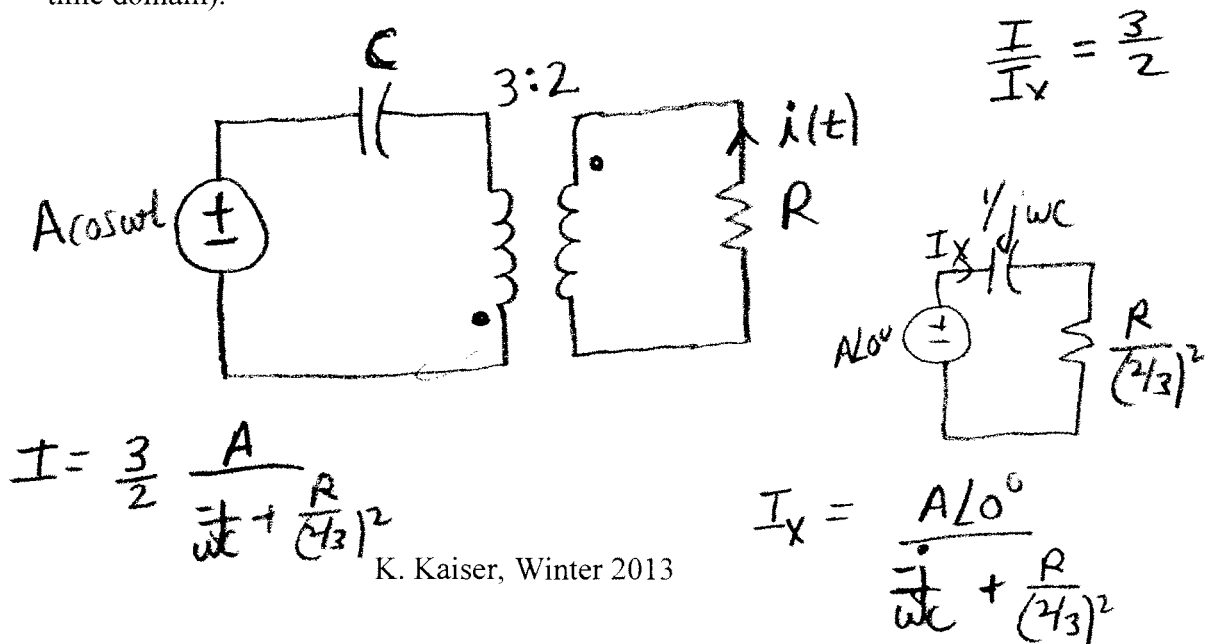10. For the following circuit involving an ideal transformer, determine $i(t)$ (in the time domain).



Printed Name: SOLN

24 pts total

Signature: _____

Answer Sheet (Provide Units)


1 1. $\frac{1}{2\pi\sqrt{28}}$ Hz

1 2. R

2 3. BRF

2 4. $\frac{(j\omega L // R_2)}{(j\omega L // R_2) + R_1 + \frac{1}{j\omega C}}$

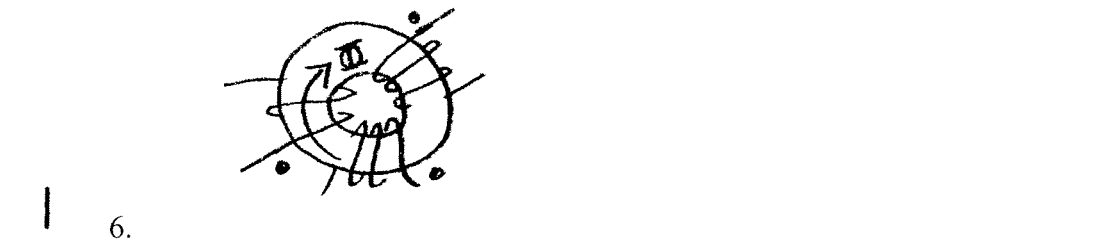3 5. $\frac{\sqrt{(-\omega^2 LCR)^2}}{(R - \omega^2 LCR)^2 + (\omega L + \omega RC)^2}$ OR $\frac{WLR}{\left(\frac{L}{C} + R^2\right)^2 + \left(WLR - \frac{R}{\omega C}\right)^2}$




1 7. zero leakage flux

1 8. $\frac{i_2}{i_1} = \frac{-2}{1}$

$$1 \quad 9. \quad \frac{v_2}{v_1} = \frac{7}{3}$$

$$4 \quad 10. \quad \left(\frac{3}{2} A \sqrt{\frac{(-1)^2}{(\omega C)^2} + \left(\frac{R}{(4/3)} \right)^2} \right) \cos \left(\omega t - \tan^{-1} \frac{1/\omega C}{R/(4/3)} \right) A$$

1 11. infinite open-loop gain

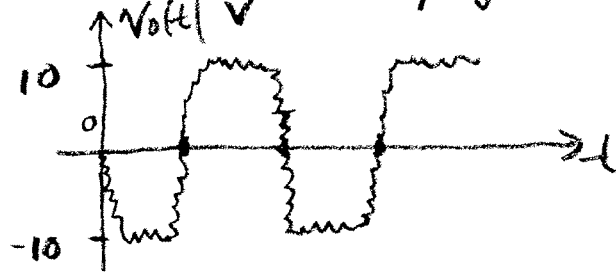


$$\omega = 2\pi f = \frac{2\pi}{T}$$

$$T = \frac{2\pi}{\omega}$$

2 12.

$$4 \quad 13. \quad \frac{j\omega L}{R_2(j\omega L + R_1)}$$

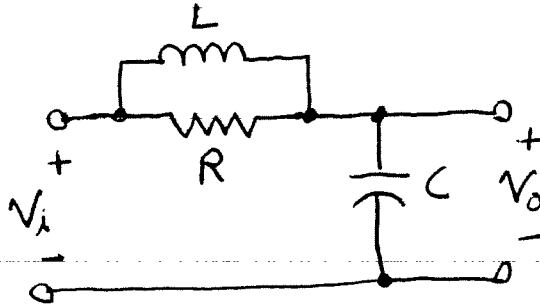4. Determine the transfer function $H(\omega) = V_o(\omega)/V_i(\omega)$ for the given using voltage division, current division, and/or Ohm's law. Do not simplify the expression. If needed, the symbol for two elements in parallel (e.g., $R_s \parallel R_L$) may be used.




5. Determine the magnitude of the given transfer function as done in class.


$$H(\omega) = \frac{R}{R + \left(j\omega L \parallel \frac{1}{j\omega C} \right)}$$

$$\frac{R}{R + \frac{j\omega L \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}}} = \frac{R}{R + \frac{j\omega L}{- \omega^2 LC + 1}} = \frac{R(1 - \omega^2 LC)}{R(1 - \omega^2 LC) + j\omega L}$$

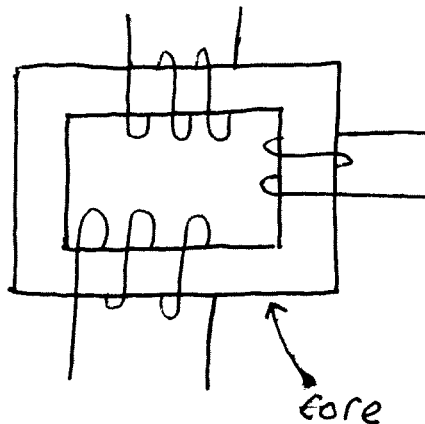
6. The physical construction of several coupled coils is shown. Carefully redraw this diagram on the solution sheet and then show one possible location for the dot marking on each coil. Clearly show the direction of the flux in the magnetic material if current is injected into each dot.



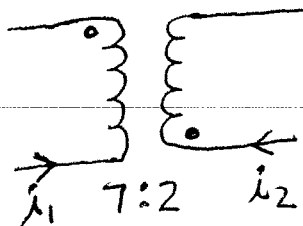
7. Name one property of ideal transformers, excluding the voltage, current, and impedance transformation relationships.
8. Determine the relationship between i_2 and i_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



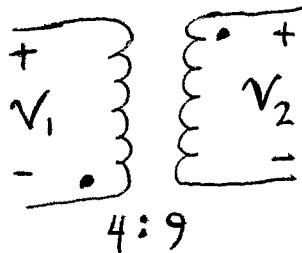9. Determine the relationship between v_2 and v_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



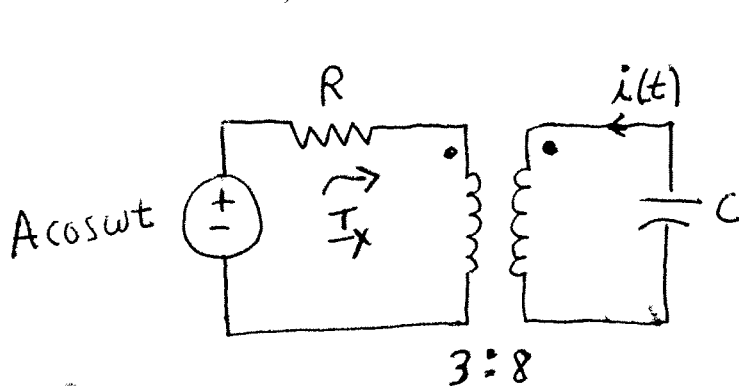10. For the following circuit involving an ideal transformer, determine $i(t)$ (in the time domain).



$$\frac{i}{i_x} = -\frac{3}{8}$$

$$i = -\frac{3}{8} i_x$$

$$I_x = \frac{A \angle 0^\circ}{R + \frac{1}{j\omega C} \left(\frac{8}{3}\right)^2}$$

$$= \frac{A \angle 0^\circ j\omega C}{\frac{9}{64} + j\omega RC}$$

$$= \frac{A \omega C}{\frac{9}{64} + j\omega RC} \angle \tan^{-1} \omega RC$$

OR

$$I_x = \frac{A \angle 0^\circ}{R - \frac{j}{\omega C} \left(\frac{8}{3}\right)^2}$$

$$i_x(t) = \frac{A}{\sqrt{R^2 + \left(\frac{9}{64\omega C}\right)^2}} \cos(\omega t - \tan^{-1} \frac{9}{64\omega RC})$$

22 pts total

Printed Name: SOLUTION

Signature: _____

Answer Sheet (Provide Units)


1 1. $\frac{1}{\sqrt{18}}$ rad/sec or $\frac{1}{2\pi\sqrt{18}}$ Hz

1 2. R

2 3. BRF

2 4. $\frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + (R // j\omega L)}$

2 5. $\frac{|R(1 - \omega^2 LC)|}{\sqrt{[R(1 - \omega^2 LC)]^2 + (\omega L)^2}}$

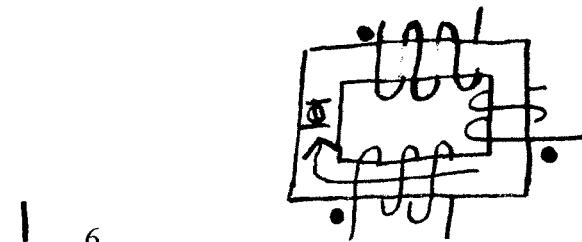


1 7. no leakage flux, infinite permeability, no R losses, . . .

1 8. $\frac{i_2}{i_1} = +\frac{1}{2}$

1 9. $\frac{V_2}{V_1} = -\frac{9}{4}$


3 10. $\frac{-3}{8} \frac{A\omega C}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + 90^\circ - \tan^{-1}(\omega RC))$
(Note: There is a handwritten '9/64' written below the denominator in the original image.)

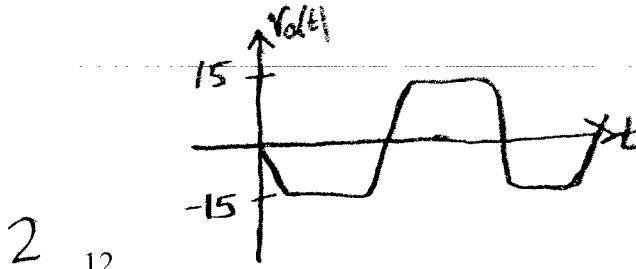1 11. infinite input resistance, zero input current, zero input Δ , ...




4 13. $\frac{V_o}{V_i} = \frac{1 - j\omega RC}{1 + j\omega RC} = \frac{2}{1 + j\omega RC} - 1$

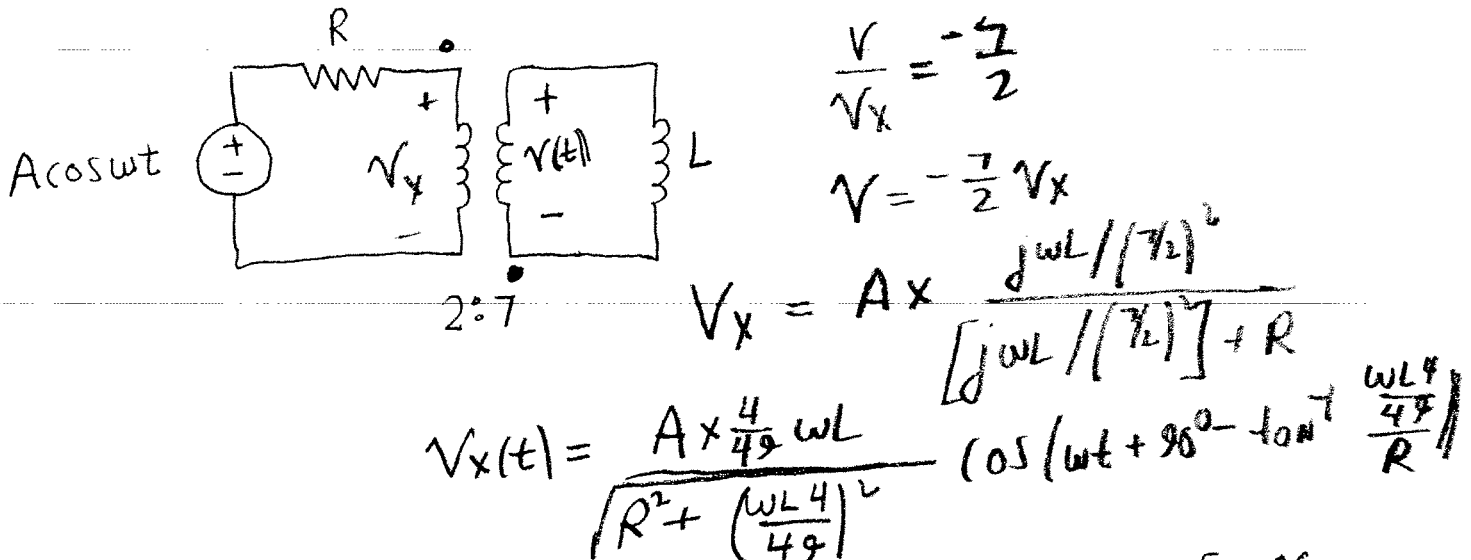16. For the following circuit involving an ideal transformer, determine $v(t)$ (in the time domain).



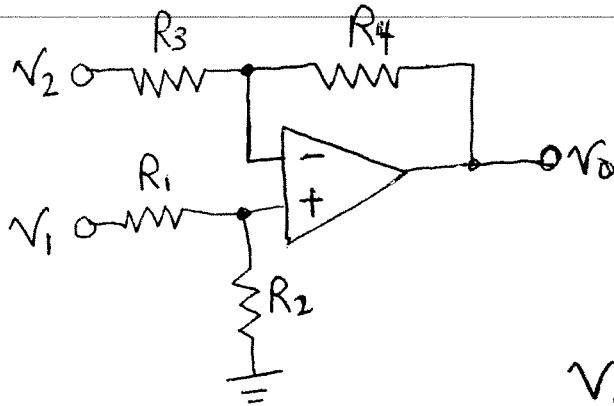17. For the following circuit involving an ideal op, determine the relationship for v_o as a function of v_1 , v_2 , and the R 's




$$v_o = v_1 \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3}\right) - v_2 \left(\frac{R_4}{R_3}\right)$$

$$2 \quad 15. \quad \frac{R}{\sqrt{1 + (\omega RC)^2} \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$2 \quad 16. \quad \frac{-7}{2} \frac{A \frac{4}{49} \omega L}{\sqrt{R^2 + \left(\frac{\omega L 4}{49}\right)^2}} \cos\left(\omega t + 90^\circ - \tan^{-1} \frac{\omega L 4}{R}\right) V$$

$$3 \quad 17. \quad v_0 = v_1 \frac{R_2}{R_1 + R_2} \left(1 + \frac{R_4}{R_3}\right) - v_2 \left(\frac{R_4}{R_3}\right)$$

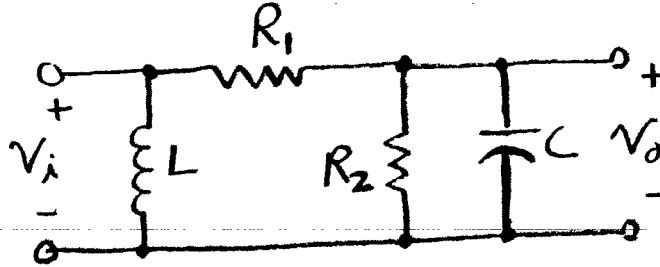4. Determine the transfer function $H(\omega) = V_o(\omega)/V_i(\omega)$ for the given using voltage division, current division, and/or Ohm's law. Do not simplify the expression. If needed, the symbol for two elements in parallel (e.g., $R_s \parallel R_L$) may be used.




5. Determine the magnitude of the given transfer function as done in class.


$$H(\omega) = \frac{R + \frac{1}{j\omega C}}{R + (j\omega L \parallel R)}$$

$$\frac{R + \frac{1}{j\omega C}}{R + \frac{j\omega L R}{R + j\omega L}} = \frac{(R + j\omega L)(R - \frac{j}{\omega C})}{R^2 + j\omega L R + j\omega L R}$$

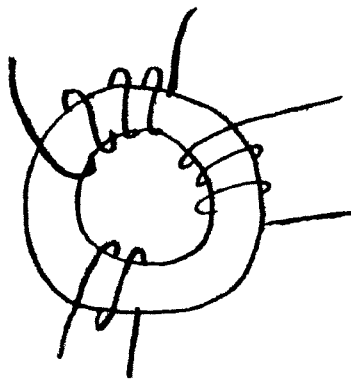
6. The physical construction of several coupled coils is shown. Carefully redraw this diagram on the solution sheet and then show one possible location for the dot marking on each coil. Clearly show the direction of the flux in the magnetic material if current is injected into each dot.



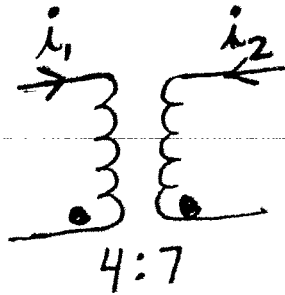
7. Name one property of ideal transformers, excluding the voltage, current, and impedance transformation relationships.
8. Determine the relationship between i_2 and i_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



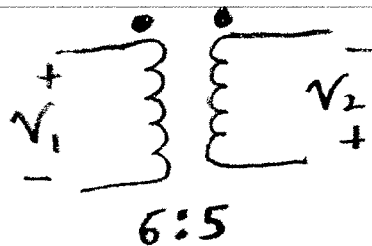9. Determine the relationship between v_2 and v_1 (as a function of the turns ratio) for the following ideal transformer operating in sinusoidal steady state.



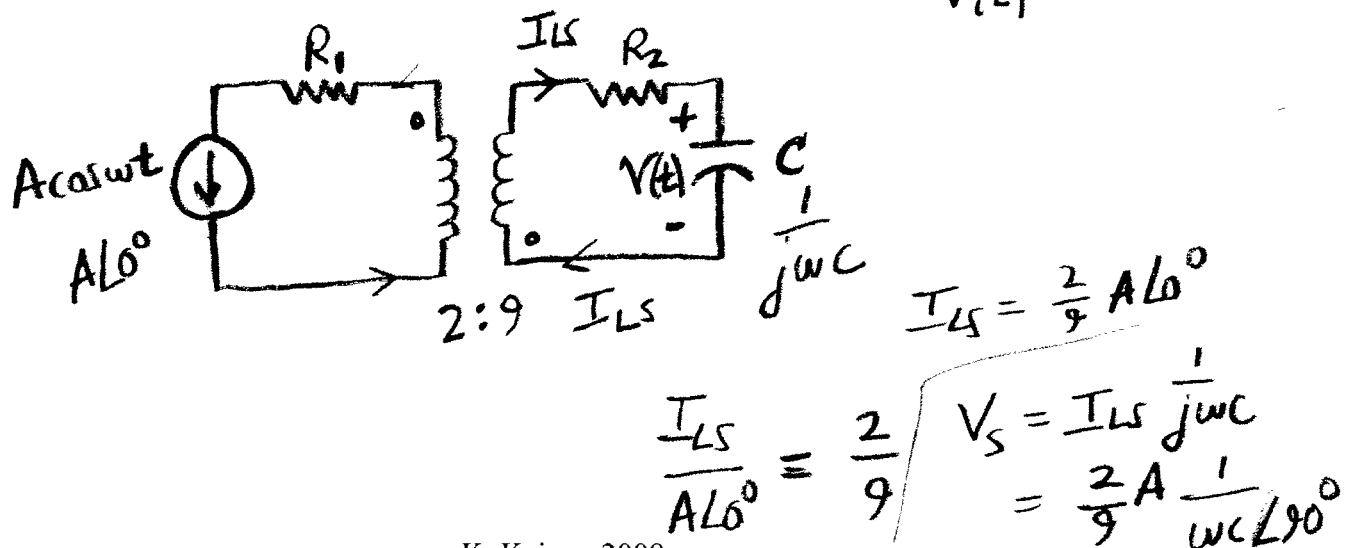10. For the following circuit involving an ideal transformer, determine $v(t)$ (in the time domain).



Printed Name: SOLN

Signature: _____

Answer Sheet (Provide Units)


1 1. $\frac{1}{\sqrt{10}}$ rad/s

1 2. R

2 3. BRF

3 4. $\frac{\frac{1}{j\omega C} \parallel R_2}{(\frac{1}{j\omega C} \parallel R_2) + R_1}$

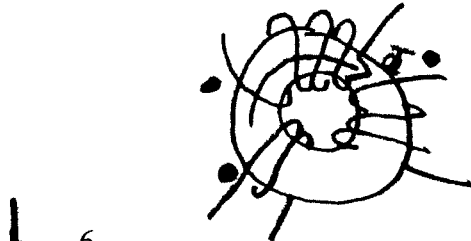3 5. $\frac{\sqrt{R^2 + (\omega L)^2} \sqrt{R^2 + (\frac{1}{\omega C})^2}}{\sqrt{(R^2)^2 + (2\omega LR)^2}}$




1 7. infinite permeability of core

1 8. $i_2 / i_1 = -4/7$

1 9. $v_2/v_1 = -5/6$

3 10. $v(t) = \frac{2}{9} \frac{A}{\omega C} \cos(\omega t - 90^\circ) \text{ V}$


1 11. $V_- - V_+ = 0$ with feedback

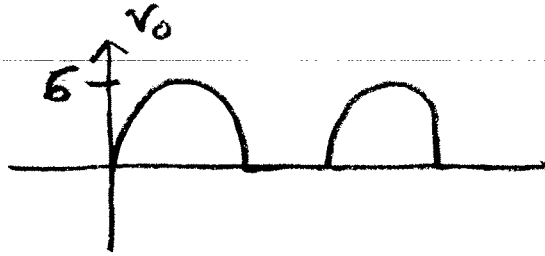

2 12.

5 13. $\frac{I_2}{V_i} = \frac{1}{R_1 R_2} \left(\frac{1}{j\omega C} \parallel R_2 \right) = \frac{1}{R_1} \frac{1}{1 + j\omega C R_2}$

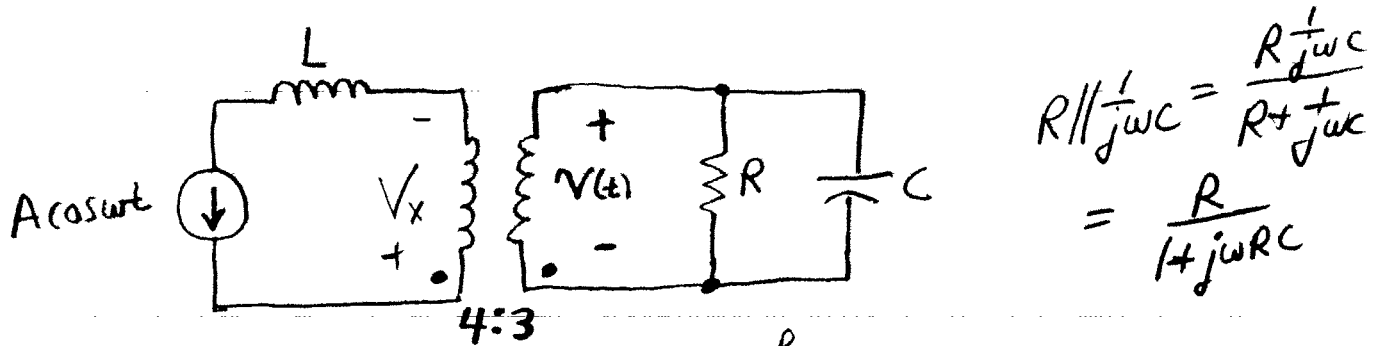16. For the following circuit involving an ideal transformer, determine $v(t)$ (in the time domain).



$$R \parallel \frac{1}{j\omega C} = \frac{R \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{R}{1 + j\omega RC}$$


$$V_x = (A \angle 0^\circ) \frac{R}{(3/4)^2 (1 + j\omega RC)}$$

$$V = -\frac{3}{4} V_x = -A \frac{R}{1 + j\omega RC} \left(\frac{4}{3}\right)$$

$$V/V_x = -3/4$$

17. For the following circuit involving an ideal op, determine the relationship

$$\frac{V_o(\omega)}{V_i(\omega)}$$

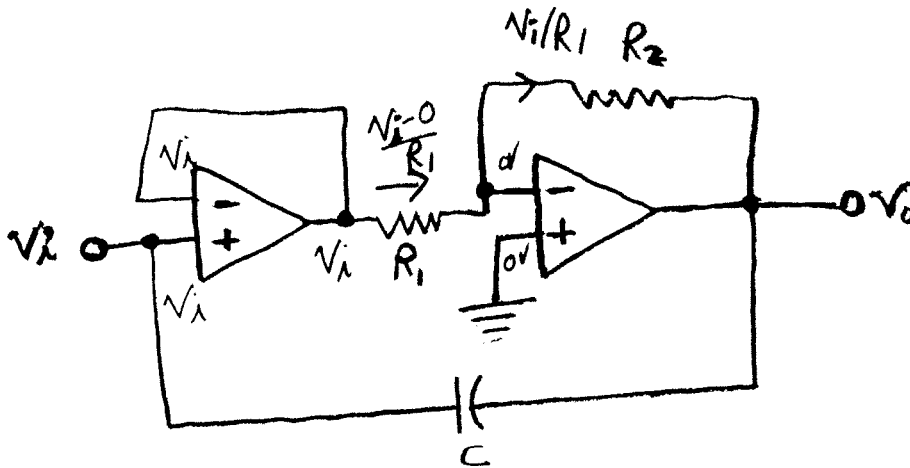

$$0 + \frac{v_1 R_2}{R_1} + v_0 = 0$$

$$\frac{v_0}{v_1} = -\frac{R_2}{R_1}$$

$$3 \quad 15. \quad \frac{WLR}{\sqrt{R^2 + (\omega L)^2}} \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2} \cdot \frac{WLR}{\sqrt{\left(R^2 + \frac{L}{C}\right)^2 + \left(WLR - \frac{R}{\omega C}\right)^2}}$$

$\frac{R\omega L}{\sqrt{R^2 + (\omega L)^2}}$
 $\frac{R\omega L}{\sqrt{R^2 + (\omega L)^2}}$

$$5 \quad 16. \quad -\frac{4R}{3} \frac{1}{\sqrt{1 + (\omega RC)^2}} \cos(\omega t - \tan^{-1}(\omega RC))$$

$$3 \quad 17. \quad \frac{V_o}{V_i} = \frac{-R_2}{R_1}$$